

# Hardware Protection Circuits

PROTECTION	DESCRIPTION	PAGE
<b>Reverse Polarity</b>	Prevents backward voltage	3
<b>Overshoot</b>	Shields against voltage surges	4
<b>Undervoltage</b>	Disables system if voltage too low	5
<b>Power Sequence</b>	Controls startup to avoid latch-up	6
<b>Overcurrent</b>	Limits current beyond thresholds	7
<b>Short Circuit</b>	Cuts off power during hard shorts	8
<b>Inrush Current</b>	Slows startup to protect the circuit	9
<b>Reverse Current</b>	Stops back flowing current	10
<b>Static Discharge</b>	Guards components from static	11
<b>Pin Overvoltage</b>	Protects pins from voltage spikes	12
<b>Cross-talk</b>	Eliminates unwanted signal	13
<b>Data Line</b>	Secures digital communication	14
<b>Supply Spike</b>	Smooths fast voltage fluctuations	15
<b>Hi-Freq Filtering</b>	Eliminates RF and digital noise	16
<b>Input Filter</b>	Blocks EMI and protects upstream	17
<b>Ind. Kickback</b>	Prevents coil voltage spikes	18
<b>Hot-Plugging</b>	Safe Connect under power	19
<b>High-Surge</b>	Handles voltage transients	20
<b>Isolation</b>	Electrical separation for safety	21
<b>Watchdog</b>	Monitors system health	22

*By Shimi Cohen*

# TABLE OF CONTENT

<b>Power Supply Protection .....</b>	<b>3</b>
<b>Reverse Polarity Protection</b>	<b>3</b>
<b>Overvoltage Protection (DC Input)</b>	<b>4</b>
<b>Undervoltage Lockout Protection</b>	<b>5</b>
<b>Power Sequencing Protection</b>	<b>6</b>
<b>Current Protection .....</b>	<b>7</b>
<b>Overcurrent Protection</b>	<b>7</b>
<b>Short Circuit Protection</b>	<b>8</b>
<b>Inrush Current Limiting</b>	<b>9</b>
<b>Reverse Current Protection</b>	<b>10</b>
<b>Signal Integrity Protection .....</b>	<b>11</b>
<b>Static Discharge (ESD) Protection</b>	<b>11</b>
<b>Input Pin Overvoltage Protection</b>	<b>12</b>
<b>Cross-talk Prevention</b>	<b>13</b>
<b>Data Line Protection</b>	<b>14</b>
<b>Electromagnetics .....</b>	<b>15</b>
<b>Power Supply Spike Protection</b>	<b>15</b>
<b>High Frequency Noise Filtering</b>	<b>16</b>
<b>Input Filter Protection</b>	<b>17</b>
<b>System Level Protection .....</b>	<b>18</b>
<b>Inductive Kickback Protection</b>	<b>18</b>
<b>Hot-Plugging Protection</b>	<b>19</b>
<b>Advanced Protection .....</b>	<b>20</b>
<b>High-Energy Surge Protection</b>	<b>20</b>
<b>Isolation Protection</b>	<b>21</b>
<b>Watchdog Protection</b>	<b>22</b>

# POWER SUPPLY PROTECTION

## Reverse Polarity Protection

### Mitigation

Prevents damage from incorrect power connection polarity.

### Explanation

When power connectors are wired backwards, reverse polarity can destroy ICs instantly. Protection circuits block reverse current while allowing forward current.

### Components Used

- **Schottky Diode:** Low forward drop (0.2-0.4V), fast switching
- **P-Channel MOSFET:** Near-zero voltage drop, higher efficiency
- **Ideal Diode Controller:** Active rectification with minimal loss

Protection Method	Voltage Drop	Power Loss	Cost	Complexity
Schottky Diode	0.2-0.4V	High	Low	Simple
P-Channel MOSFET	<0.1V	Very Low	Medium	Medium
Ideal Diode IC	<0.05V	Minimal	High	Complex

### Practical Example


Battery Protection Circuit

#### Circuit

BAT in → [PMOS + Zener] → BAT out

#### Components

- PMOS
- Zener Diode

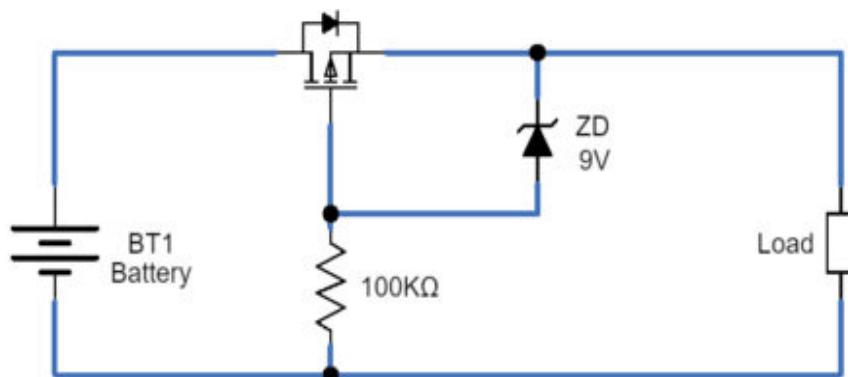

# Overvoltage Protection (DC Input)

## Mitigation

Clamps input voltage to safe operating levels.

## Explanation

Transient overvoltage from power supplies, automotive load dumps, or industrial environments can exceed IC absolute maximum ratings. Protection circuits either clamp or crowbar excessive voltage.

## Components Used

- **TVS Diodes:** Fast response (<1ns), self-resetting
- **Zener Diodes:** Precise voltage clamping, lower cost
- **Crowbar Circuits:** SCR-based, triggers fuse/breaker

Component	Response Time	Clamping Accuracy	Energy Handling	Reset
TVS Diode	<1ns	±5%	400W-30kW	Automatic
Zener Diode	<10ns	±2%	1W-50W	Automatic
Crowbar SCR	<1μs	±10%	Very High	Manual

## PRACTICAL EXAMPLE

24V Industrial Supply

### Input

24V ±20% (19.2V - 28.8V)

### Protection


SMBJ30A TVS (30V breakdown, 48.4V clamping)

### Load

Sensitive 3.3V logic requiring <6V absolute max
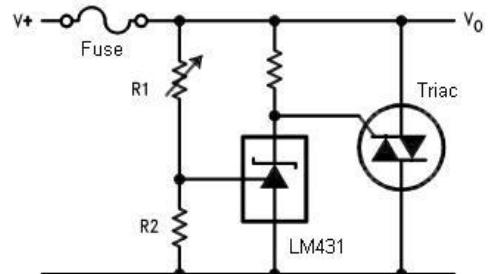
### Result

Any spike >30V gets clamped to <48V, triggering upstream fuse



# Undervoltage Lockout Protection

## Mitigation

Prevents operation when supply voltage is insufficient.

## Explanation

Low supply voltages cause unpredictable digital logic states, corrupted memory, and potential system damage. UVLO circuits maintain reset until voltage reaches safe operating levels.

## Components Used

- **UVLO ICs:** Dedicated voltage supervisors with precise thresholds
- **PMIC Integration:** Power management ICs with built-in UVLO
- **Comparator Circuits:** Discrete implementations with hysteresis

## Practical Example

MCU System


### Application

ARM Cortex-M4 @ 3.3V
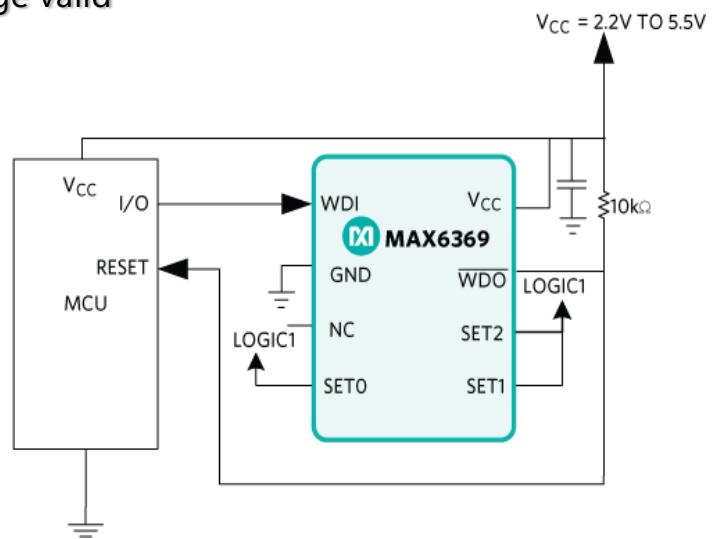
### UVLO IC

MAX6369

- Rising threshold: 3.08V (typical)
- Falling threshold: 2.93V (typical)
- Hysteresis: 150mV prevents oscillation
- Reset delay: 200ms after voltage valid



# Power Sequencing Protection

## Mitigation

Ensures correct power-up and power-down order.

## Explanation

Complex systems with multiple supply rails require specific sequencing to prevent latch-up, excessive current draw, or logic corruption.

## Components Used

- **Sequencer ICs:** Programmable timing and thresholds
- **"Oring" Diodes:** Prevents reverse current between rails
- **Power MOSFETs:** Controlled rail switching

## Practical Example

FPGA Power System


### Sequence Required

1. 5V First
2. 3.3V I/O
3. 2.5V Auxiliary
4. 1.8V Transceiver
5. 1.5V DDR memory
6. 1.2V Core Logic
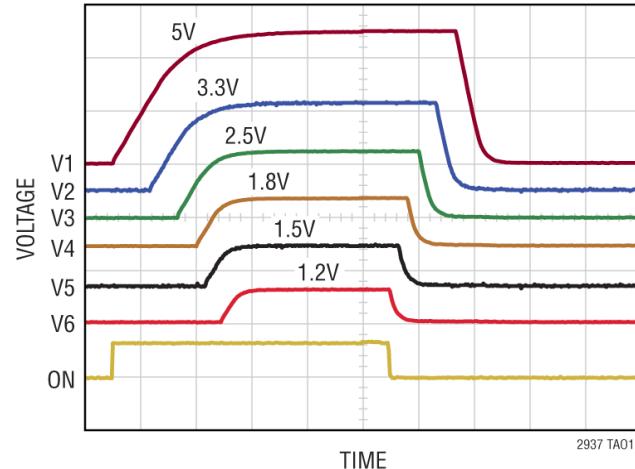
### Implementation

LTC2937 6-channel sequencer

- Monitors all rails with 0.8% accuracy
- Programmable delays via I2C
- Automatic shutdown on any rail fault



# CURRENT PROTECTION

## Overcurrent Protection

### Mitigation

Breaks circuit when current exceeds safe limits.

### Explanation

Excessive current causes component heating, trace damage, and potential fire hazards. Current limiting protects both the supply and load circuits.

### Components Used

- **Fuses:** One-time protection, very reliable
- **Circuit Breakers:** Resettable, mechanical operation
- **Current Limiters:** Active electronic limiting

Protection Type	Response Time	Reset Method	Accuracy	Cost
Fast-Blow Fuse	0.1-10ms	Replace	±20%	Very Low
Slow-Blow Fuse	1-100ms	Replace	±20%	Low
PTC Resettable	0.1-10s	Automatic	±30%	Medium
Electronic Limit	<1µs	Automatic	±5%	High

### Practical Example

USB Power Delivery:

#### Application

USB-C 5V/3A Power Supply

#### Primary

3.5A fast-blow fuse (automotive grade)

#### Secondary

MIC2097 current-limited switch

- 3.1A current limit (typical)
- 85mΩ on-resistance
- Thermal shutdown at 165°C
- Automatic retry after fault clears



# Short Circuit Protection

## Mitigation

Rapidly disconnects power during short circuits.

## Explanation

Short circuits create near-infinite current demand, limited only by supply impedance and trace resistance. Protection must act within microseconds to prevent damage.

## Components Used

- Poly-fuses (PTC): Self-resetting, temperature activated
- Current Switches: Electronic, fast response
- Magnetic Breakers: Instantaneous trip on high current

## Practical Example

DC Motor Drive:

### Application


24V/10A Brushed DC Motor

### Protection

Bourns MF-R300 PTC + TPS2065 Load Switch
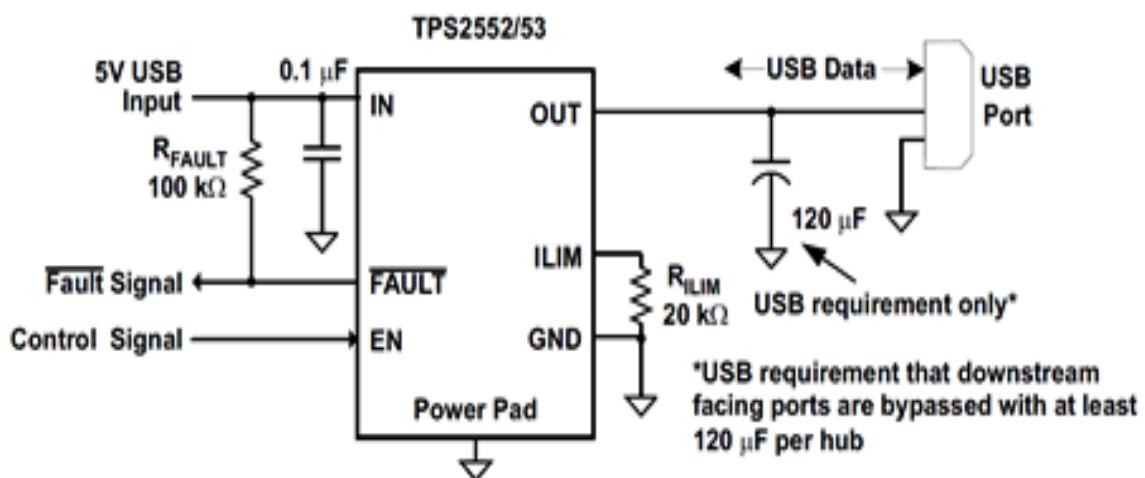
### PTC Spec

- Hold current 3.0A
- Trip current 6.0A
- Max voltage 30V



# Inrush Current Limiting

## MITIGATION

Controls surge current during power-up.

## EXPLANATION

Capacitive loads create high inrush currents that can trip protection circuits or damage power supplies. Soft-start circuits gradually increase current.

## COMPONENTS USED

- **NTC Thermistors:** Passive, temperature-dependent resistance
- **Soft-start ICs:** Active control with precise timing
- **Series Resistance:** Simple, constant limitation

## PRACTICAL EXAMPLE

Switch-Mode Power Supply:

### Application

100W SMPS with 2200 $\mu$ F Input Capacitor

### Without Protection

50A+ inrush spike

### With 5 $\Omega$ NTC (B57364S0509M)

- Cold resistance: 5 $\Omega$  (limits to 4.8A @ 24V)
- Hot resistance: 0.05 $\Omega$  (minimal steady-state loss)
- Time constant: ~2 seconds to reach 10% resistance



# Reverse Current Protection

## Mitigation

Prevents current flow in reverse direction.

## Explanation

Reverse current occurs during power-down, battery backup switching, or system faults. Can cause unexpected operation or component stress.

## Components Used

- Schottky Diodes: Low forward drop, fast recovery
- Ideal Diode Controllers: MOSFET-based, minimal loss
- Body Diode Blocking: Additional MOSFET in series

## Practical Example

Battery Backup System

### Application

5V System with 6V Battery Backup

### Main Supply


5V/2A switching regulator

Backup: 4x AA NiMH (4.8V nominal)
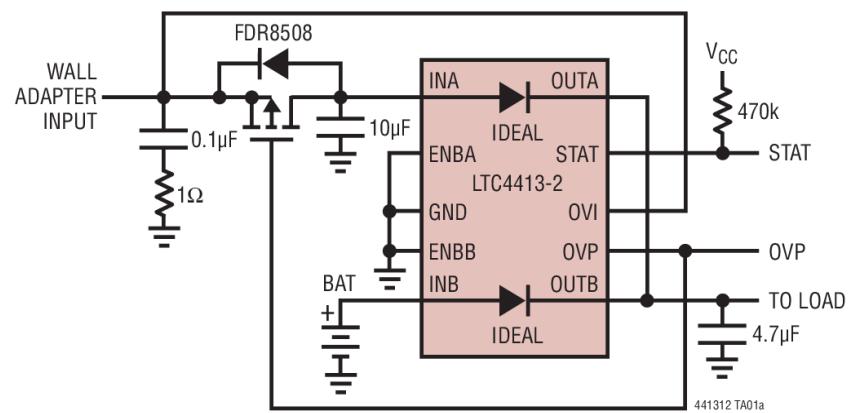
### Protection

LTC4413 Dual Input Power Manager

- Automatic switchover at 4.5V main supply
- <25mV forward drop on both paths
- Prevents reverse current in both directions



# SIGNAL INTEGRITY PROTECTION

## Static Discharge (ESD) Protection

### Mitigation

Shunts electrostatic discharge to ground.

### Explanation

Human body can generate 15kV+ static charges. ESD events create nanosecond current spikes exceeding 30A, destroying junction interfaces in semiconductors.

### Components Used

- **TVS Diodes:** Bidirectional clamping for signal lines
- **ESD Arrays:** Multi-channel protection in single package
- **Series Resistors:** Current limiting during ESD events

ESD Standard	Test Voltage	Current Peak	Duration	Application
HBM (Human)	±8kV	30A	100ns	General handling
MM (Machine)	±800V	100A	10ns	Manufacturing
CDM (Device)	±2kV	20A	1ns	IC-level stress

### Practical Example

USB Interface Protection

#### Interface


USB 2.0 Data Lines (D+, D-)

#### ESD Protection

USBLC6-2SC6
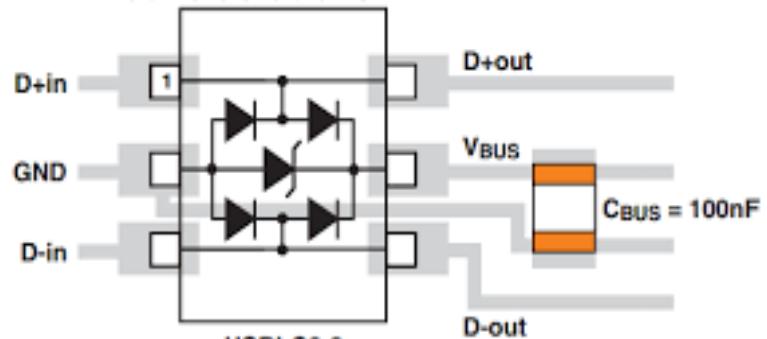
#### Specifications

- Clamping voltage: 10V @ 1A
- Leakage current: <1µA
- Capacitance: 7pF (maintains signal integrity)
- ESD rating: ±15kV Contact, ±8kV Air Gap



# Input Pin Overvoltage Protection

## Mitigation

Protects MCU and logic pins from voltage spikes.

## Explanation

Digital inputs typically tolerate  $V_{CC} + 0.3V$  maximum. External signals, long cables, or system faults can inject higher voltages causing latch-up or permanent damage.

## Components Used

- Series Resistor: Current limiting (1k $\Omega$ -10k $\Omega$  typical)
- Zener Diodes (two): Precise voltage reference clamping

## Practical Example

Industrial 24V Input to 3.3V Logic

### Signal Path


24V\_SENSOR → Protection → MCU\_GPIO

### Protection Circuit

1. 100 $\Omega$  series resistor (current limit)
2. Schottky to VCC (clamp positive)
3. Schottky to GND (clamp negative)
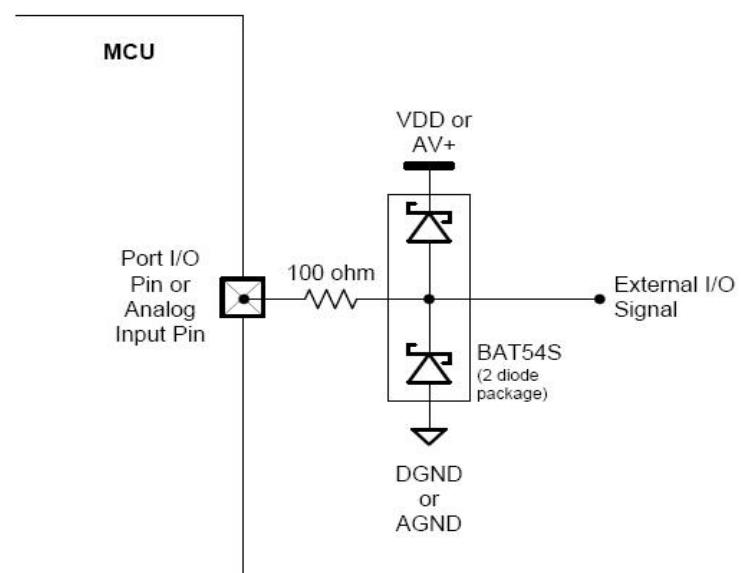
### Result

Any input from -0.7V to +40V safely clamped to 0V-3.6V



# Cross-talk Prevention

## Mitigation

Prevents signal interference between traces.

## Explanation

High-speed digital switching creates electromagnetic fields that couple into adjacent traces. Coupling increases with frequency, trace length, and proximity.

## Components Used

- **Ground Traces:** Shielding between sensitive signals
- **Differential Pairs:** Balanced signaling with noise immunity
- **Guard Rings:** Grounded traces surrounding critical signals

## Design Rules

- **3W Rule:** Space traces  $3 \times$  trace width apart
- **Microstrip:** Controlled impedance with ground plane
- **Via Stitching:** Connect ground planes every  $\lambda/20$

## Practical Example


High-Speed ADC Interface

### Application

16-bit 1MSPS ADC with SPI

### Critical Traces

CLK, MOSI, MISO (25MHz max)

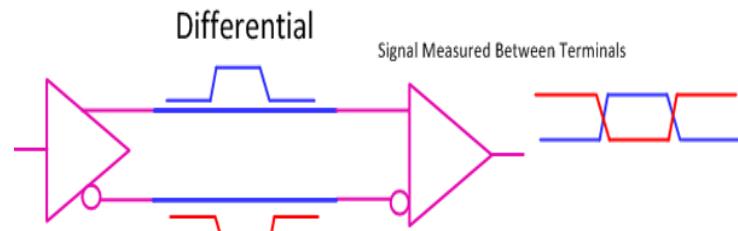

### Protection Method

- Differential clock pairs
- Ground traces between each signal
- Via stitching every 5mm
- Series termination:  $33\Omega$  resistors

### Result

<5% amplitude coupling between adjacent channels

# Data Line Protection

## Mitigation

Protects communication interfaces from transients.

## Explanation

Communication lines act as antennas for electromagnetic interference and provide paths for ESD injection. Protection must maintain signal integrity while clamping harmful voltages.

## Components Used

- **ESD Arrays:** Multi-channel protection for bus interfaces
- **Common Mode Chokes:** Differential noise filtering
- **Series Resistors:** Bandwidth limiting and current protection

## Practical Example

Automotive CAN Bus Protection

### Interface

CAN High/Low Differential Bus

Environment:

12V automotive with load dump transients

### Protection

1. NUP2105LT1G dual TVS array. Clamping: 24V @ 1A pulse. Capacitance: 85pF diff.
2. Common mode choke: 100µH
3. 120Ω termination with series 10Ω

### Result

Passes ISO 10605 ESD testing ( $\pm 25\text{kV}$ )

---

**SOT-23  
DUAL BIDIRECTIONAL  
VOLTAGE SUPPRESSOR  
350 W PEAK POWER**

---



SOT-23

# ELECTROMAGNETICS

## Power Supply Spike Protection

### Mitigation

Filters transients from switching power supplies.

### Explanation

mode converters create high-frequency noise due to rapid current switching. Spikes couple through parasitic inductance and capacitance, affecting sensitive analog circuits.

### Components Used

- **Decoupling Capacitors:** High-frequency filtering (ceramic)
- **Bulk Capacitors:** Low-frequency energy storage (electrolytic)
- **Ferrite Beads:** Resistive at high frequencies

Frequency Range	Capacitor Type	Typical Value	ESR	Application
DC-100kHz	Electrolytic	100µF-1000µF	0.1Ω	Bulk storage
100kHz-10MHz	Tantalum	10µF-100µF	0.01Ω	Mid-frequency
10MHz-1GHz	Ceramic X7R	0.1µF-10µF	0.001Ω	High-frequency
>1GHz	Ceramic COG	10pF-1000pF	<0.001Ω	Very Hi-Freq

### Practical Example

Analog Front-End Power

#### **Application**


24-bit ADC requiring  $<10\mu\text{Vpp}$  noise with 5V supply (500KHz Switching)

#### **Filter Network**

1.  $470\mu\text{F}$  electrolytic (bulk storage)
2.  $10\mu\text{F}$  tantalum (medium frequency)
3.  $0.1\mu\text{F}$  ceramic (switching noise)
4. 2 Ferrite beads: BLM21PG221SN1D
5.  $10\text{pF}$  ceramic (VHF suppression)
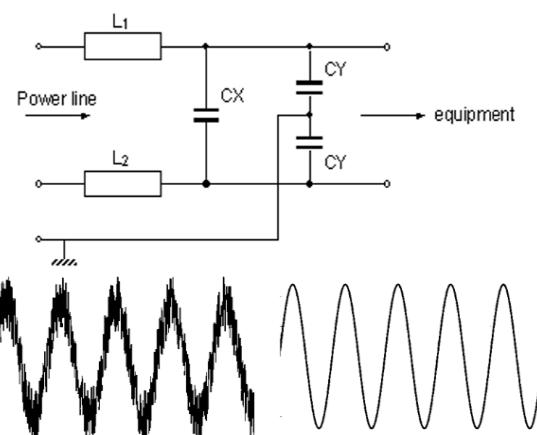
#### **Result**

Power supply noise  $<2\mu\text{Vpp}$  at ADC



# High Frequency Noise Filtering

## Mitigation

Removes transient noise above useful signal bandwidth.

## Explanation

High-frequency noise degrades analog performance, causes digital logic errors, and increases EMI emissions. Filtering removes unwanted spectral content.

## Components Used


- **RC Filters:** Simple, predictable roll off characteristics
- **LC Filters:** Sharper roll off, resonant peaking possible
- **Ferrite Beads:** Resistive damping of high frequencies

## Filter Design Guidelines

- **Cutoff Frequency:** 3-10× below noise frequency
- **Order:** Higher order = steeper roll-off
- **Q Factor:** Damping prevents resonant peaks

## Practical Example

Precision Voltage Reference:

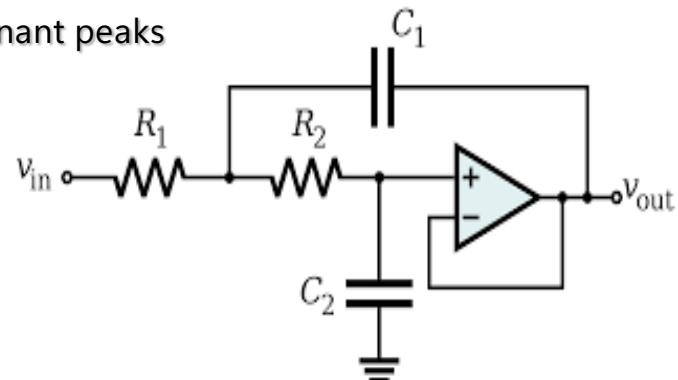

### Application

4.096V voltage reference for 18-bit ADC

Digital switching at 16MHz fundamental

Required Attenuation > 60dB @ 16MHz

### Implementation

- 3rd order Sallen-Key lowpass filter
- Cutoff frequency: 159kHz (-3dB)
- Components:  $R_1=R_2=1\text{k}\Omega$ ,  $C_1=2.2\text{nF}$ ,  $C_2=1\text{nF}$
- Op-amp: OPA827 (low noise, high PSRR)

### Result

<1 $\mu$ Vpp noise in measurement bandwidth

# Input Filter Protection

## Mitigation

Protects against power line disturbances.

## Explanation

AC power lines carry transients from lightning, motor switching, and power factor correction circuits. Input filters prevent these from entering sensitive equipment.

## Components Used

- **π-Filters:** Capacitor-inductor-capacitor configuration
- **Common Mode Chokes:** Balanced filtering of both AC lines
- **Metal Oxide Varistors:** High-energy transient clamping

## Practical Example

Industrial Power Supply Input

### Application

- 240VAC Industrial Environment
- Transient Spec required IEC 61000-4-5 (1.2/50μs, 4kV line-ground)

### Filter Design

1. MOV: 20mm varistor (385V RMS, 6kA surge)
2. Common mode choke: 2×4.7mH (Würth 744823047)
3. Differential capacitor: 100nF X2-class
4. Common mode capacitors: 2×2.2nF Y2-class

### Result

>40dB attenuation from 150kHz-30MHz



# SYSTEM LEVEL PROTECTION

## Inductive Kickback Protection

### Mitigation

Protects switching transistors from inductive voltage spikes.

### Explanation

When current is interrupted, stored magnetic energy creates voltage spikes following  $V = L(di/dt)$ . These spikes can exceed breakdown voltages.

### Components Used

- **Flyback Diodes:** Provides current path during switch-off
- **Snubber Circuits:** RC networks for gradual energy dissipation
- **TVS Diodes:** Fast clamping for high-energy spikes

### PRACTICAL EXAMPLE

Relay Drive Circuit

#### Load


12V automotive relay (coil: 150mH, 80mA)

#### Protection

1N4148 flyback diode
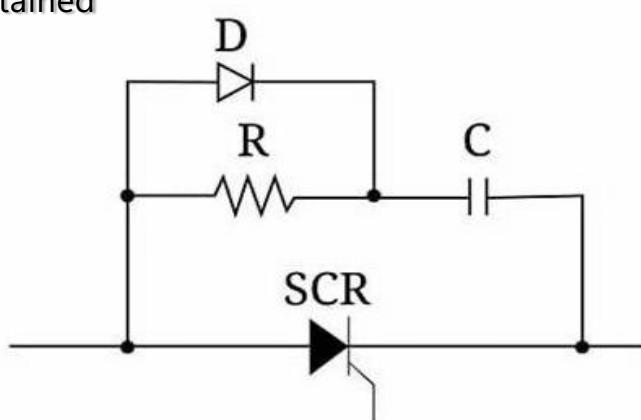
#### Analysis

- No protection: Spike =  $12V + L(di/dt) = 12V + 150mH \times (80mA/10ns) = 1212V$
- With flyback diode: Spike clamped to  $12V + 0.7V = 12.7V$
- MOSFET safe operating area maintained



# Hot-Plugging Protection

## Mitigation

Prevents damage during live circuit connection.

## Explanation

Connecting circuits under power creates transients from capacitor charging, ground potential differences, and connector arcing. Protection circuits manage these transition events.

## Components Used

- **TVS Diodes:** Transient voltage suppression
- **Soft-start Circuits:** Controlled power application
- **Current Limiters:** Inrush current management

## Practical Example

PCIe Card Installation

### Interface

PCIe x1 connector (3.3V, 12V supplies)

### Protection Requirements


- Hot-plug compatible
- Inrush current <1.5A peak
- Connector wear <100 cycles

### Implementation

1. TPS2065 hot-swap controller
2. Soft-start time: 10ms typical
3. Current limit: 1.5A with foldback
4. Undervoltage lockout: 2.9V threshold
5. Thermal shutdown: 150°C

### Result

Clean power-up with <50mV supply droop

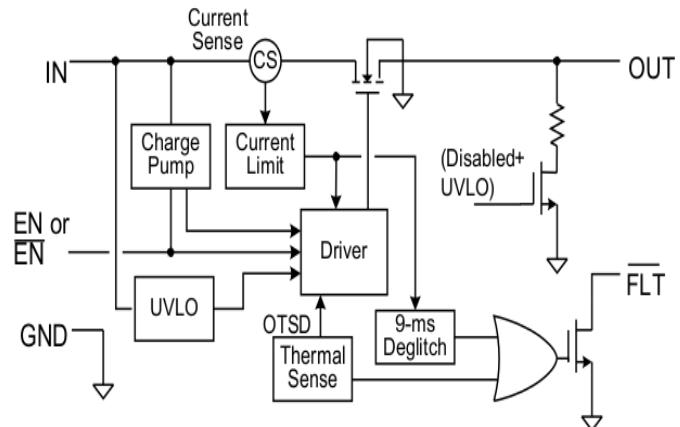

# ADVANCED PROTECTION

## High-Energy Surge Protection

### Mitigation

Diverts high-voltage, high-energy transients to ground.

### Explanation

Lightning strikes and power system faults create kilovolt transients with joules of energy. Standard TVS diodes cannot handle these energy levels without coordination with other protective devices.

### Components Used

- **Gas Discharge Tubes:** High-voltage breakdown, high energy handling
- **Metal Oxide Varistors:** Fast response, moderate energy
- **Crowbar Circuits:** SCR-triggered, very high energy

Device Type	Breakdown	Energy Handling	Response Time	Applications
GDT	90V-10kV	10J-1000J	1-100µs	Telecom, outdoor
MOV	18V-1800V	0.1J-10J	<25ns	AC mains, automotive
TVS	5V-600V	1mJ-400J	<1ns	Signal lines, DC supply

### Practical Example

Outdoor Ethernet Installation

#### Application

POE in outdoor security camera.


Direct lightning exposure possible.

#### Protection Cascade

1. Primary: Gas discharge tube (230V breakdown, 5kA, 10J)
2. Secondary: 36V MOV (bidirectional, 6kA peak)
3. Tertiary: PESD5V0S1BL TVS array on data lines
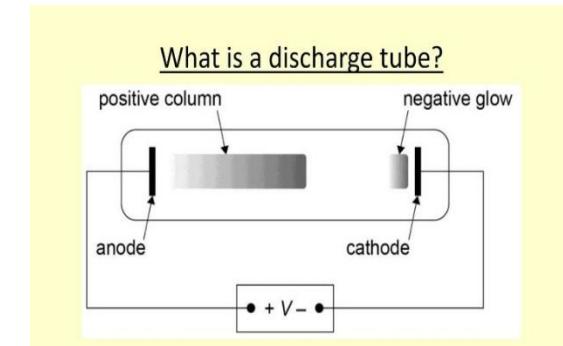
#### Result

Survives IEC 61000-4-5 Level 4 (4kV/2kA) transients



# Isolation Protection

## Mitigation

Eliminates ground loops and voltage differences between systems.

## Explanation

systems with different ground potentials creates current flow through signal connections. Isolation breaks the DC path while maintaining signal transfer.

## Components Used

- Optocouplers: LED-photodetector pairs for digital signals
- Isolation Transformers: Magnetic coupling for power and signals
- Capacitive Isolators: Electric field coupling for high-speed digital

## Practical Example

Industrial Process Control

### Application

4-20mA sensor interface with  
120VAC noise environment

### Isolation Requirements

- 2.5kV isolation voltage (IEC 60601)
- <1% signal accuracy over temperature
- Common mode rejection >80dB @ 60Hz


### Implementation

Analog Devices AD7400A Sigma-Delta Isolator

- Specifications: 2.5kV isolation, 20-bit resolution
- Common mode transient immunity: 25kV/ $\mu$ s
- Power consumption: 15mW total
- Accuracy:  $\pm 0.05\%$  over -40°C to +125°C
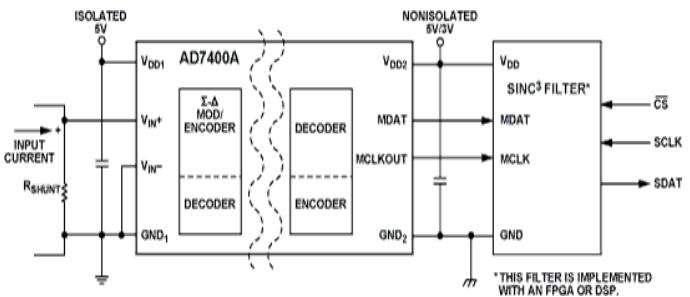
### Result

Noise-free measurement in harsh industrial environment



# Watchdog Protection

## Mitigation

Resets system during software lockup or hardware failure.

## Explanation

Embedded systems can hang due to software bugs, memory corruption, or electromagnetic interference. Watchdog circuits monitor system activity and force reset when problems occur.

## Components Used

- **External Watchdog ICs:** Independent monitoring circuits
- **Window Watchdogs:** Monitor timing windows, not just timeouts
- **Supervisory ICs:** Combine voltage, temperature, and watchdog functions

## Practical Example

Medical Device Controller

### Application

Insulin pump controller (safety-critical application)

### Watchdog IC

MAX6369 with 1.6s timeout

### Safety Requirements

- Independence of main processor
- Tamper-resistant design
- Fail-safe default state

### Result

System recovers from SW failures

