
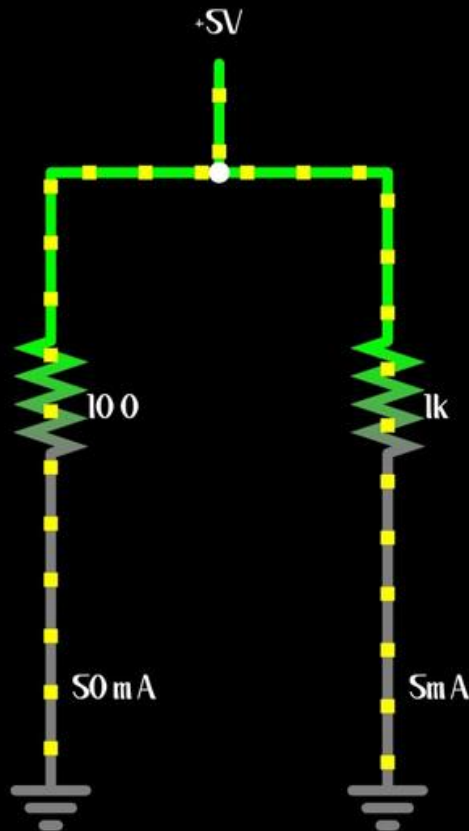


Basic Circuit

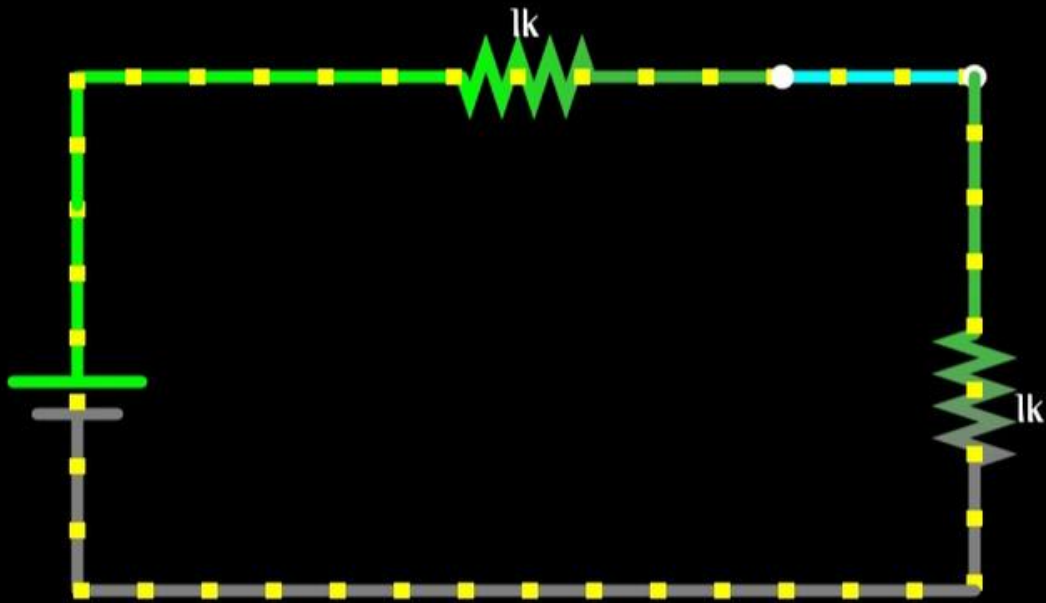


- ◆ This is a basic resistor circuit that demonstrates Ohm's Law.
- ◆ The circuit consists of a resistor connected series with a power source.
- ◆ The main goal is to calculate the current flowing through the resistor based on its resistance and the applied voltage, using Ohm's Law ($I = V/R$).

Voltage divider




- ◆ This is a voltage divider circuit that splits an input voltage into smaller, proportional output voltages.
- ◆ The circuit consists of two resistors connected in series across a power supply.
- ◆ The circuit demonstrates how to use the voltage divider formula ($V_{out} = V_{in} * R2 / (R1 + R2)$) to calculate the output voltage.

Current divider

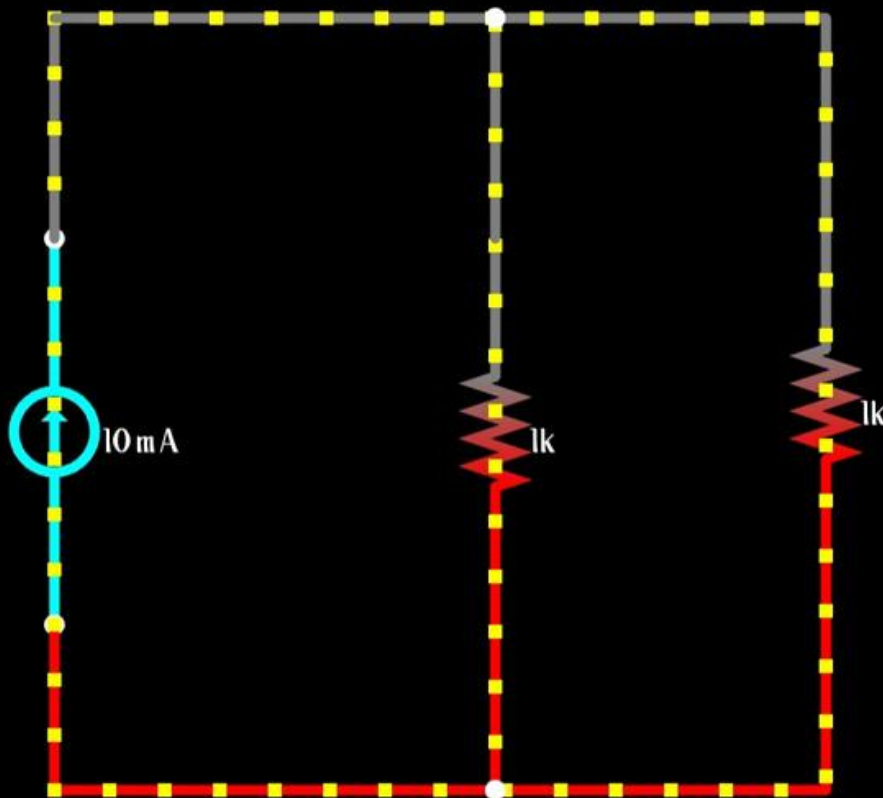


- ◆ This is a current divider circuit that splits the total current into smaller currents across multiple parallel branches.
- ◆ The circuit consists of two resistors connected in parallel to a power source.
- ◆ Based on the current divider rule ($I_1 = I_{\text{total}} * (R_2 / (R_1 + R_2))$ and $I_2 = I_{\text{total}} * (R_1 / (R_1 + R_2))$).

Series circuit

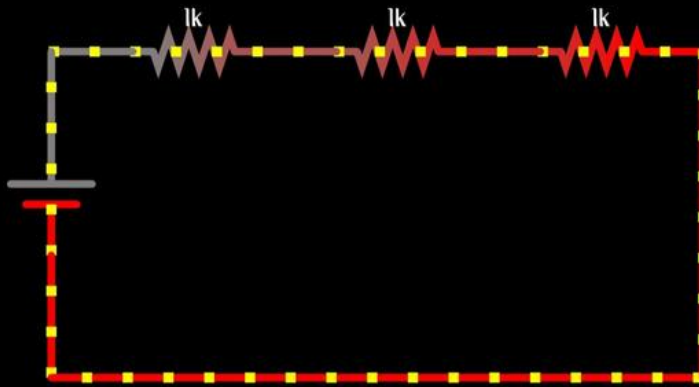


Parallel circuit

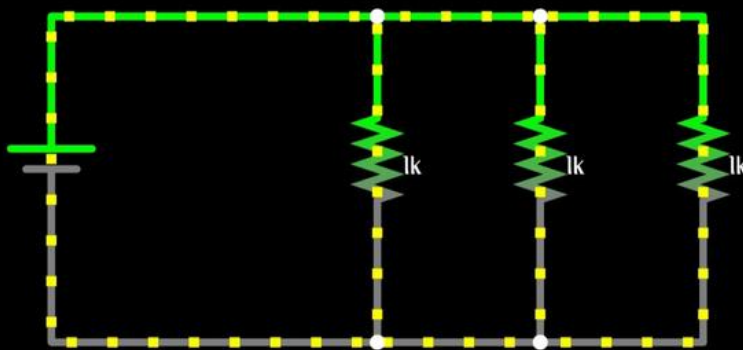


- ◆ This is a combination of series and parallel circuits designed to demonstrate the difference in behavior between the two configurations.
- ◆ In the series circuit, resistors are connected end-to-end.
- ◆ In the parallel circuit, resistors are connected across the same voltage source,

LED controlled circuit

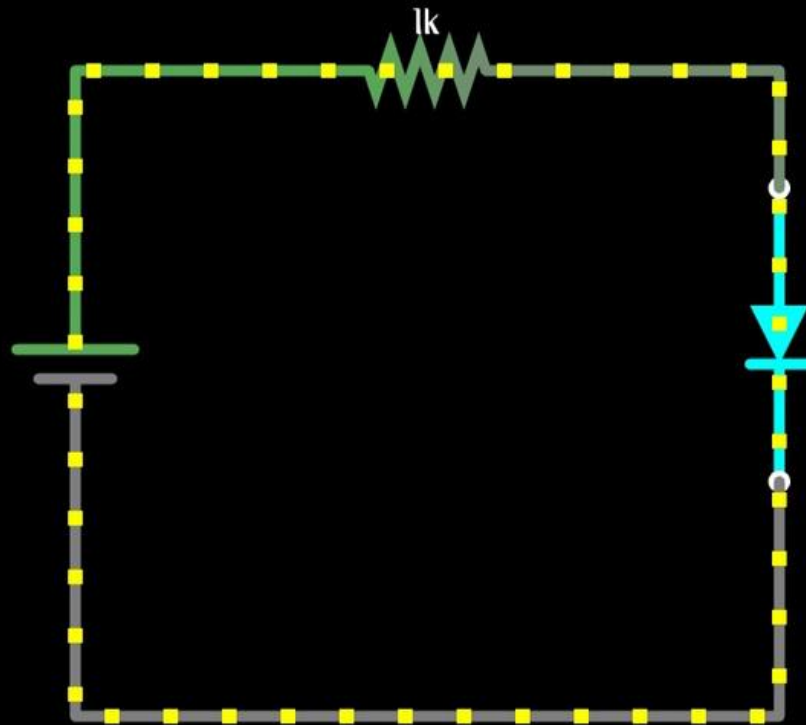

- ◆ This is a basic LED control circuit that regulates the current flow to light an LED based on a control switch.
- ◆ The circuit consists of an LED connected in series with a current-limiting resistor .
- ◆ This circuit demonstrates how to control the operation of an LED .



Switch controlled LED

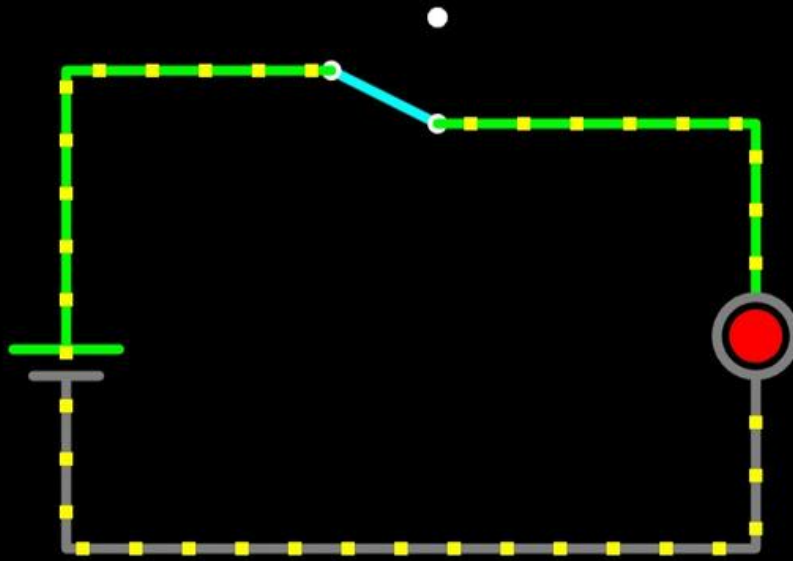

- ◆ This is a switch-controlled LED circuit that allows the user to turn an LED on and off by opening or closing a switch.
- ◆ When the switch is closed, current flows through the circuit, causing the LED to light up.
- ◆ When the switch is open, the circuit is incomplete, and the LED turns off.


Capacitor discharging

Capacitor charging

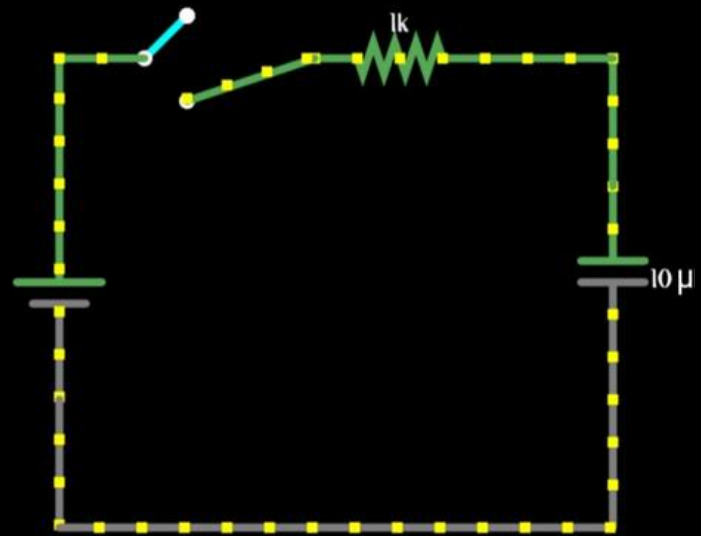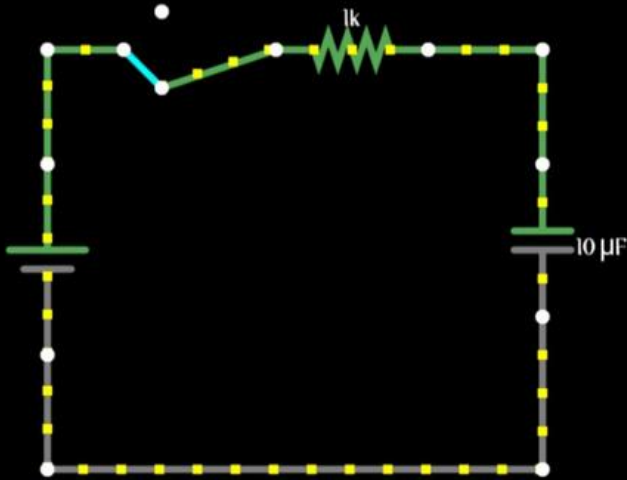


- ◆ This circuit demonstrates the charging and discharging behavior of a capacitor in an RC (resistor-capacitor) circuit.
- ◆ During the charging phase, when the power supply is connected, the capacitor gradually accumulates charge, and its voltage increases.
- ◆ During the discharging phase, when the power supply is disconnected, the capacitor releases its stored charge through the resistor, and its voltage decreases.

RC time constant circuit

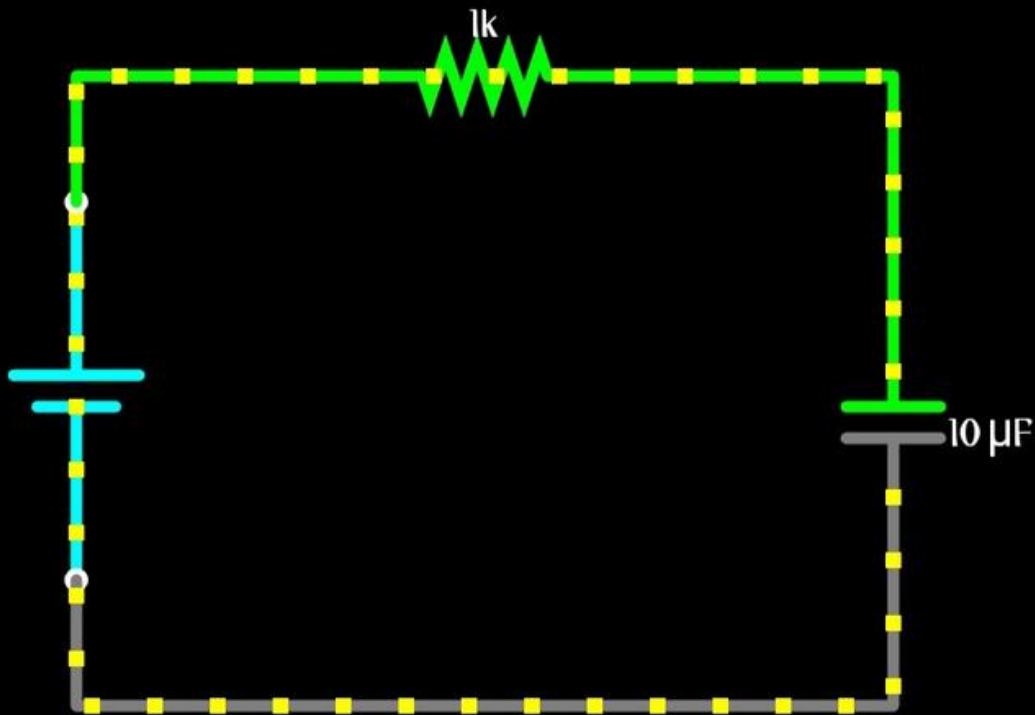


- ◆ This circuit demonstrates the RC time constant, which defines the rate at which a capacitor charges and discharges in an RC circuit.
- ◆ The circuit consists of a resistor, a capacitor, and a power supply.
- ◆ The time constant (τ) is given by the formula
$$\tau = R * C,$$

Battery tester circuit

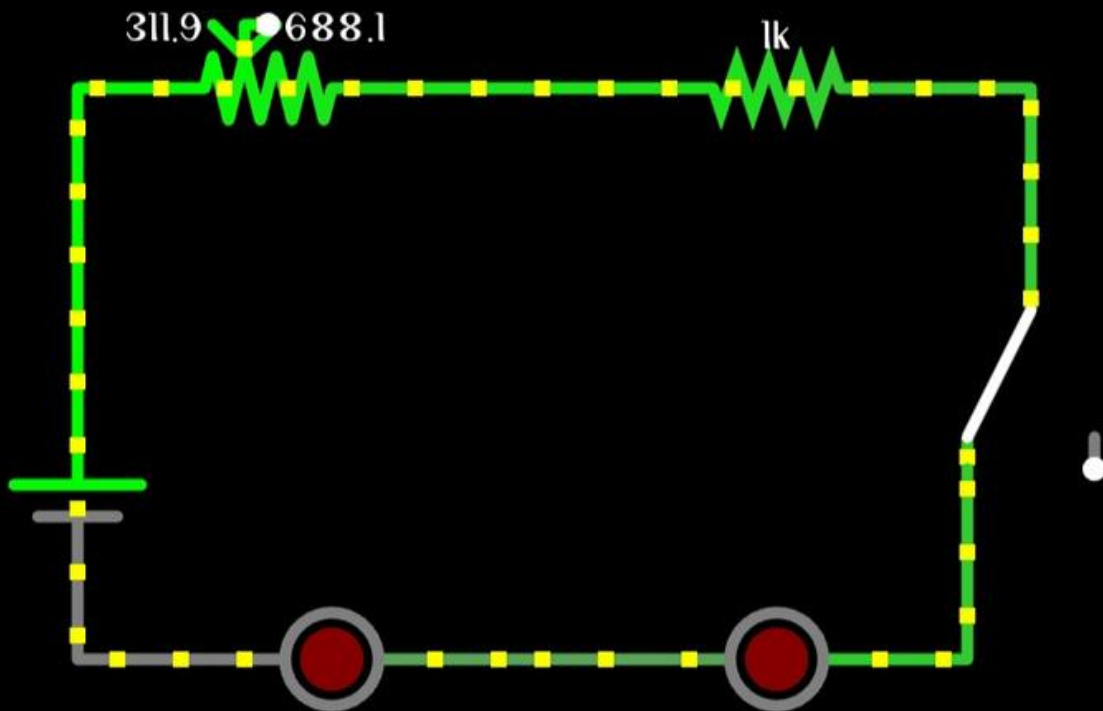


- ◆ This is a simple battery tester circuit designed to measure the voltage of a battery and indicate its charge level.
- ◆ The resistor is used to limit the current and prevent damage to the components.
- ◆ If the voltage is above a certain threshold, the LED lights up

Voltage follower circuit

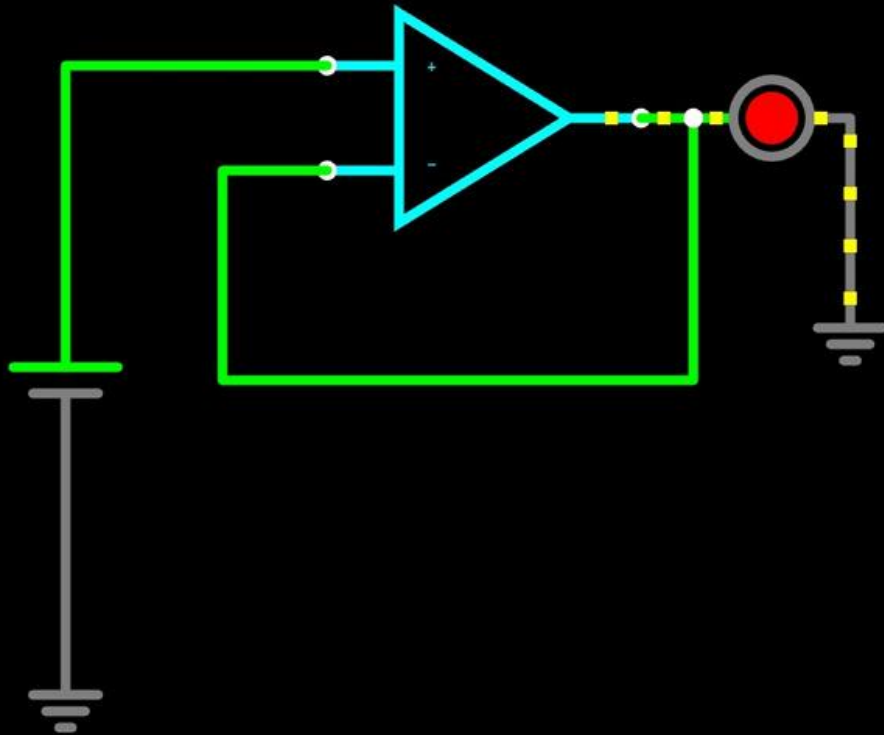


- ◆ This is a voltage follower (also known as a buffer amplifier) circuit that provides unity gain while isolating the input and output stages.
- ◆ The circuit typically consists of an operational amplifier (op-amp) .
- ◆ The primary function of the voltage follower is to ensure that the voltage at the output is the same as the input voltage ($V_{out} = V_{in}$)

Inverting amplifier

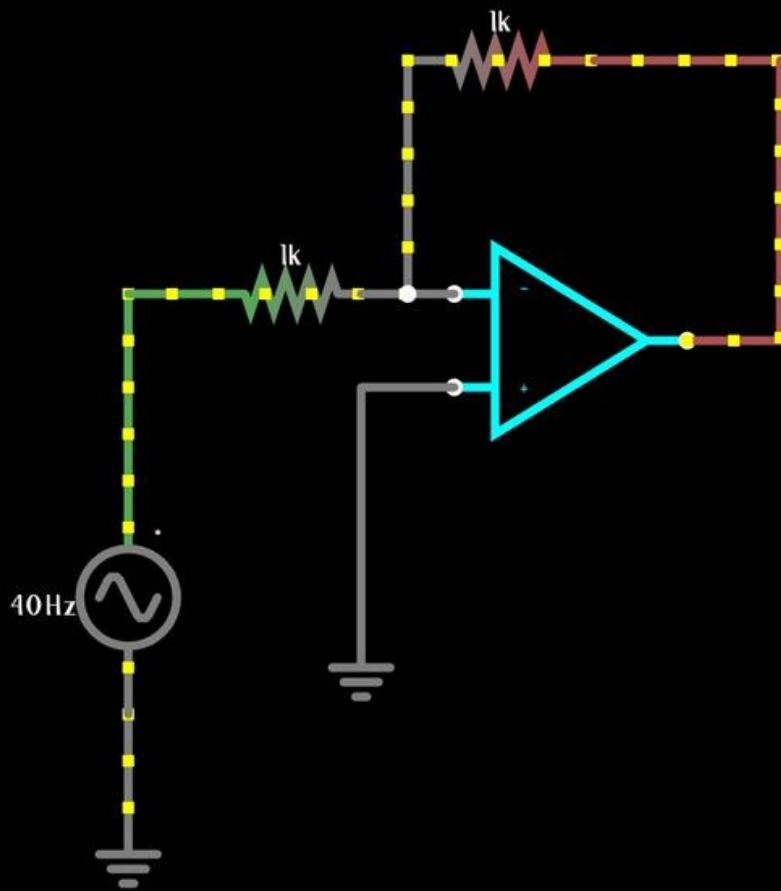


- ◆ This is an inverting amplifier circuit that uses an operational amplifier (op-amp) to invert and amplify an input signal.
- ◆ The circuit consists of an op-amp, a resistor connected to the input signal, and a feedback resistor connected between the output and the inverting input of the op-amp.
- ◆ This circuit is commonly used in applications where signal inversion is required, such as audio processing, signal conditioning, and waveform generation.

Non-inverting amplifier

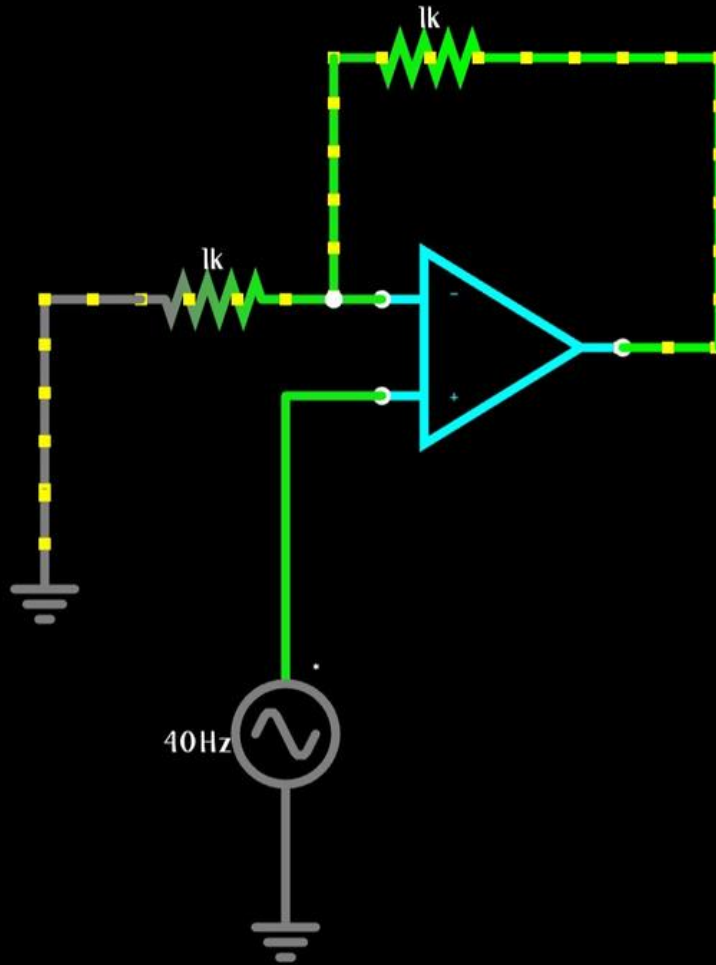


- ◆ This is a non-inverting amplifier circuit that uses an operational amplifier (op-amp) to amplify an input signal without inverting its phase.
- ◆ The input signal is applied to the non-inverting input of the op-amp.
- ◆ This circuit is widely used in applications requiring signal amplification with preserved polarity, such as audio amplification, sensor signal conditioning.

Summing amplifier

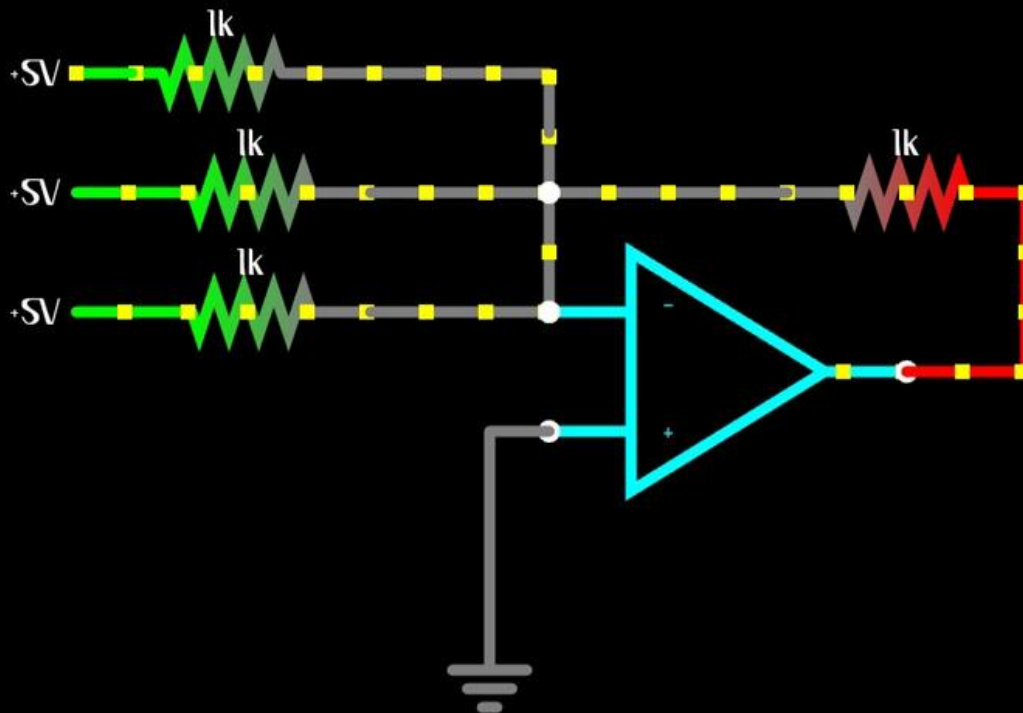


- ◆ This is a summing amplifier circuit that combines multiple input signals into a single output signal, which is the weighted sum of the inputs.
- ◆ The circuit typically consists of an operational amplifier (op-amp), multiple input resistors, and a feedback resistor.
- ◆ This circuit is used in applications such as audio mixing, signal processing, and analog computing,

Differential amplifier

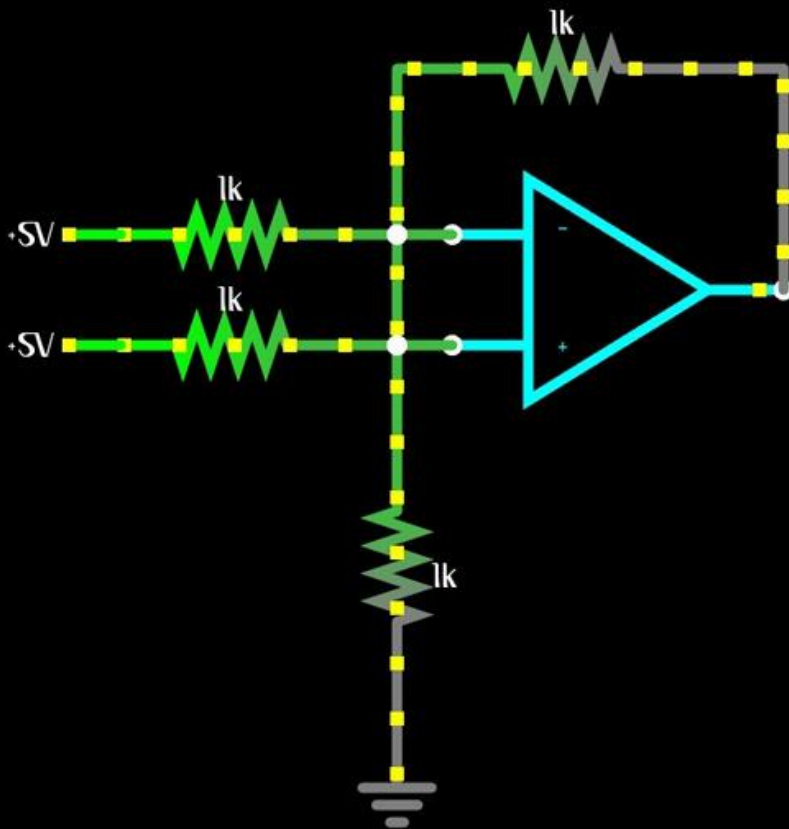


- ◆ This is a differential amplifier circuit that amplifies the difference between two input signals while rejecting any common-mode signals (signals that are common to both inputs).
- ◆ The differential amplifier outputs a voltage proportional to the difference between the two input voltages.
- ◆ This circuit is crucial for applications requiring precise measurement of voltage differences, such as in instrumentation, sensor interfacing.

comparator circuit

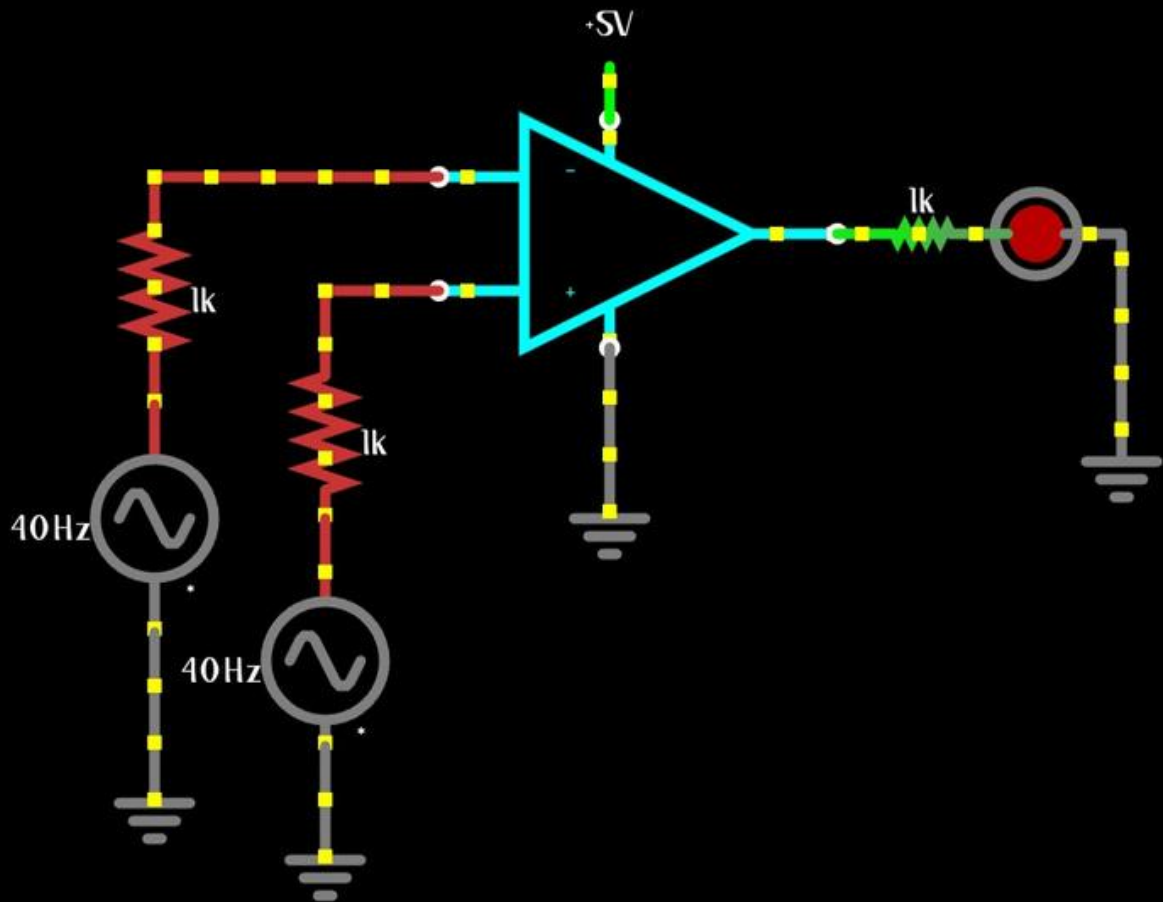


- ◆ This comparator circuit compares two input voltages and outputs a high or low voltage depending on which input is greater.
- ◆ It uses an operational amplifier to generate a digital output that indicates which input voltage is higher.
- ◆ Making it useful in applications like voltage level detection, zero-crossing detection, and pulse-width modulation.

Schmitt trigger

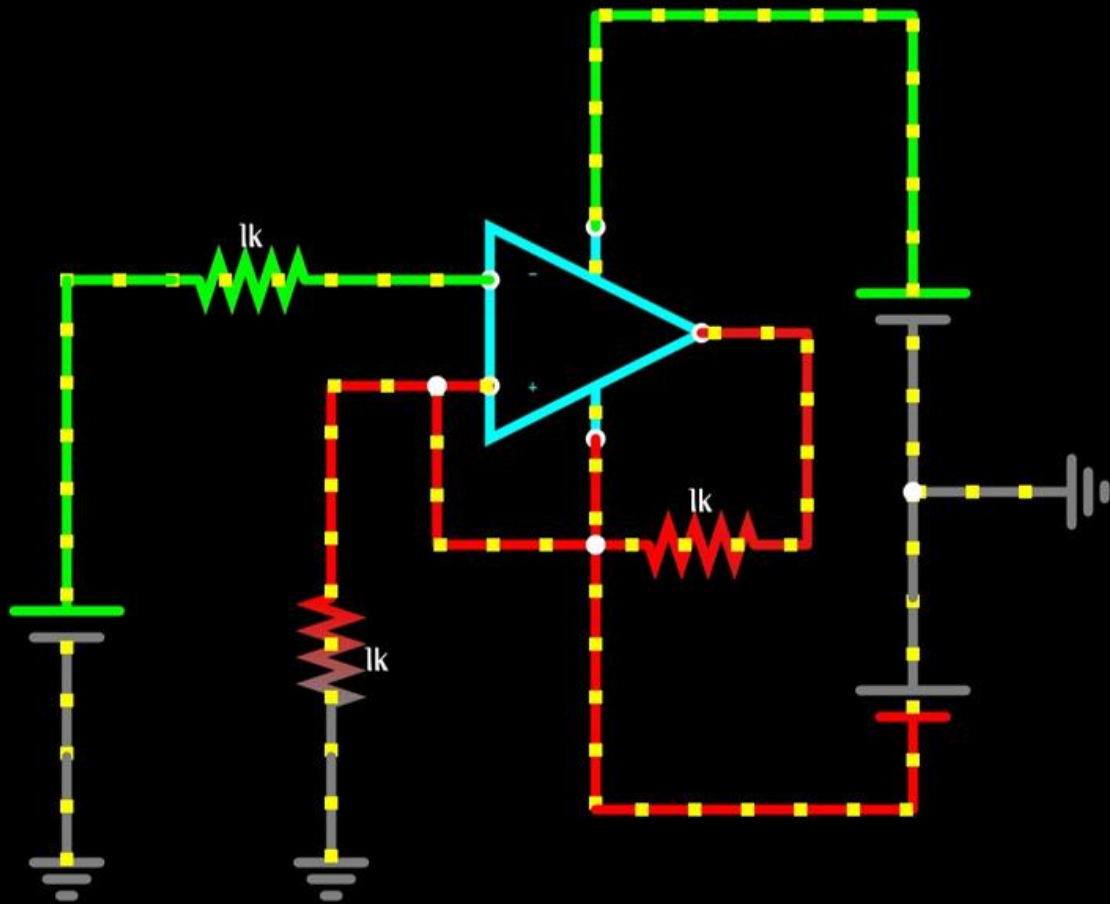


- ◆ The Schmitt trigger converts noisy or slow-varying signals into clean digital outputs by introducing hysteresis.
- ◆ It uses positive feedback to set distinct upper and lower threshold voltages, ensuring stable transitions.
- ◆ This circuit is commonly used in signal conditioning, noise filtering, and waveform shaping.

Voltage clipper circuit

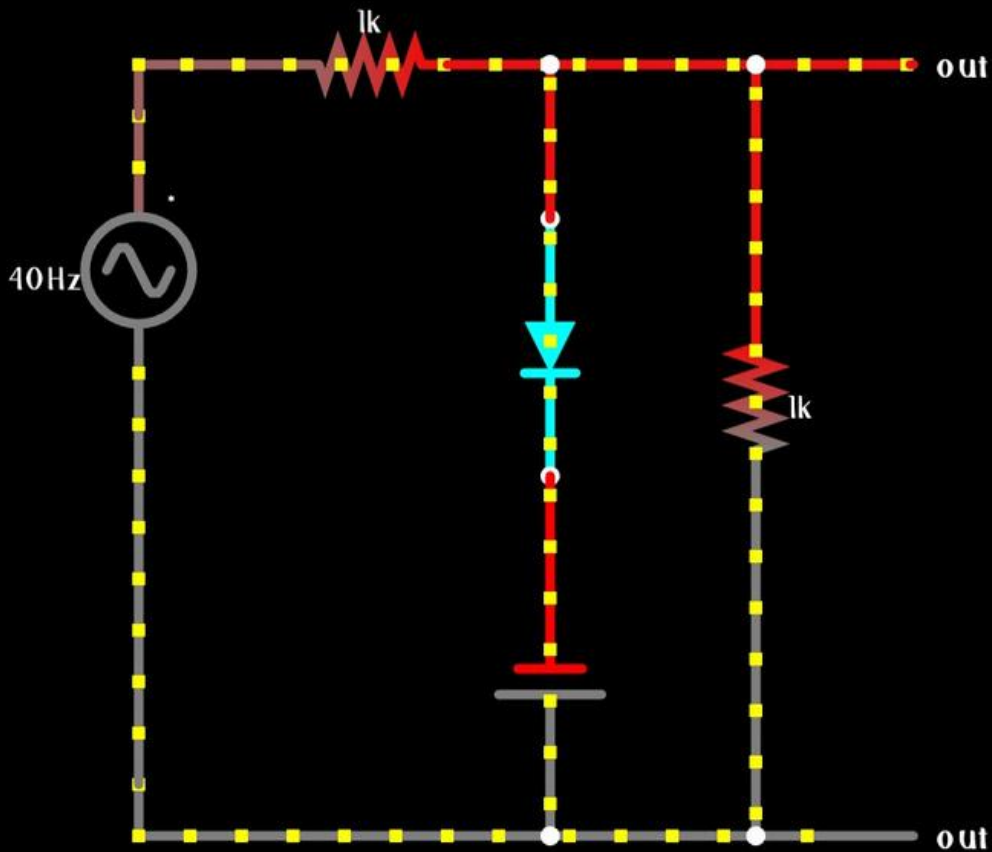


- ◆ Limits the voltage in a circuit by "clipping" any voltage that exceeds a predefined threshold.
- ◆ Uses diodes to conduct and protect the circuit when the input voltage surpasses the set limit.
- ◆ Commonly used in signal protection, waveform shaping, and preventing overvoltage damage in electronic circuits.

Positive clamper with negative bias

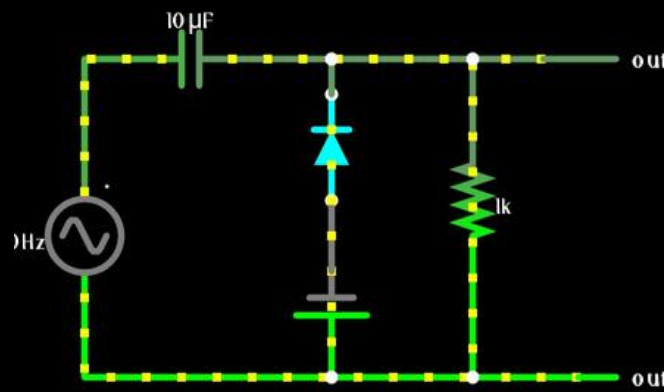


Negative clamper with positive bias

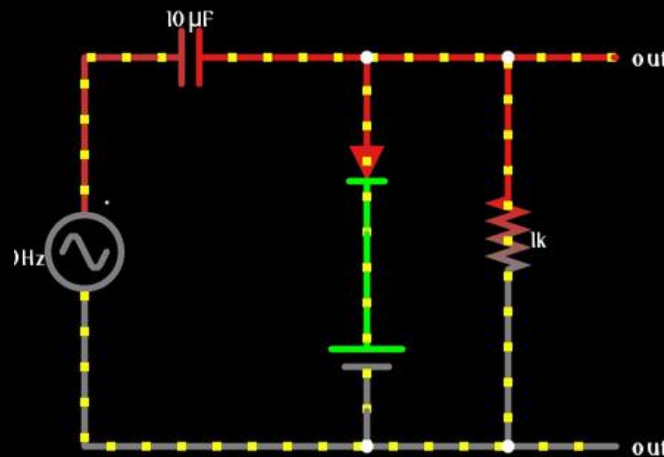

◆ Positive Clamper: Shifts the entire input signal upward by adding a DC voltage, ensuring the signal stays above a certain reference level. Typically uses a diode and capacitor.


◆ Negative Clamper: Shifts the input signal downward by subtracting a DC voltage, ensuring the signal stays below a certain reference level. It also uses a diode and capacitor.

Peak detector circuit

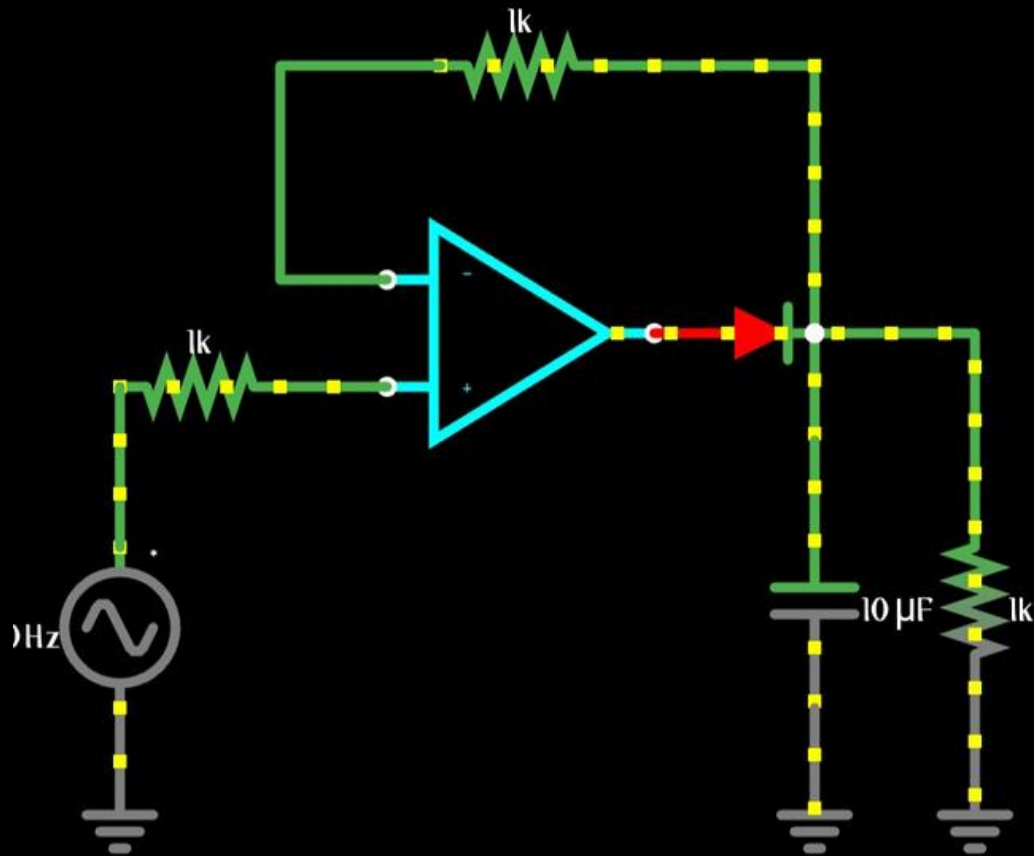


- ◆ Detects and holds the peak (maximum) value of an input signal, maintaining this value for a certain period.
- ◆ Uses a diode, capacitor, and resistor to capture the peak voltage and prevent the signal from dropping below that level.
- ◆ Commonly used in signal processing, audio peak detection.

Half wave rectifier

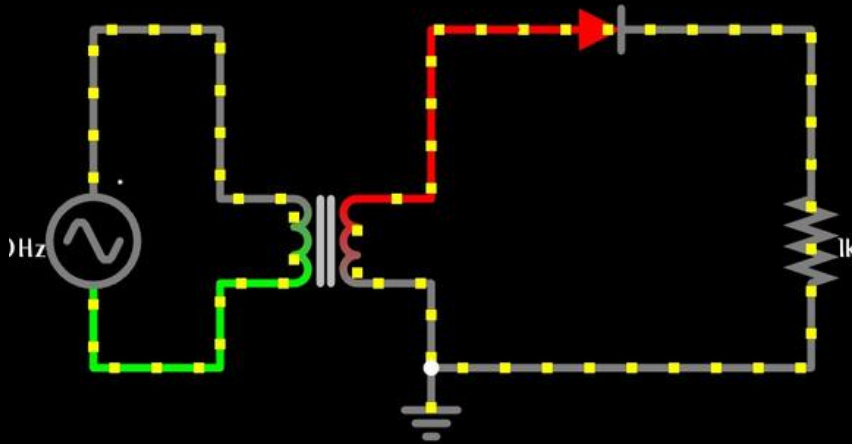


Full wave rectifier

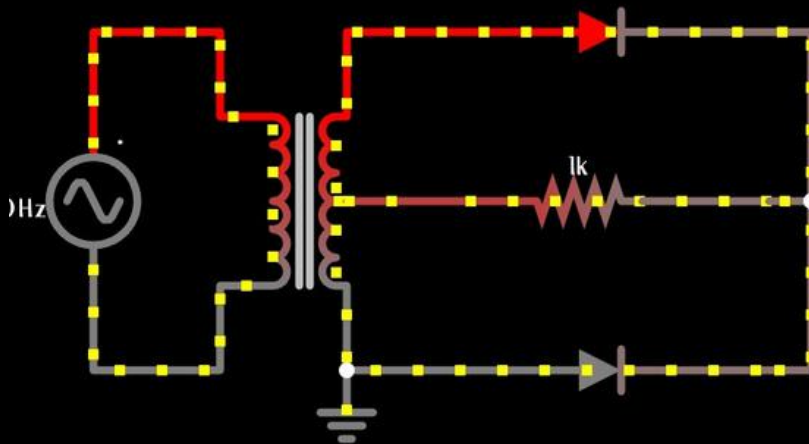

◆ Half-Wave Rectifier: Converts only one half (positive or negative) of an AC signal into DC by allowing current to flow through the load during one half-cycle, using a single diode.


◆ Full-Wave Rectifier: Converts both halves of an AC signal into DC by using two or four diodes in a bridge configuration, providing smoother output with a higher average DC voltage.

Low pass RC filter

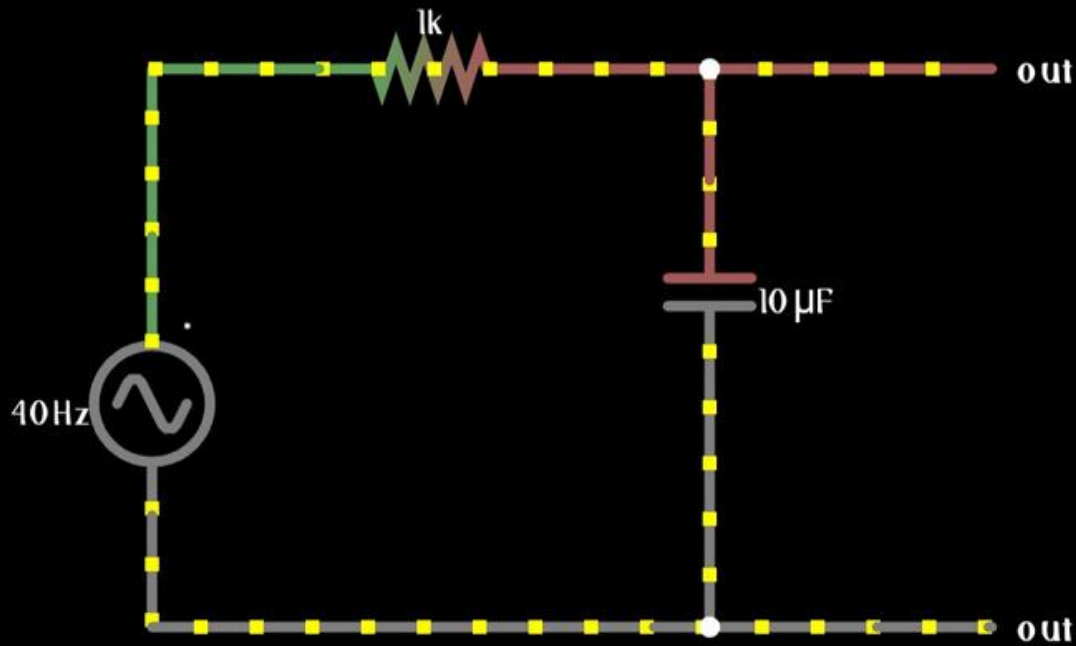


- ◆ Allows low-frequency signals to pass through while attenuating high-frequency signals.
- ◆ Typically consists of a resistor and capacitor (RC filter) or an inductor and capacitor (LC filter), with the cutoff frequency .
- ◆ Used in audio systems, signal processing, and noise reduction to remove high-frequency noise or smooth out signals.

High pass RC filter

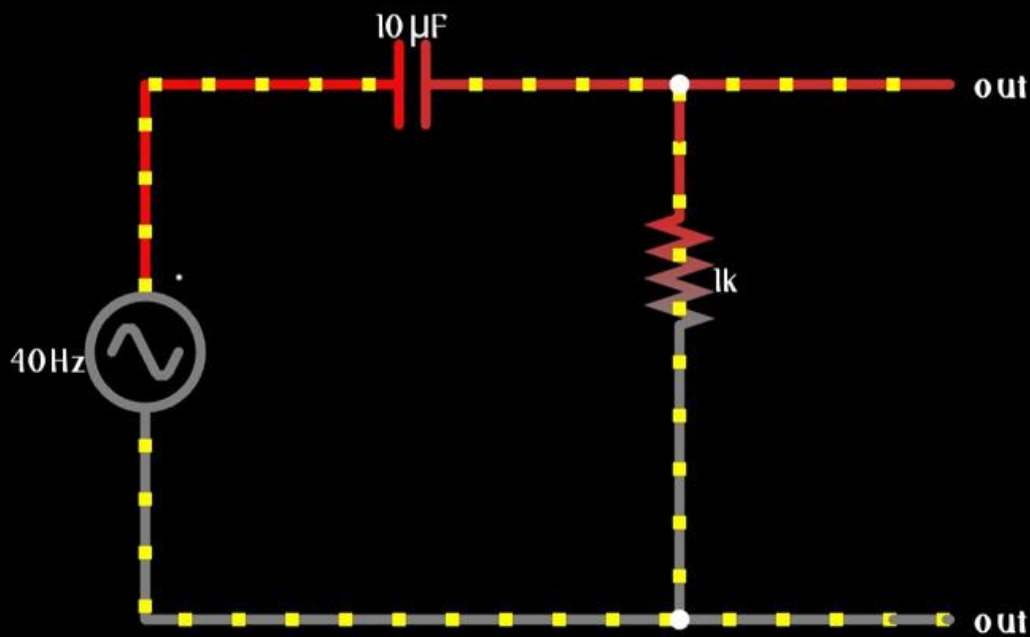


- ◆ Allows high-frequency signals to pass through while attenuating low-frequency signals.
- ◆ Typically uses a resistor and capacitor (RC filter) or an inductor and capacitor (LC filter), with the cutoff frequency .
- ◆ Used in audio processing, signal conditioning, and noise filtering to eliminate low-frequency noise or unwanted components from a signal.

Band pass filter

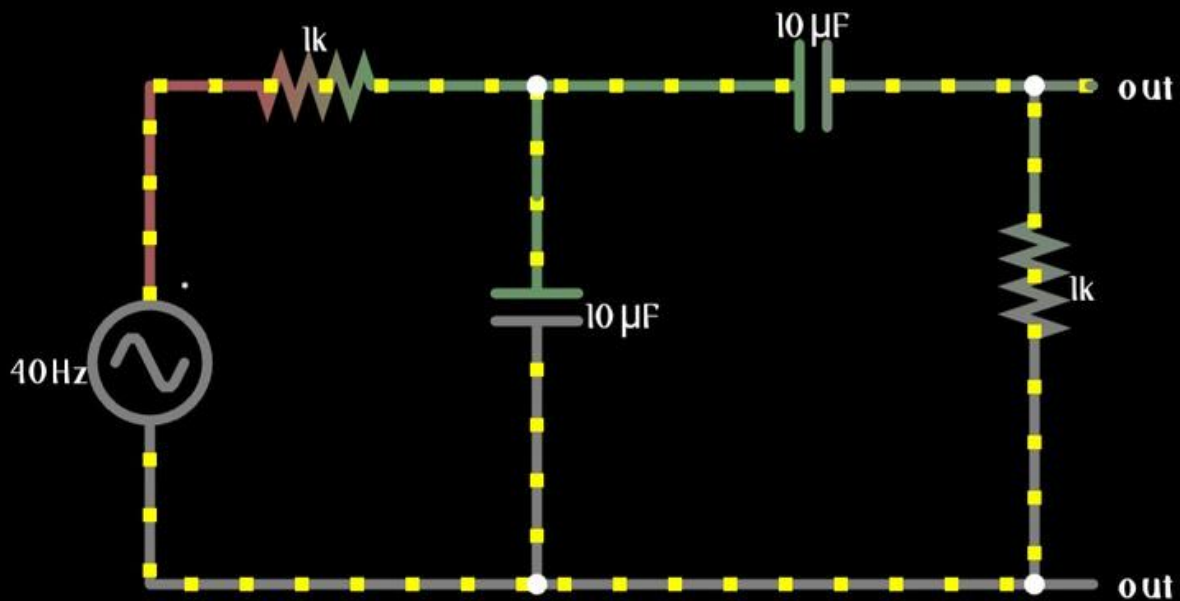


- ◆ Allows signals within a specific frequency range to pass through while attenuating frequencies outside this range.
- ◆ Combines a low-pass filter and a high-pass filter to define the lower and upper cutoff frequencies, creating a band of allowed frequencies.
- ◆ Used in wireless communication, audio processing, and instrumentation to isolate desired frequency bands from a signal.

Band stop filter

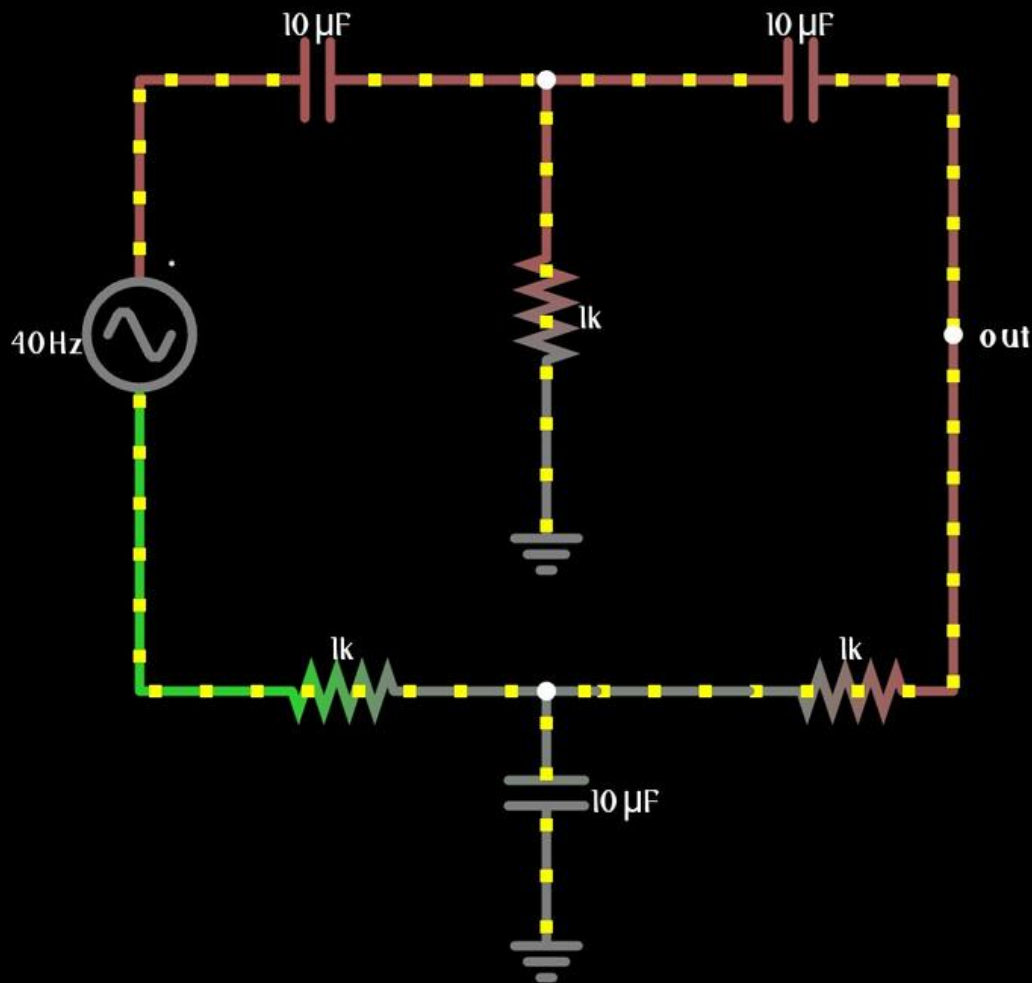


- ◆ Attenuates signals within a specific frequency range while allowing frequencies outside this range to pass through.
- ◆ Combines a low-pass filter and a high-pass filter in parallel, creating a "notch" where the undesired frequencies are blocked.
- ◆ Used in communication systems, audio processing, and power systems to eliminate interference.

Active low pass filter

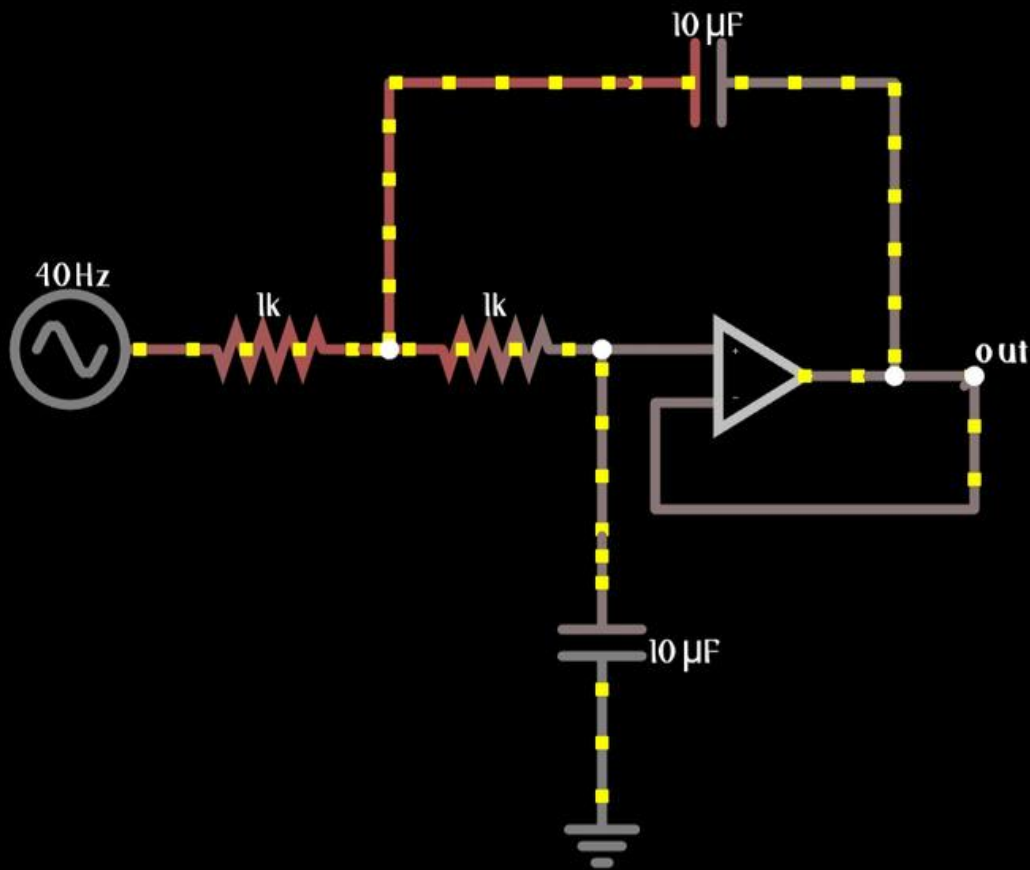


- ◆ Passes low-frequency signals while attenuating high-frequency signals, with added amplification.
- ◆ Uses an operational amplifier (op-amp) along with resistors and capacitors to improve gain and performance compared to passive filters.
- ◆ Commonly used in audio systems, signal processing, and communication systems for noise reduction and smoothing signals.

Active high pass filter

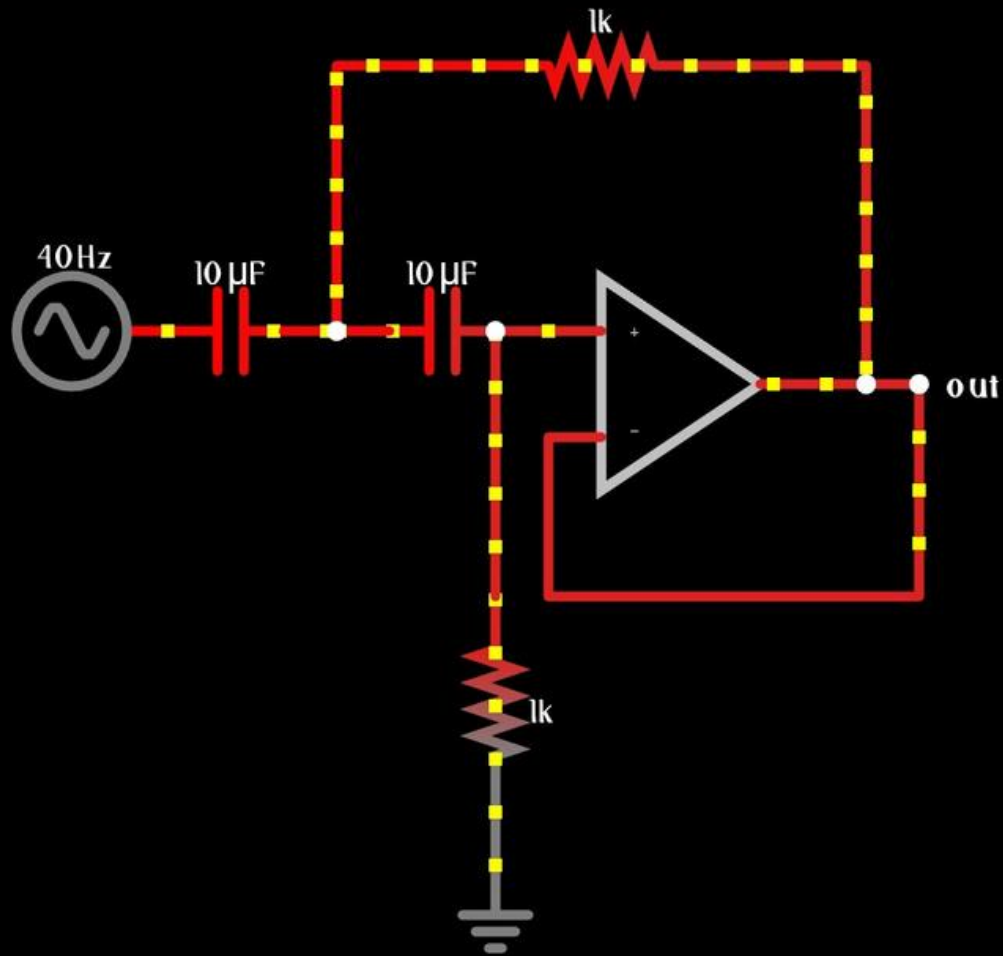


- ◆ Passes high-frequency signals while attenuating low-frequency signals, with added amplification.
- ◆ Utilizes an operational amplifier (op-amp) with resistors and capacitors to improve gain and performance over passive filters.
- ◆ Used in audio processing, communication systems, and signal conditioning to remove low-frequency noise or interference.

LC filter

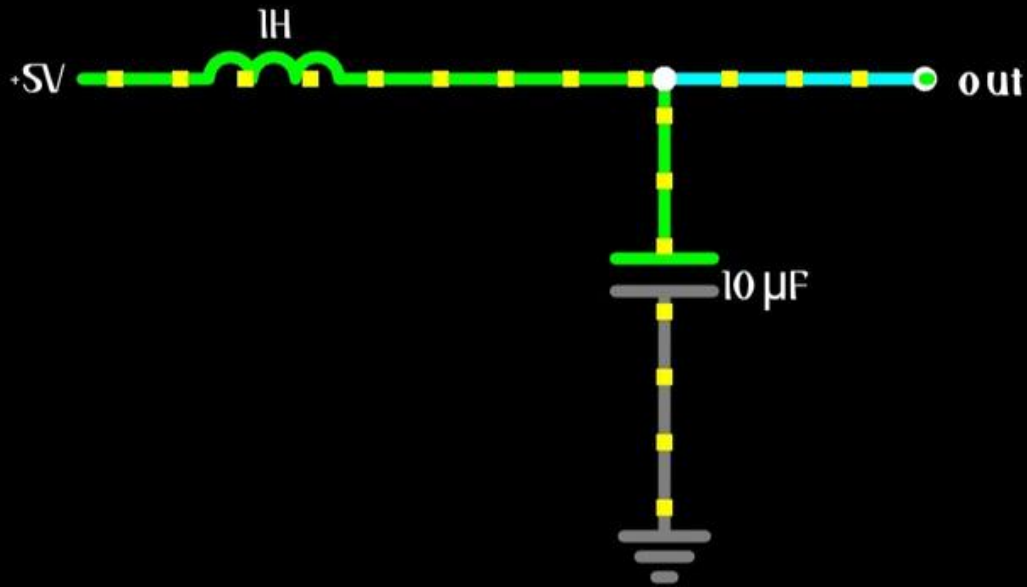


- ◆ Filters signals by allowing specific frequencies to pass while attenuating others, using inductors (L) and capacitors (C).
- ◆ The inductor and capacitor work together to create low-pass, high-pass, bandpass, or band-stop filter characteristics, depending on the configuration.
- ◆ Commonly used in power supplies, radio frequency (RF) circuits, and audio systems .

RLC band pass filter

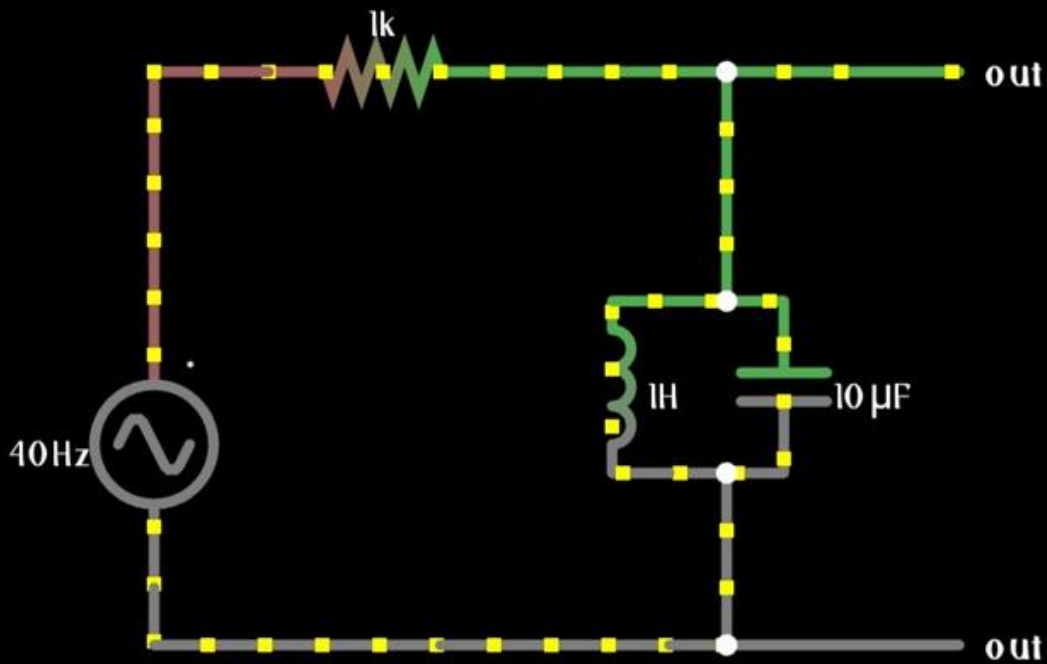


- ◆ Allows signals within a specific frequency range to pass through while attenuating frequencies outside this range.
- ◆ Combines a resistor (R), inductor (L), and capacitor (C) in series or parallel, with the resonant frequency determined by the values of L and C.
- ◆ Used in communication systems, audio processing, and RF circuits to isolate or amplify desired frequency bands.

Twin-t notch filter

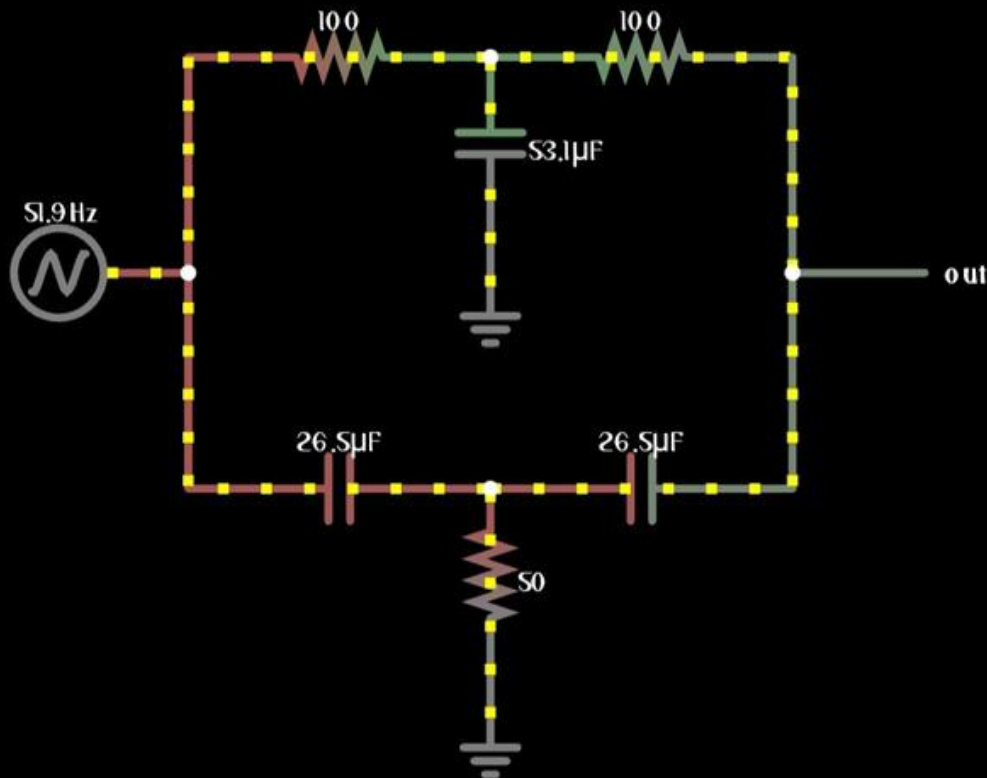


- ◆ Attenuates a specific frequency (notch frequency) while allowing other frequencies to pass, creating a sharp "notch" in the frequency response.
- ◆ Uses two T-shaped resistor-capacitor (RC) networks arranged in parallel, one for high-pass and the other for low-pass, to effectively cancel signals at the notch frequency.
- ◆ Commonly used in audio systems, instrumentation, and communication systems .

State variable filter

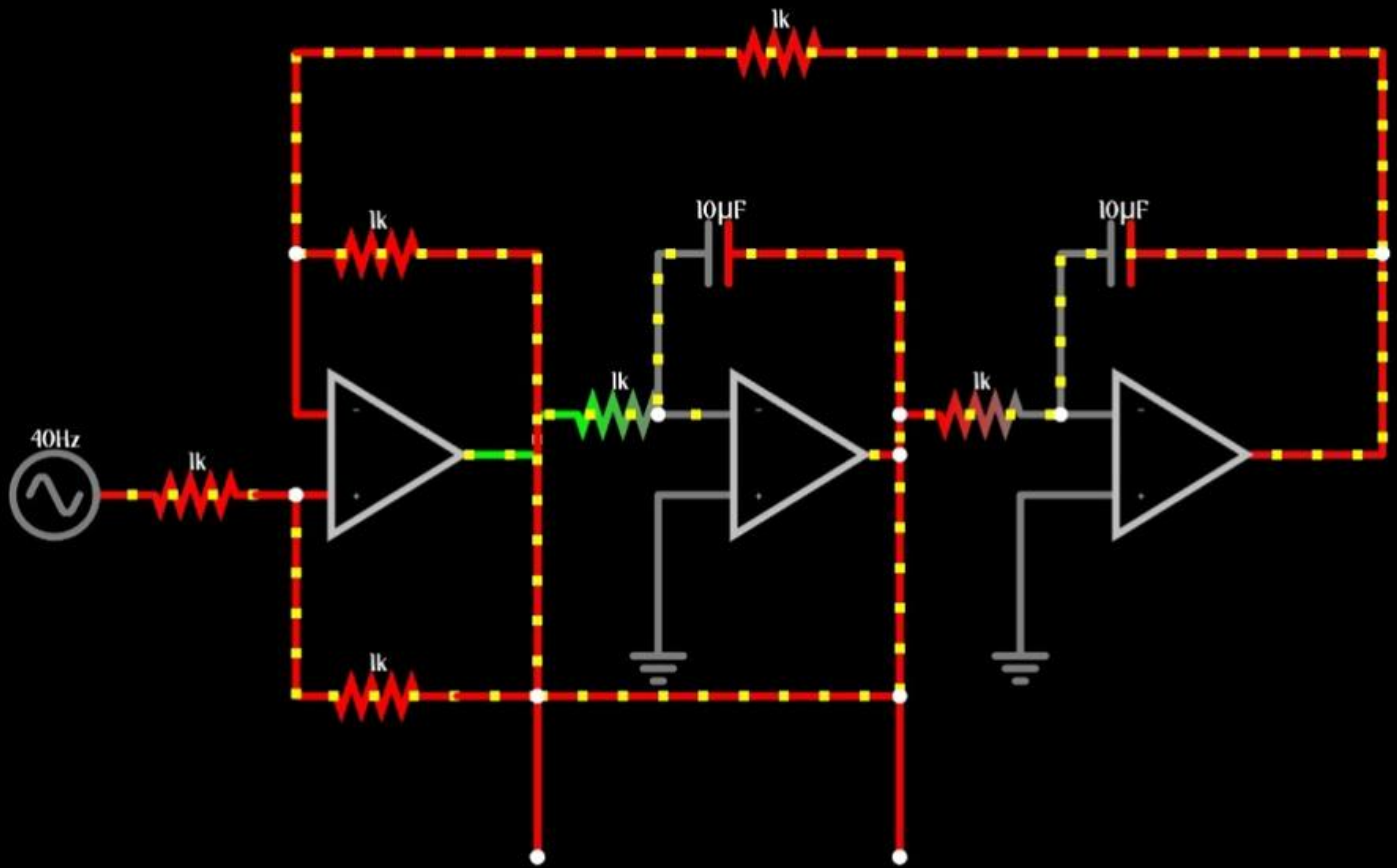


- ◆ Provides simultaneous low-pass, high-pass, and band-pass outputs, allowing versatile filtering of input signals.
- ◆ Utilizes multiple operational amplifiers (op-amps) in a feedback configuration with resistors and capacitors to define the filter characteristics and cutoff frequencies.
- ◆ Commonly used in audio processing, signal analysis, and communication systems .

Simple RC oscillator

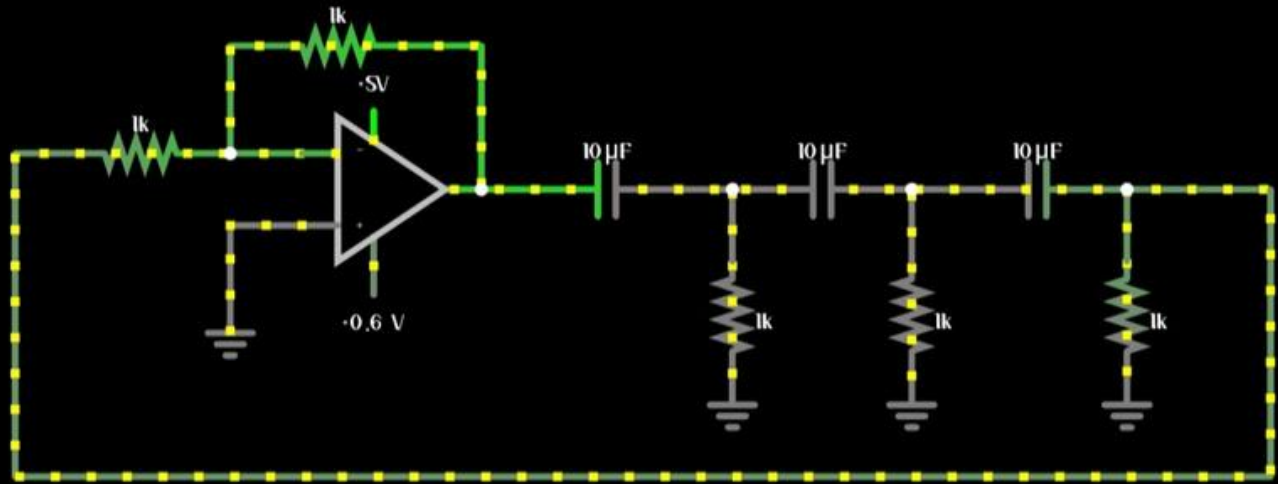


- ◆ Generates a sinusoidal waveform at a specific frequency using resistors and capacitors (RC network).
- ◆ Uses an RC network for frequency determination and an amplifier (like an op-amp or transistor) to sustain oscillations based on positive feedback.
- ◆ Used in audio signal generation, function generators, and as clock signals in low-frequency applications.

LC oscillator

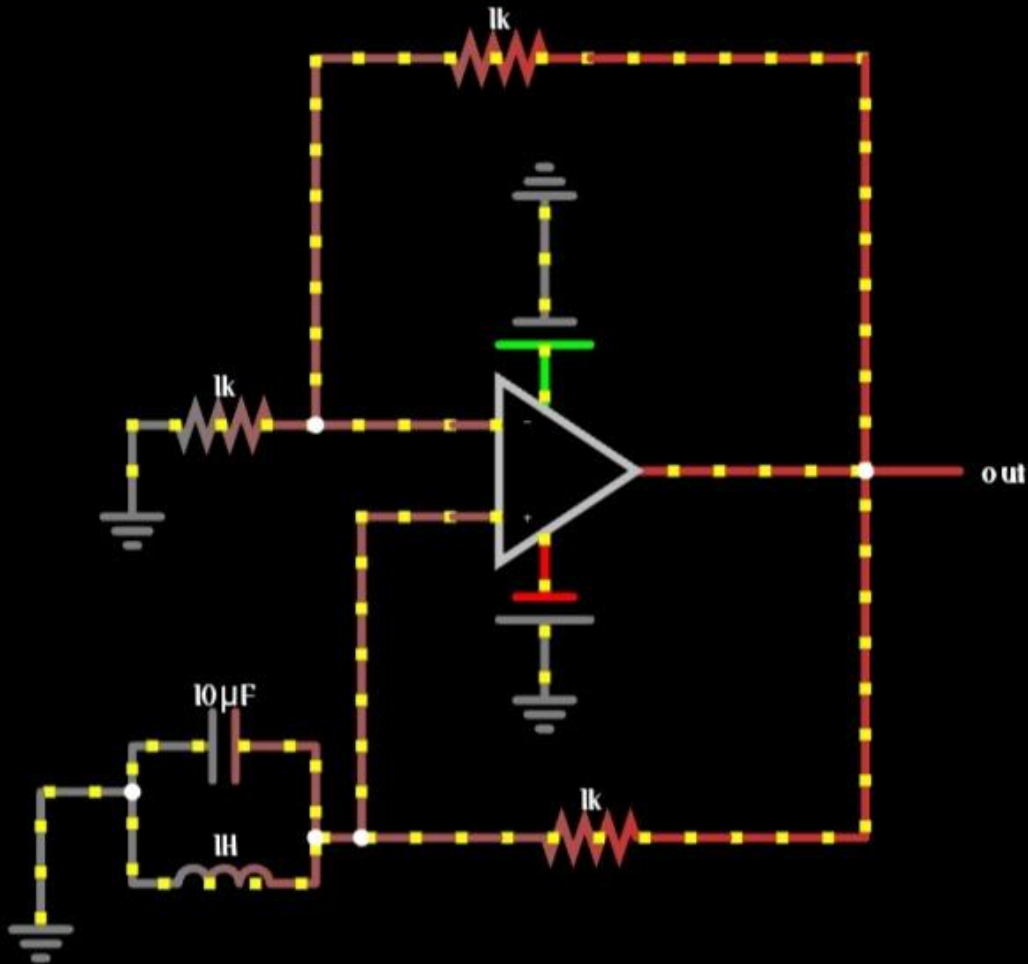


- ◆ Generates sinusoidal waveforms at high frequencies using an inductor (L) and capacitor (C) as the frequency-determining components.
- ◆ The LC circuit forms a resonant tank that oscillates at a specific frequency, sustained by positive feedback from an amplifier.
- ◆ Commonly used in radio transmitters, receivers, and signal generation for communication systems and RF circuits.

Hartley Oscillator

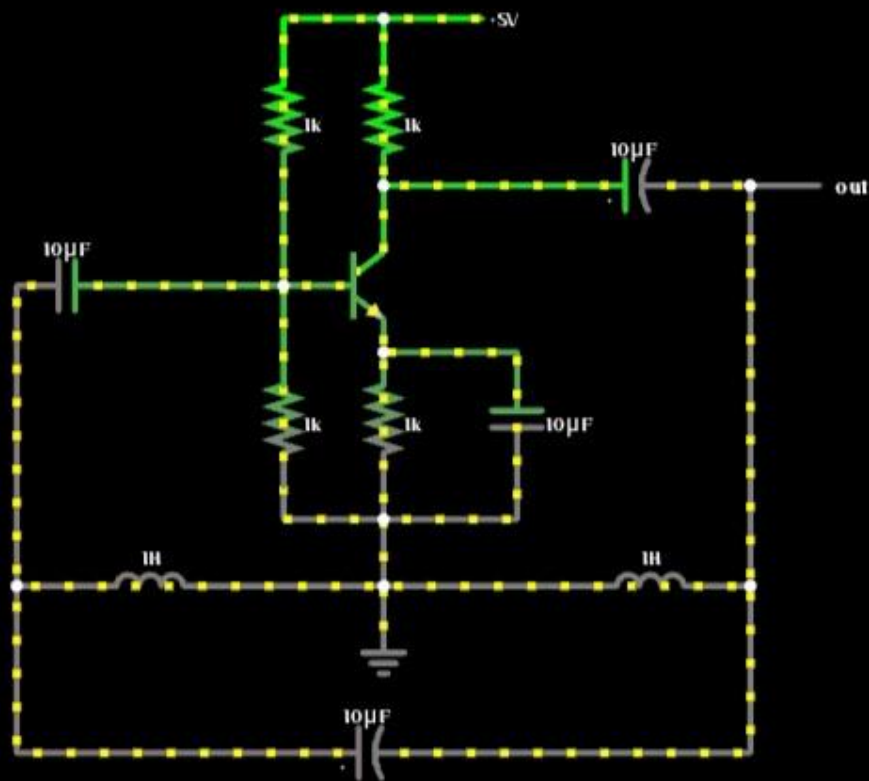


- ◆ Generates sinusoidal waveforms, typically in the radio frequency (RF) range, using an LC circuit with a tapped inductor.
- ◆ determine the oscillation frequency, with positive feedback provided by the tapped inductor to sustain oscillations.
- ◆ Widely used in RF oscillators, signal generators, and communication systems.

Colpitts oscillator

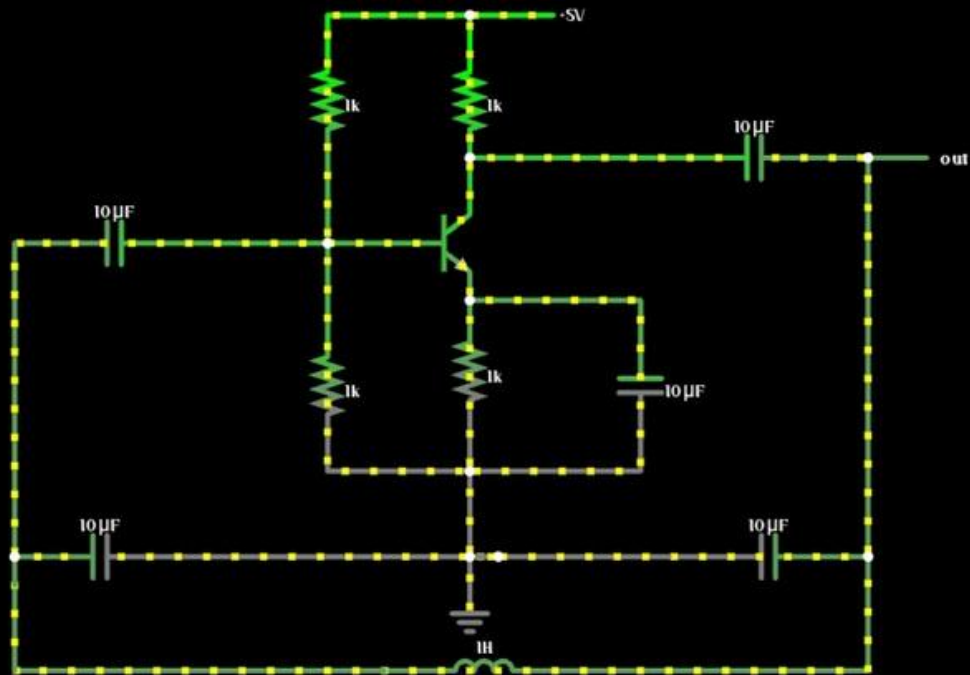


- ◆ Generates sinusoidal waveforms at high frequencies typically used in RF and communication systems.
 - ◆ Uses an LC tank circuit with a capacitive voltage divider to determine the oscillation frequency, with positive feedback provided by the divider.
 - ◆ Commonly used in RF signal generation, local oscillators in transmitters, and frequency synthesizers due to its stability and simplicity.

Wien-bridge oscillator

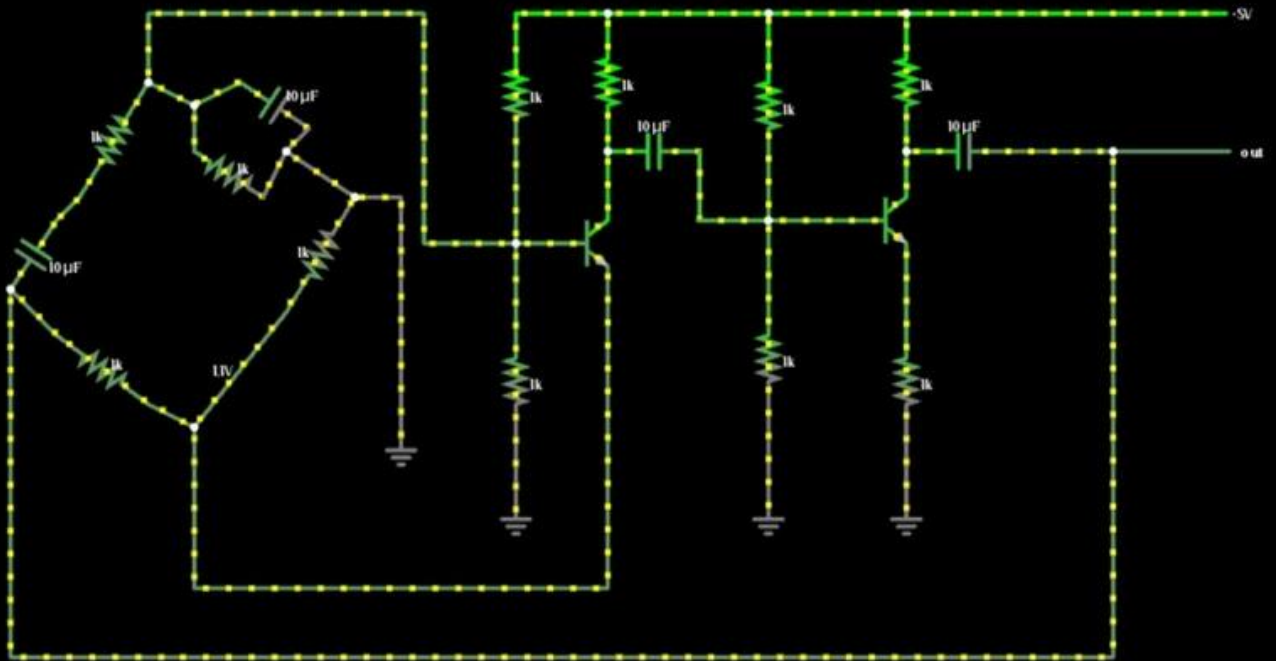


- ◆ Generates low-frequency sinusoidal waveforms with excellent frequency stability.
- ◆ Uses an RC network (Wien Bridge) for frequency selection and an amplifier (usually an op-amp) with positive feedback to sustain oscillations.
- ◆ Commonly used in audio signal generation, testing equipment, and function generators due to its simplicity.

Crystal oscillator

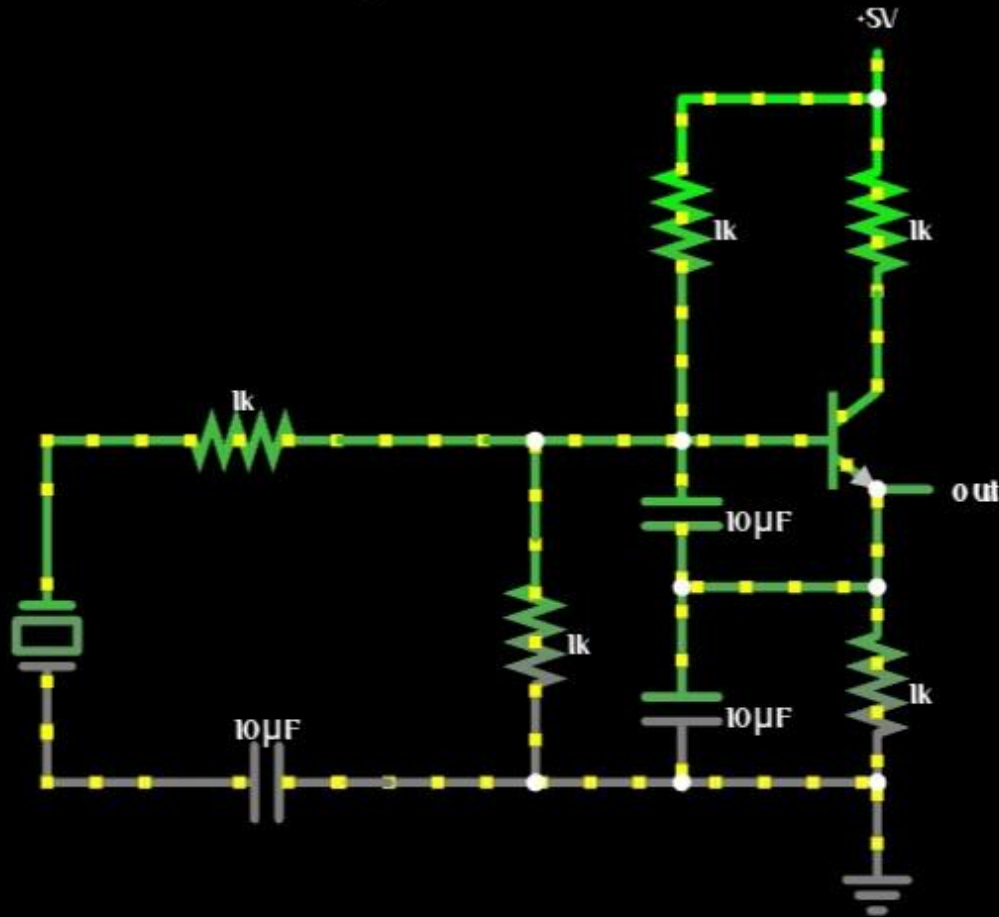


- ◆ Generates highly stable sinusoidal waveforms with precise frequency control using a quartz crystal.
- ◆ Utilizes the piezoelectric properties of the quartz crystal to create oscillations at a fixed natural frequency, sustained by an amplifier circuit.
- ◆ Widely used in clocks, microcontrollers, communication systems.

555 Timer astable oscillator

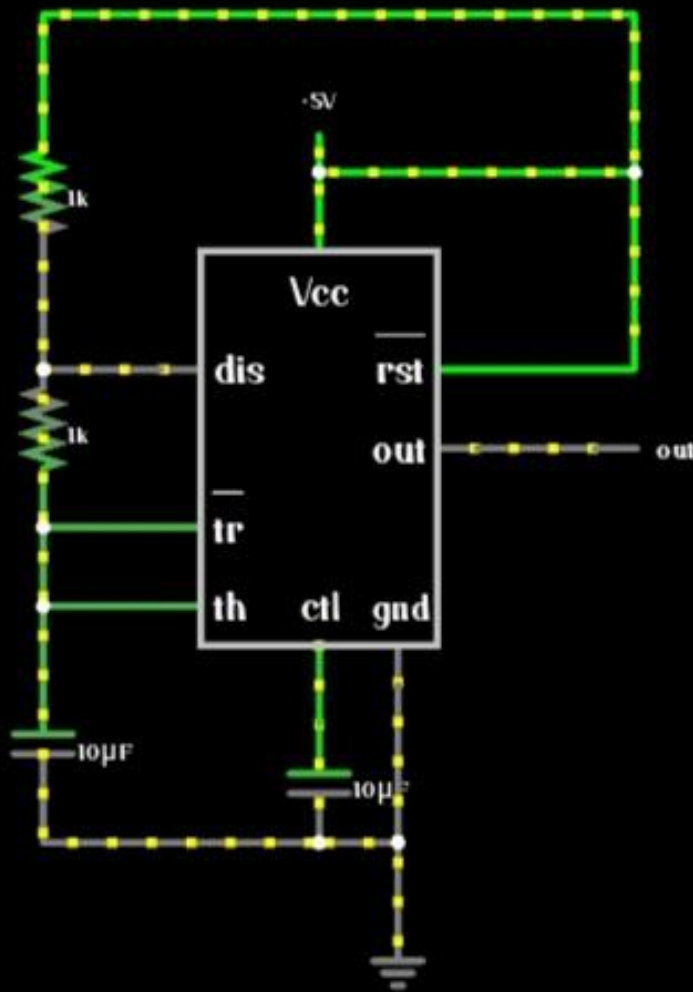


- ◆ Generates a continuous square wave output without requiring an external trigger.
- ◆ Configures the 555 timer in astable mode using resistors and a capacitor to set the frequency and duty cycle of the oscillation.
- ◆ Commonly used in pulse generation, clock signals, LED and motor control, and other timing-related circuits.

555 Timer monostable oscillator

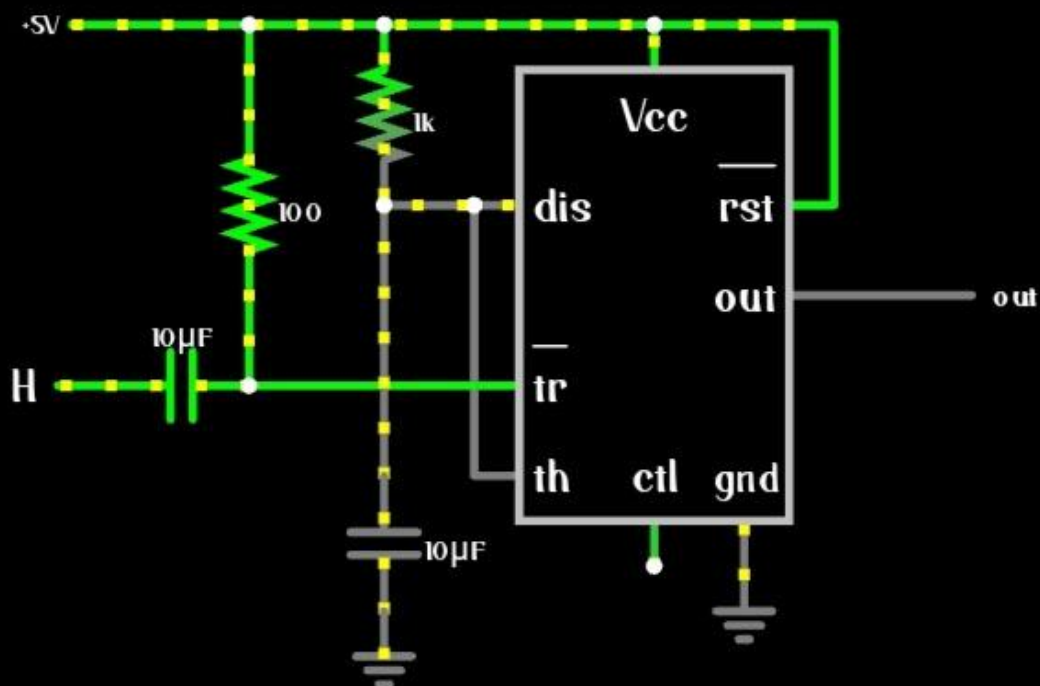


- ◆ Generates a single pulse of a fixed duration in response to an external trigger.
- ◆ Configures the 555 timer in monostable mode, where the pulse width is determined by a resistor and capacitor connected to the circuit.
- ◆ Used in timing applications like pulse width generation, debouncing switches, and creating delay circuits.

Phase shift oscillator

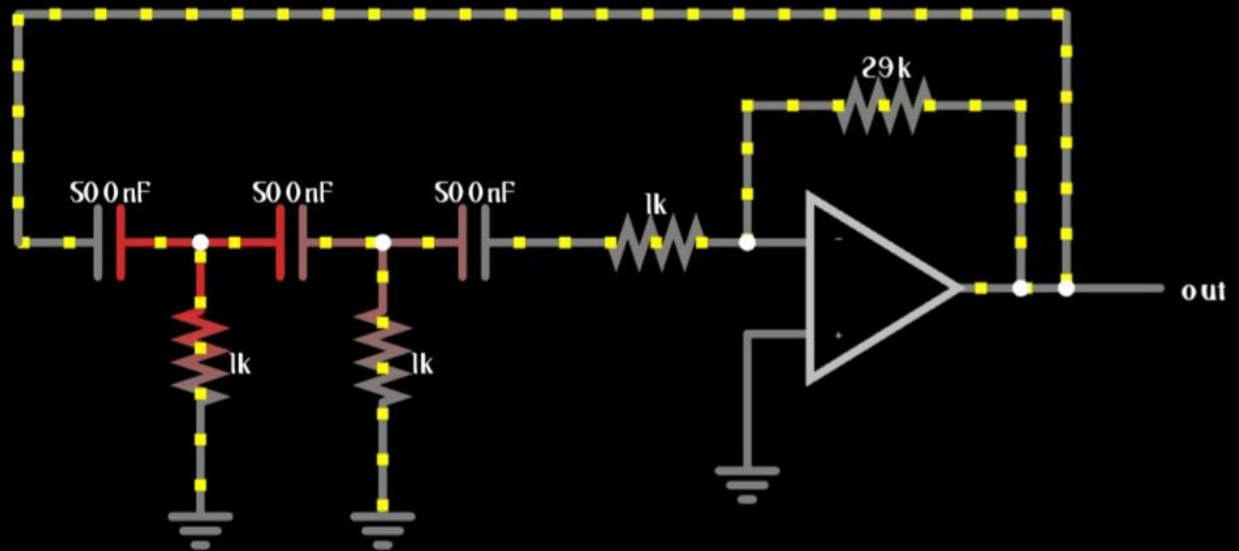


- ◆ Generates sinusoidal waveforms at low to mid-range frequencies using phase shift networks.
- ◆ Uses an amplifier (like a transistor or op-amp) and a series of RC networks to produce a 180-degree phase shift, combined with amplifier feedback to sustain oscillations.
- ◆ Commonly used in audio frequency generation, signal processing, and testing equipment .

Voltage - controlled oscillator

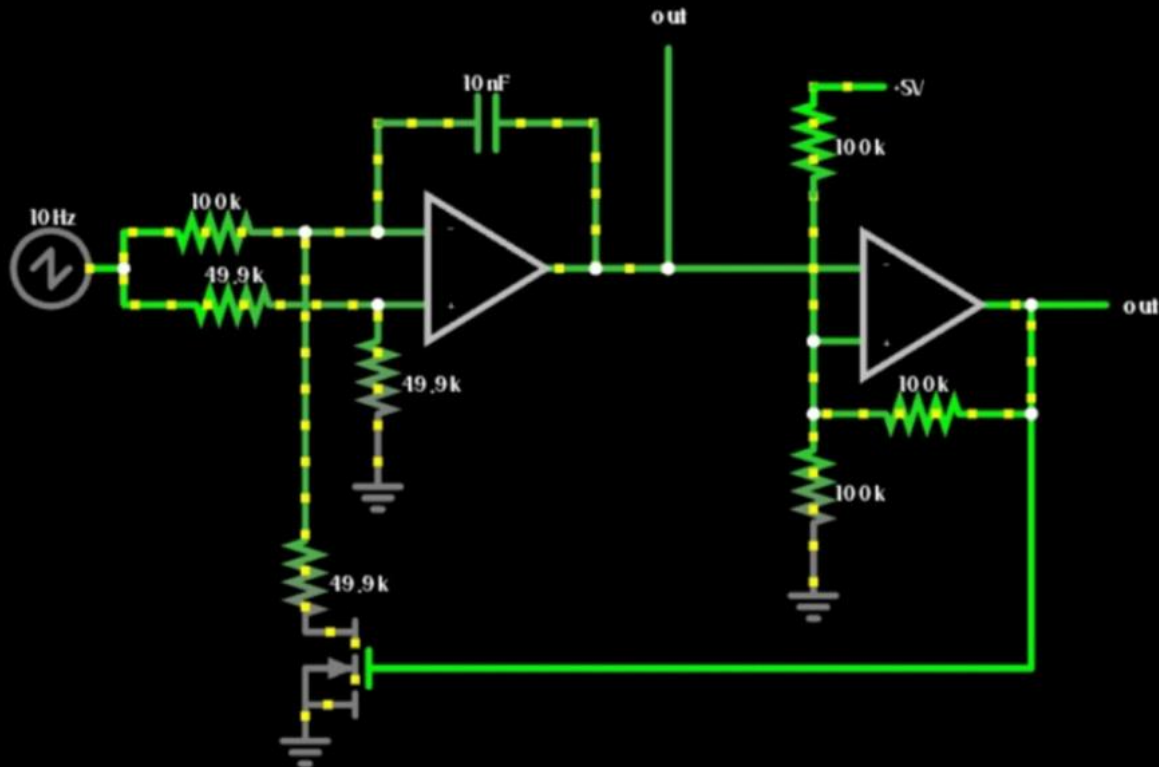


- ◆ Generates a frequency that is directly proportional to an input control voltage, allowing the frequency to be adjusted dynamically.
- ◆ Uses an electronic oscillator circuit where the control voltage modulates the timing components (e.g., capacitors or inductors) to change the oscillation frequency.
- ◆ used in communication systems, frequency modulation, synthesizers, and signal generation .

Basic power supply

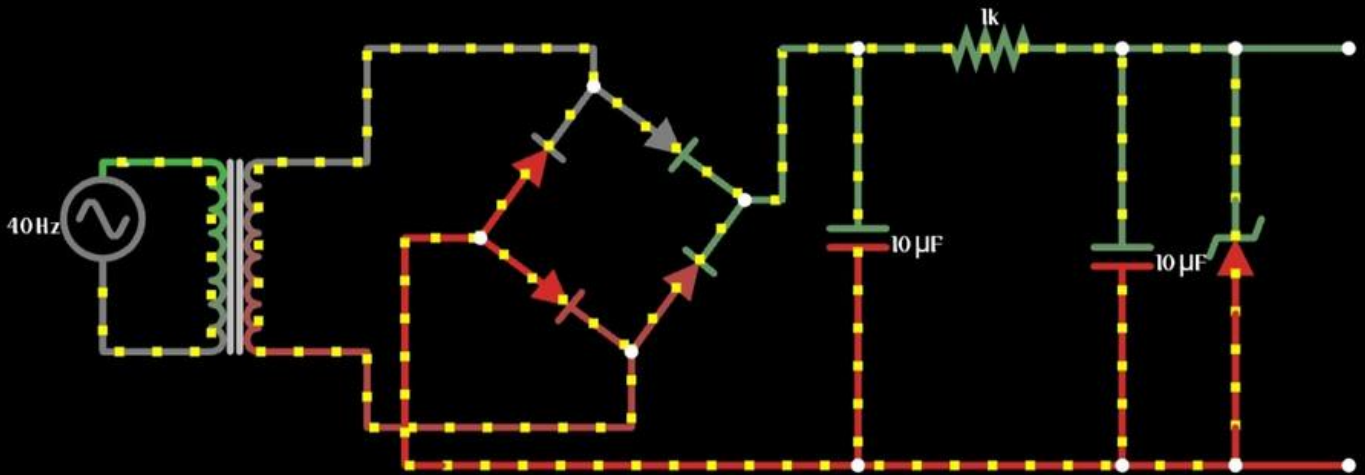


- ◆ Converts AC (alternating current) to DC (direct current) to provide power to electronic devices.
- ◆ Typically includes a transformer to step down voltage, a rectifier to convert AC to DC, a filter to smooth the output, and a voltage regulator to provide a stable DC output.
- ◆ Used in powering low-voltage devices, such as electronic circuits, microcontrollers, and communication equipment.

Zener diode as voltage regulator

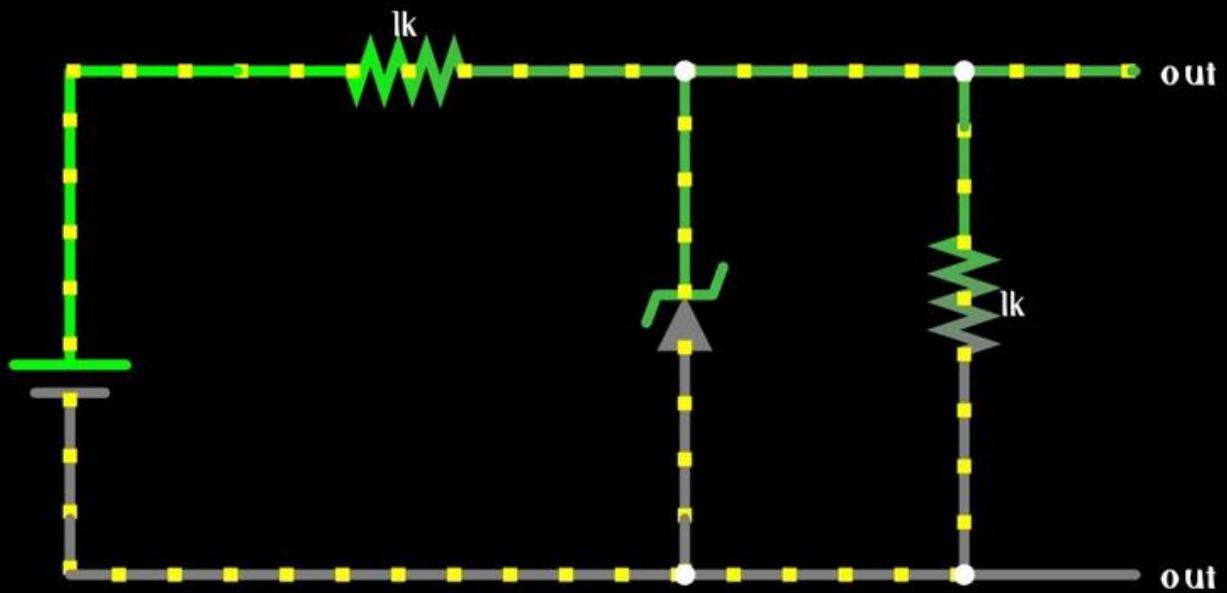


- ◆ Maintains a constant output voltage by allowing current to flow in the reverse direction once the Zener diode reaches its breakdown voltage.
- ◆ The Zener diode is placed in reverse bias across the load, and when the input voltage exceeds the Zener voltage.
- ◆ Commonly used in low-power voltage regulation applications, providing stable voltage for circuits like power supplies, protection circuits.

LM 317 adjustable regulator

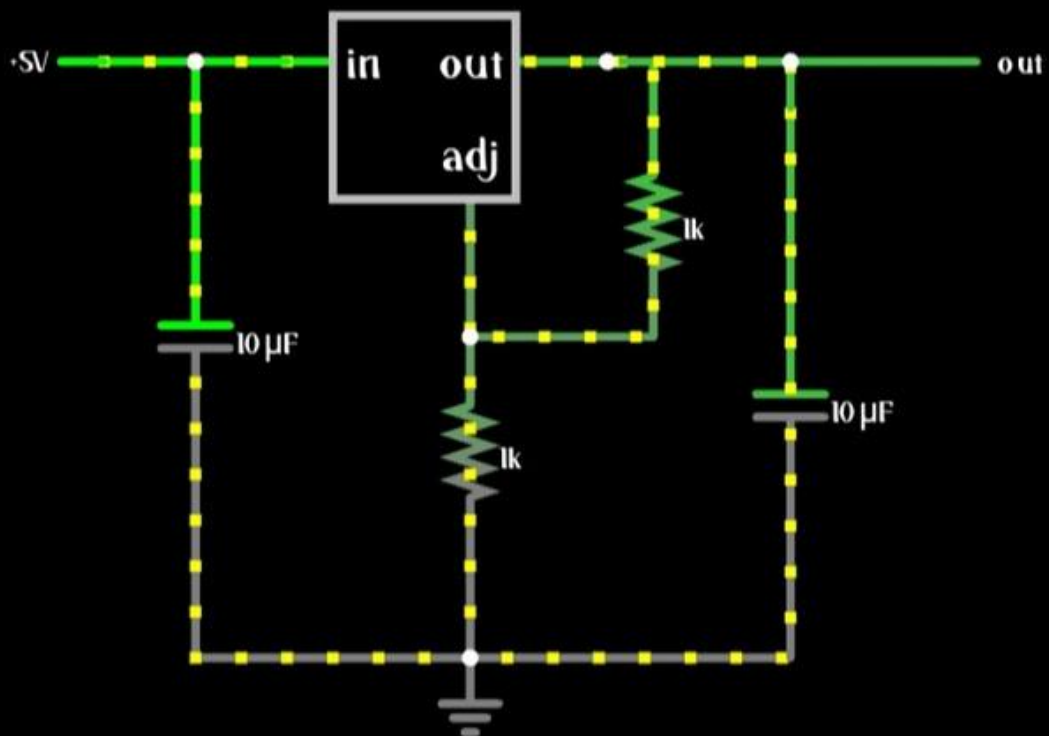

- ◆ Provides a stable output voltage that can be adjusted within a specific range by using external resistors.
- ◆ The LM317 adjusts the output voltage based on the ratio of two external resistors connected to its adjustment pin, allowing for a wide range of output voltages.
- ◆ Used in power supplies, battery chargers, and other applications where a stable and adjustable DC voltage is required.

Switch regulator

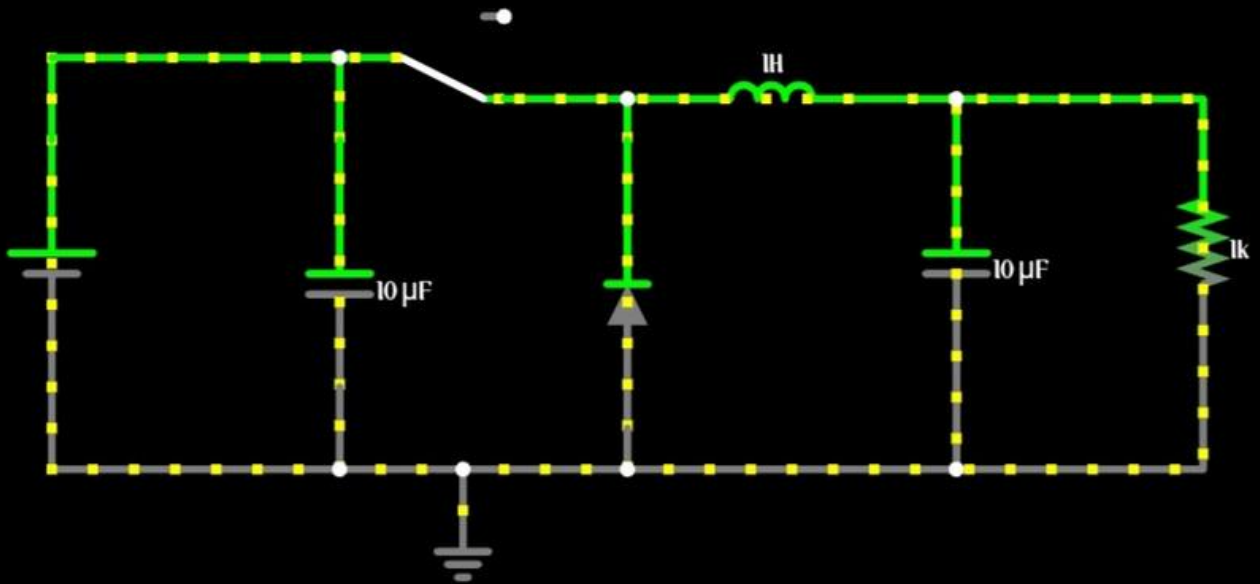


- ◆ Converts an input voltage to a different, stable output voltage using a high-efficiency switching method, either step-up (boost) or step-down (buck).

- ◆ Utilizes inductors, capacitors, and semiconductor switches to rapidly switch the input voltage on and off, storing energy in the inductor and then releasing it to regulate the output voltage.


- ◆ Commonly used in power supplies, battery-operated devices, and energy-efficient circuits.

Boost converter

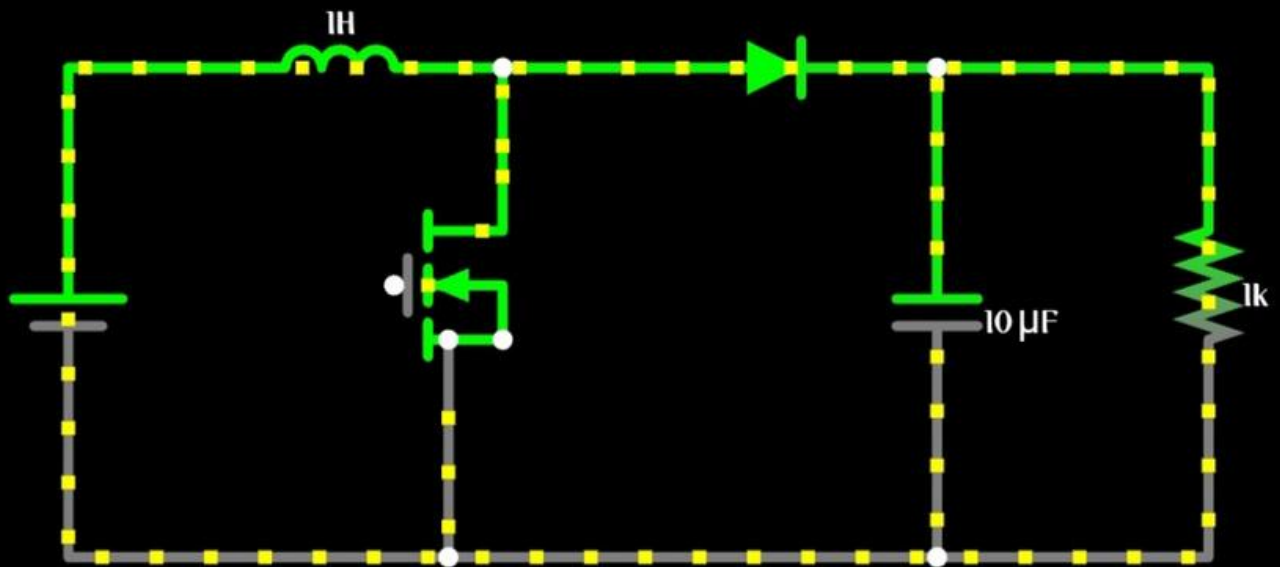


- ◆ Steps up (increases) a lower input voltage to a higher, stable output voltage.
- ◆ Uses an inductor, a diode, a switch (typically a transistor), and a capacitor to store energy during the "on" phase and release it during the "off" phase, boosting the voltage.
- ◆ Commonly used in battery-powered devices, power supplies, and renewable energy systems where a higher voltage is required.

Buck-boost converter

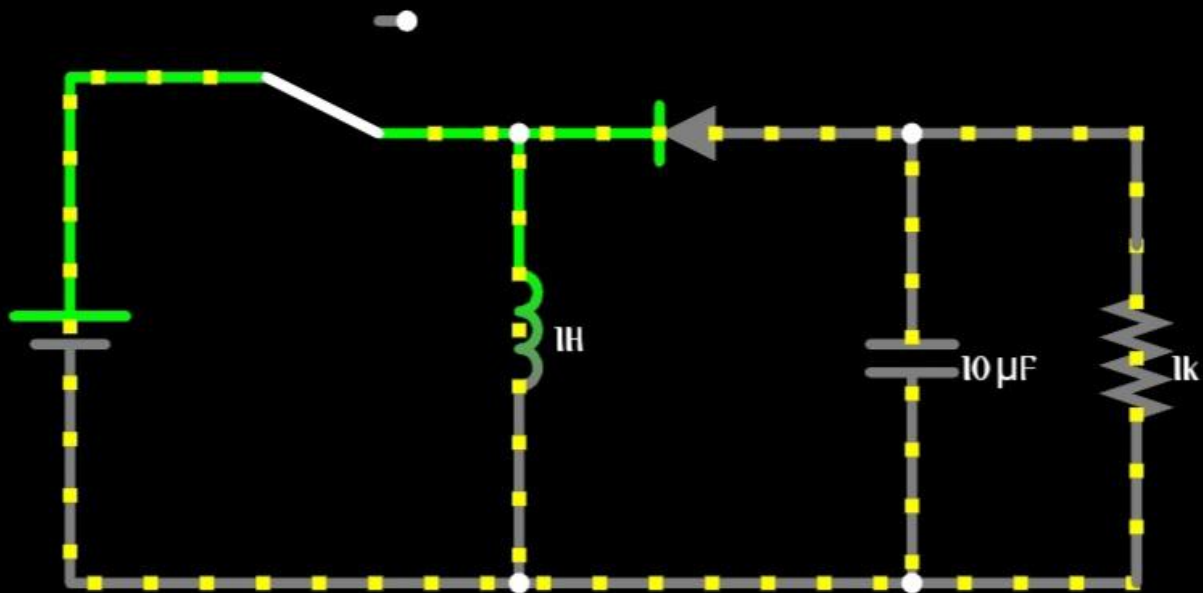


- ◆ Provides a stable output voltage that can be either higher or lower than the input voltage, depending on the configuration and load requirements.
- ◆ Combines the principles of both buck (step-down) and boost (step-up) converters, using an inductor, switch, diode, and capacitor to regulate the voltage.
- ◆ Used in applications where the input voltage can vary above or below the desired output voltage, such as in battery-powered devices.

Charge pump circuit

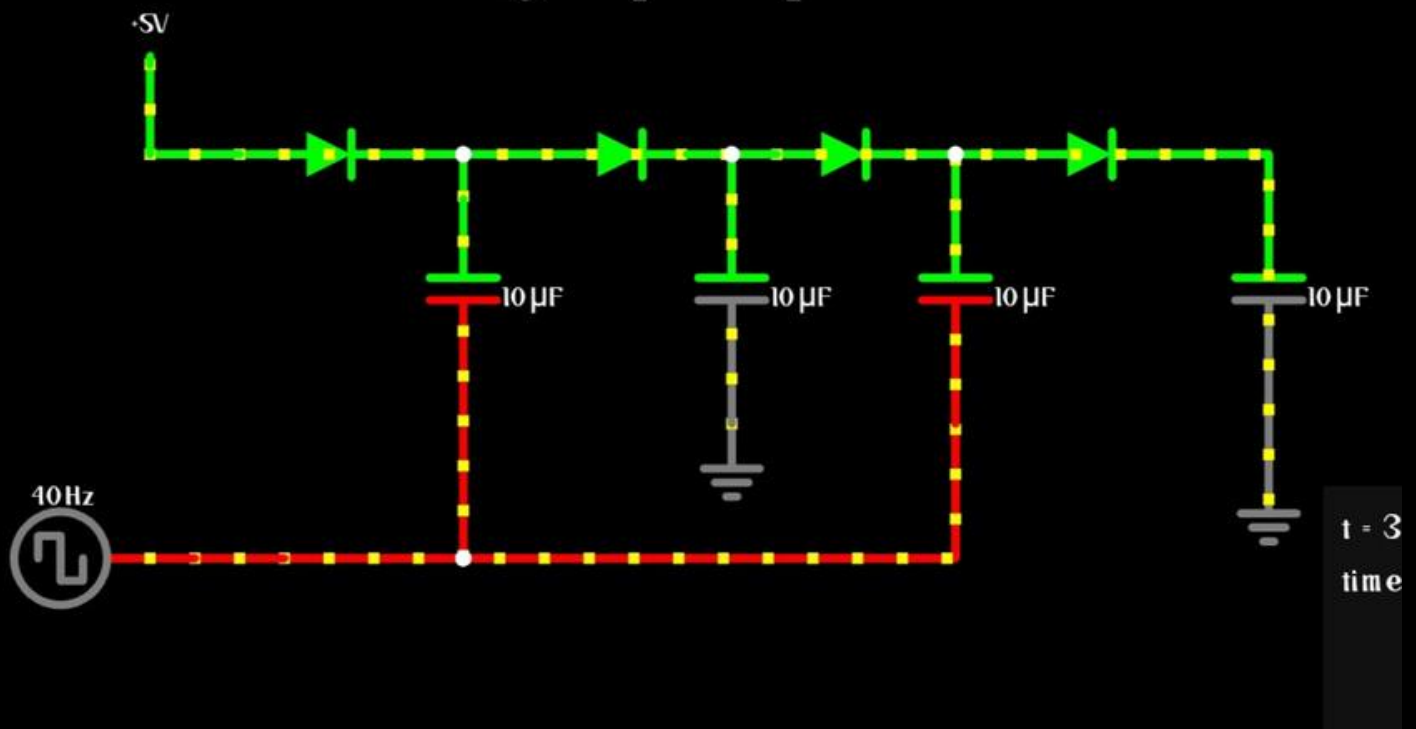


- ◆ Converts DC voltage from a lower level to a higher (boost) or lower (inverted) level using capacitors as energy storage elements instead of inductors.
- ◆ Uses a series of capacitors and switches (typically diodes or transistors) to transfer and "pump" charge in a sequence, changing the voltage level.
- ◆ Often used in low-power applications, such as in voltage doubling, inverting, or generating higher voltage rails .

Solar charger circuit

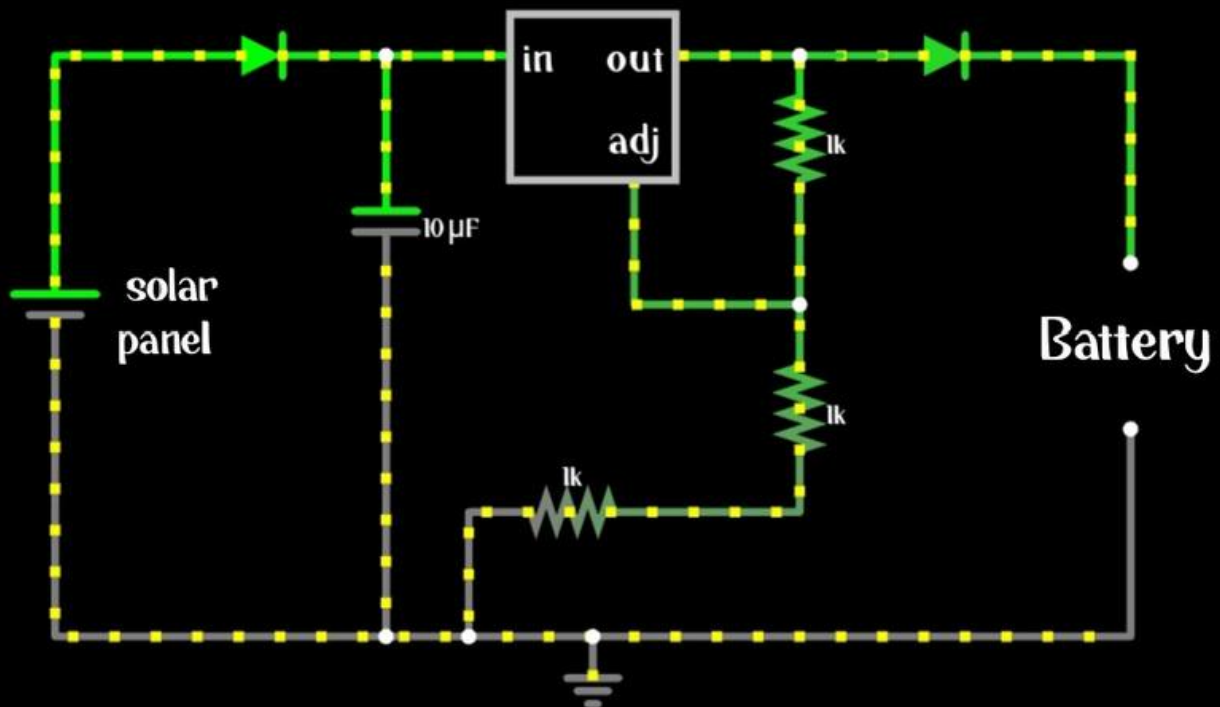


- ◆ Converts solar energy into electrical energy to charge batteries or power electronic devices.
- ◆ Uses a solar panel to convert sunlight into DC electricity, which is then regulated by a charge controller to safely charge the battery and prevent overcharging.
- ◆ Commonly used in solar-powered devices, off-grid systems, and portable battery charging solutions .

Battery management circuit

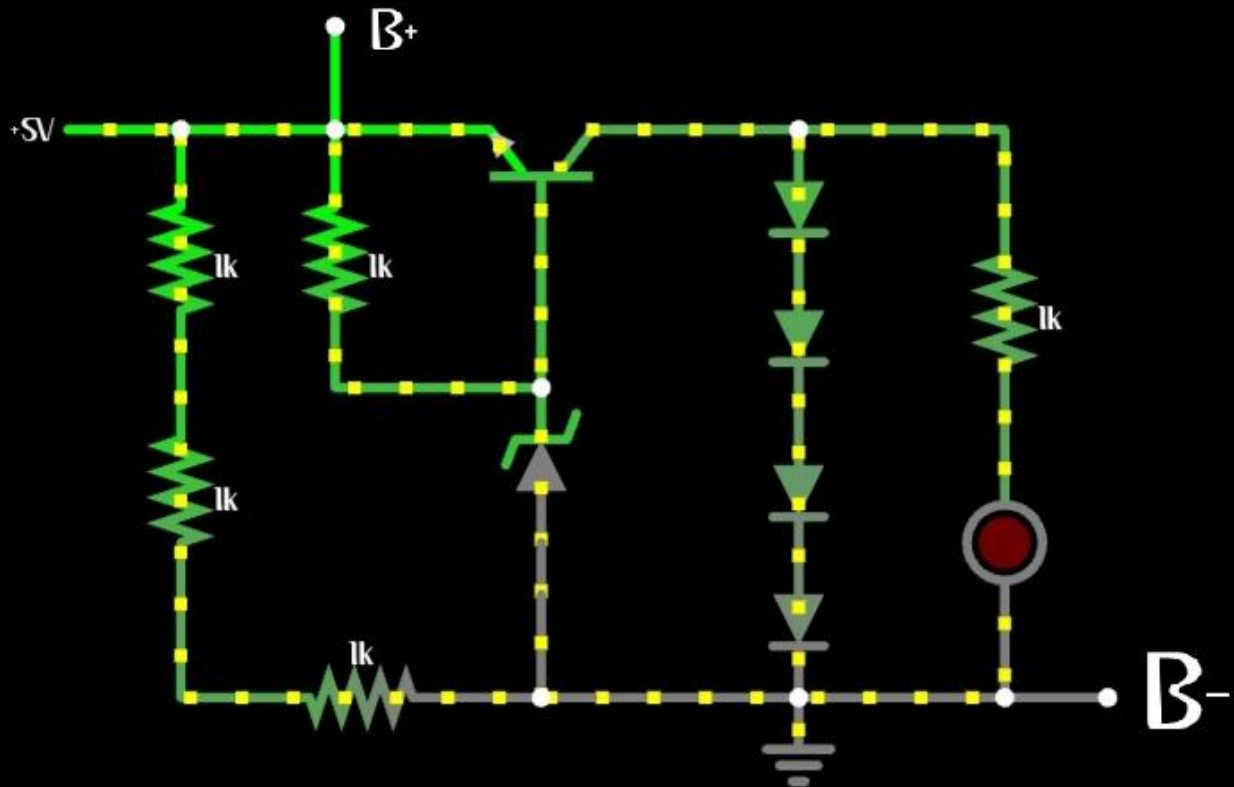


- ◆ Manages the charging, discharging, and overall health of a rechargeable battery to ensure safe and efficient operation.
- ◆ Includes a battery protection circuit to prevent overcharging, over-discharging, and excessive current, as well as a charge controller to regulate charging.
- ◆ Commonly used in lithium-ion and other rechargeable battery-powered devices, including electric vehicles, power banks.

Uninterruptible power supply (UPS)

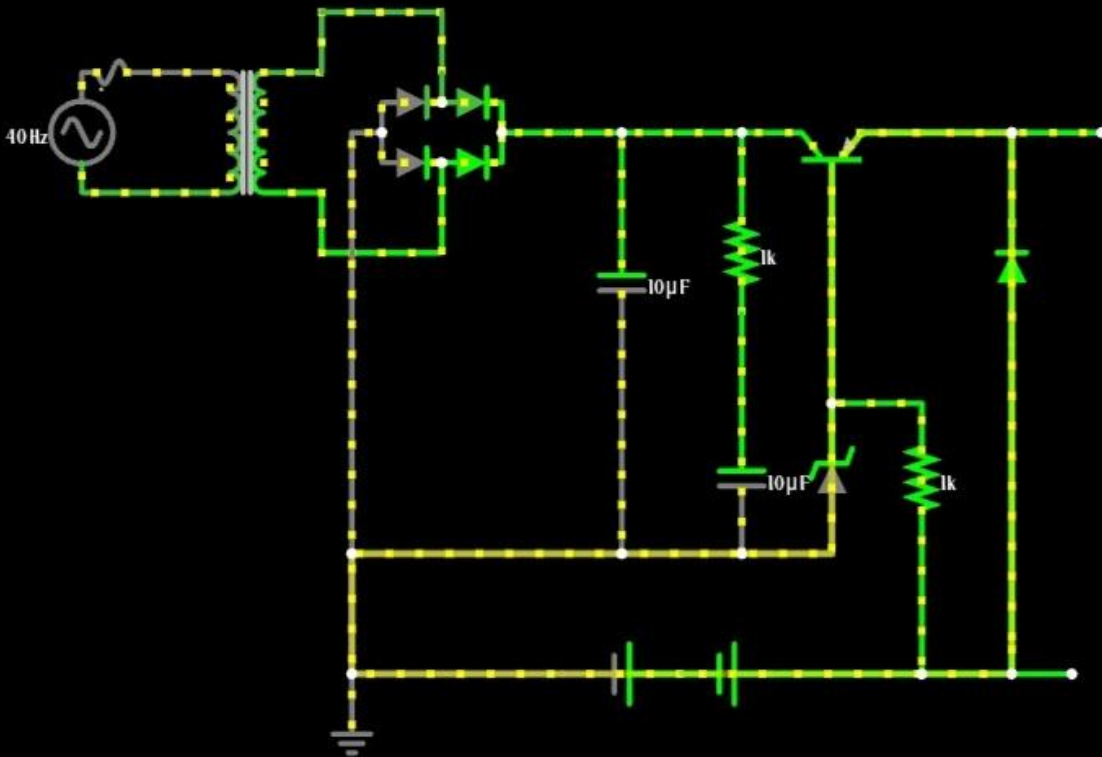


- ◆ Provides backup power to electronic devices during power outages, ensuring continuous operation and preventing data loss.
- ◆ Consists of a battery, charger, and inverter system, which stores energy in a battery and supplies it to connected devices .
- ◆ Widely used in homes, offices, and data centers to protect sensitive equipment like computers, servers, and medical devices.

AND gate using transistor

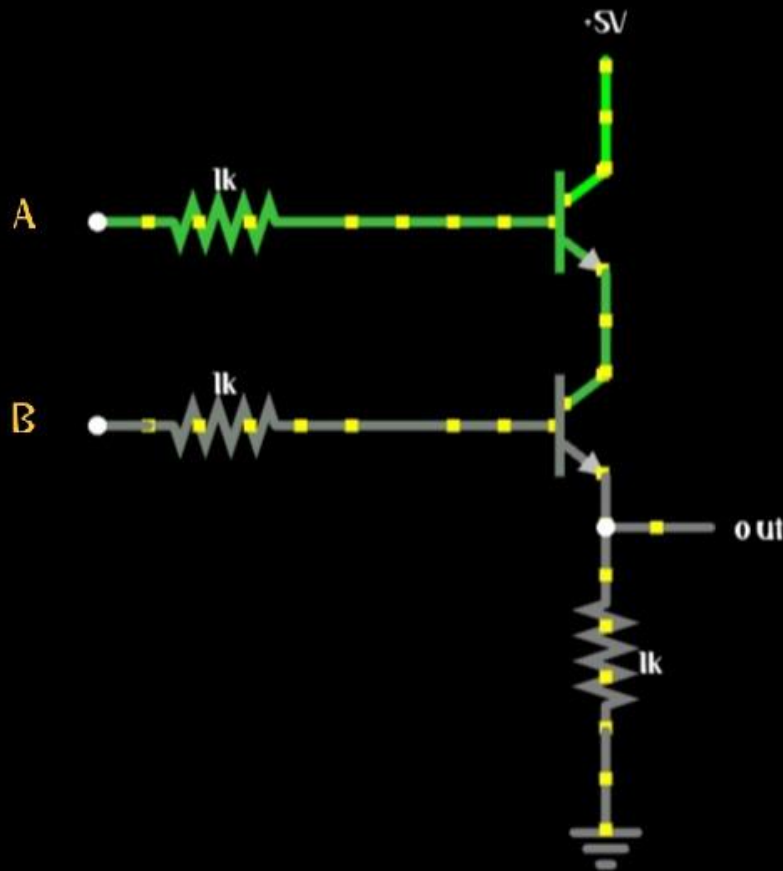


- ◆ Implements the logical AND operation, outputting a high signal only when both inputs are high.
- ◆ Uses two transistors in series, with each transistor acting as a switch. The output is high only when both transistors are turned on by their respective inputs, completing the circuit.
- ◆ Commonly used in digital logic circuits for performing binary operations.

OR gate using transistor

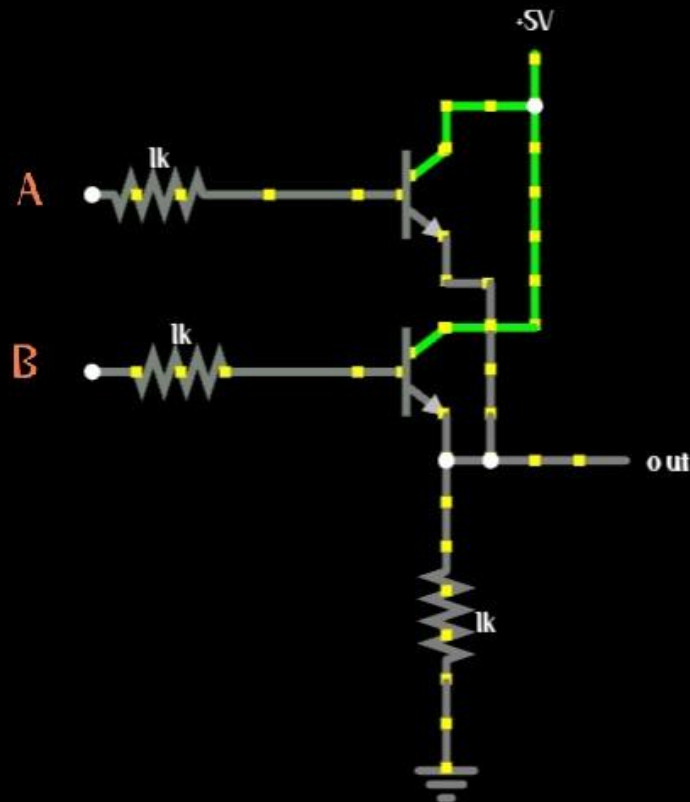


- ◆ Implements the logical OR operation, outputting a high signal when at least one of the inputs is high.
- ◆ Uses two transistors in parallel, with each transistor acting as a switch. The output is high if either of the transistors is turned on by its respective input, completing the circuit.
- ◆ Commonly used in digital circuits for decision-making processes, binary logic operations.

NOT gate using transistor

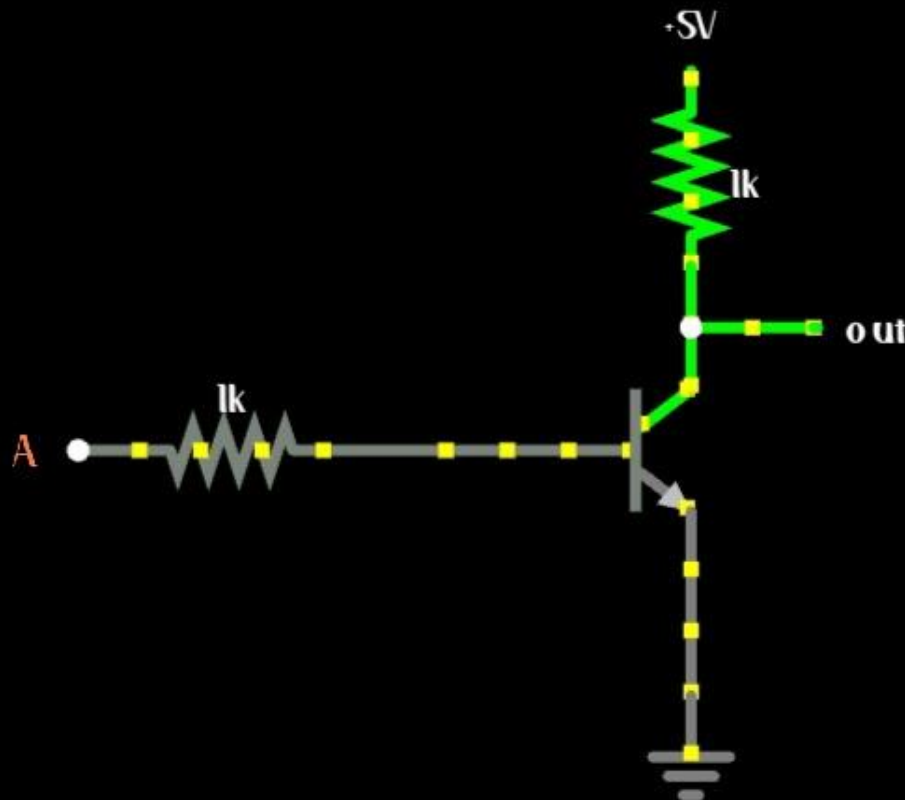


- ◆ Implements the logical NOT operation, inverting the input signal (output is high when input is low and vice versa).
- ◆ Uses a single transistor, typically in a common-emitter configuration, When the input is high, the transistor conducts and the output is low; when the input is low, the transistor is off, and the output is high.
- ◆ Used in digital logic circuits, signal inversion, and in building more complex logic gates and circuits.

NAND gate

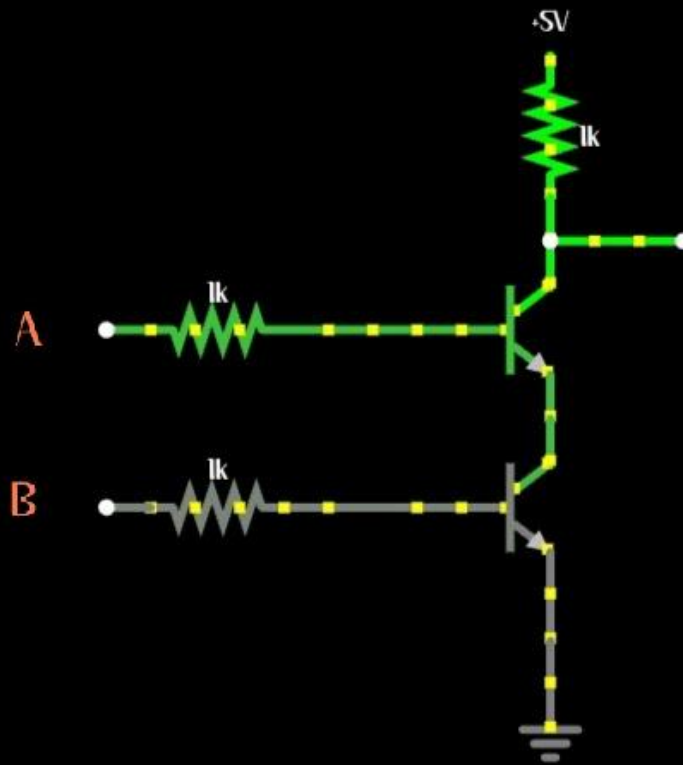


- ◆ Implements the logical NAND operation, outputting a low signal only when both inputs are high; otherwise, it outputs a high signal.
- ◆ Uses two transistors in series (similar to an AND gate), but with a NOT operation applied to the output. When either input is low, at least one transistor is off, and the output is high.
- ◆ Commonly used in digital electronics for building more complex logic circuits, memory storage, and arithmetic operations.

NOR gate

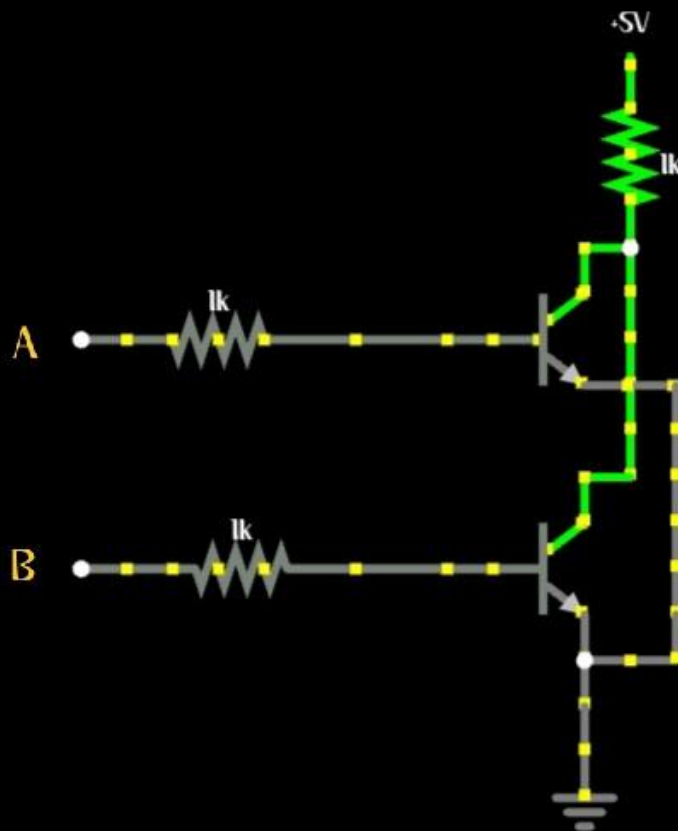


- ◆ Implements the logical NOR operation, outputting a high signal only when both inputs are low; otherwise, it outputs a low signal.
- ◆ Uses two transistors in parallel, arranged in a way that when both inputs are low, neither transistor conducts, and the output is high.
- ◆ Used in digital logic circuits, especially in building other complex gates, memory circuits, and for performing decision-making operations .

XOR gate

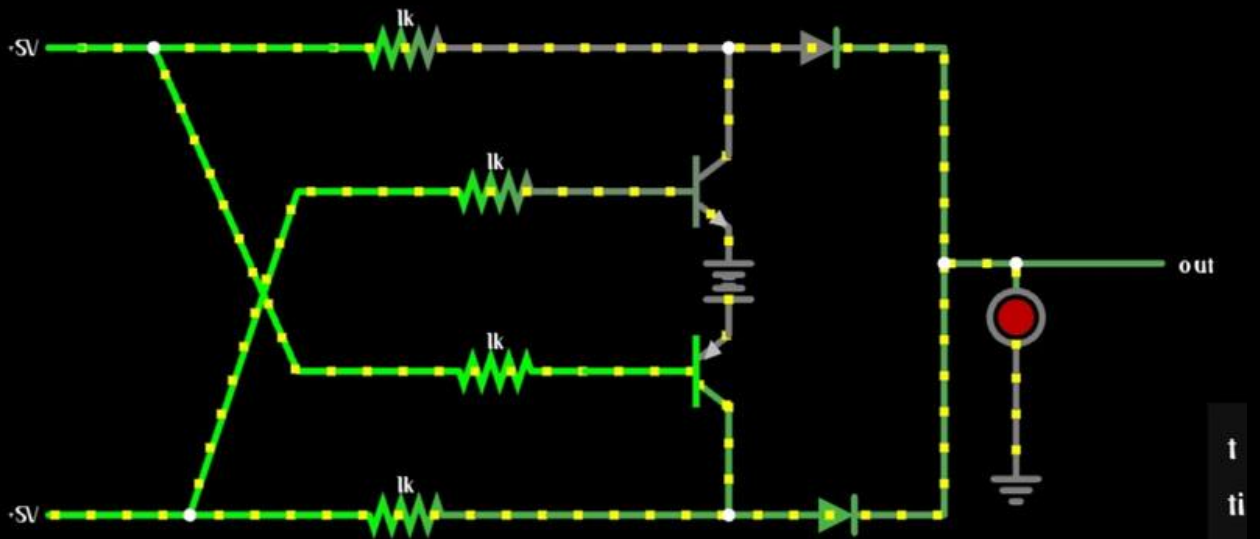


- ◆ Implements the logical XOR (exclusive OR) operation, outputting a high signal when the inputs are different (one high, one low), and a low signal when the inputs are the same (both high or both low).
- ◆ The output is high only when exactly one of the two inputs is high, as the transistors switch accordingly.
- ◆ Used in digital circuits for tasks such as error detection, arithmetic operations (like adders), and signal comparison in logic systems.

XNOR gate

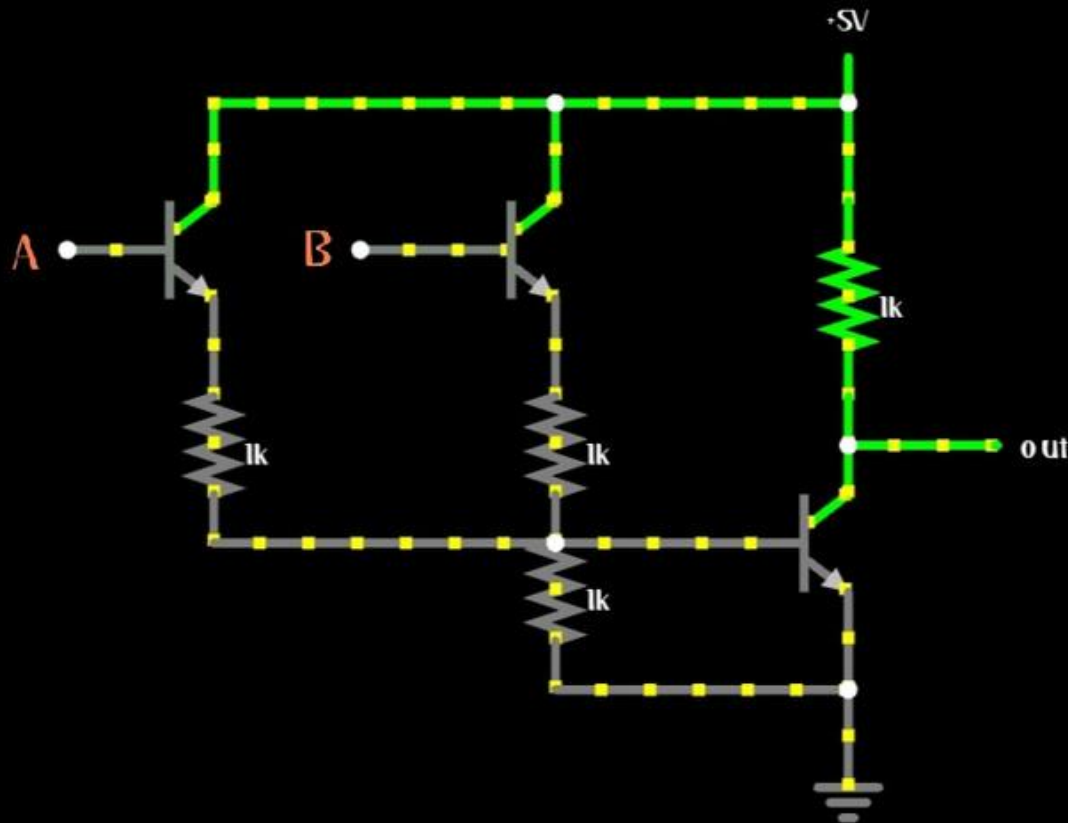


- ◆ Implements the logical XNOR (exclusive NOR) operation, outputting a high signal when the inputs are the same (both high or both low), and a low signal when the inputs are different.
- ◆ Typically uses a combination of XOR and NOT gates. The circuit is built with multiple transistors arranged in series and parallel .
- ◆ Commonly used in digital circuits for equality comparison, parity checking.

Half adder

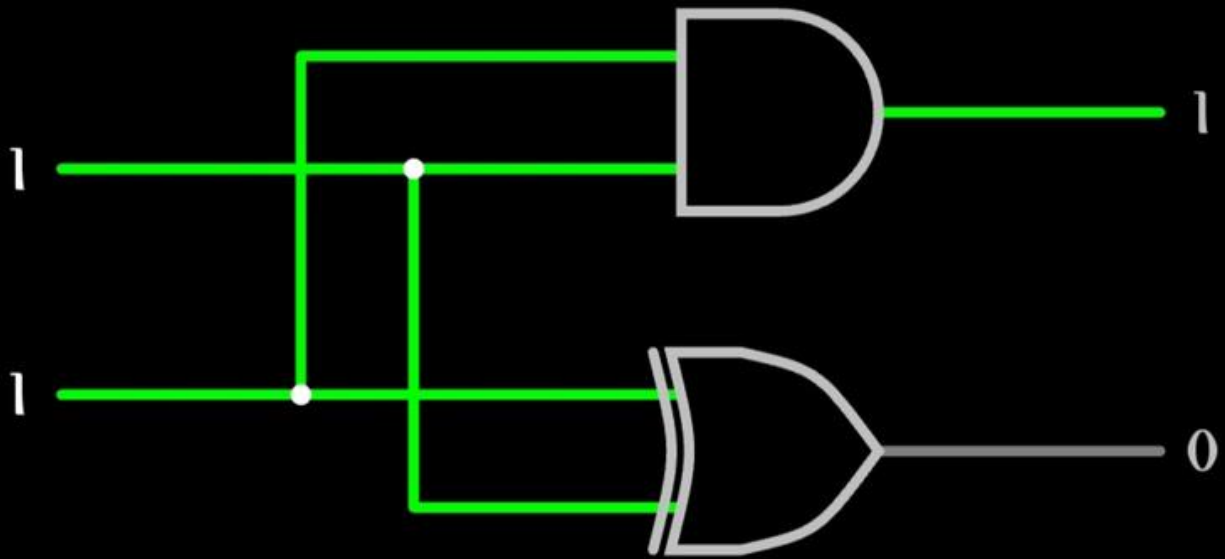


- ◆ Performs the addition of two single-bit binary numbers, providing a sum and a carry output.
- ◆ The sum output is generated by an XOR gate, and the carry output is generated by an AND gate. The circuit adds the two input bits and handles carry-over when both bits are 1.
- ◆ Used in digital systems, particularly in arithmetic logic units (ALUs), binary addition operations.

Full adder

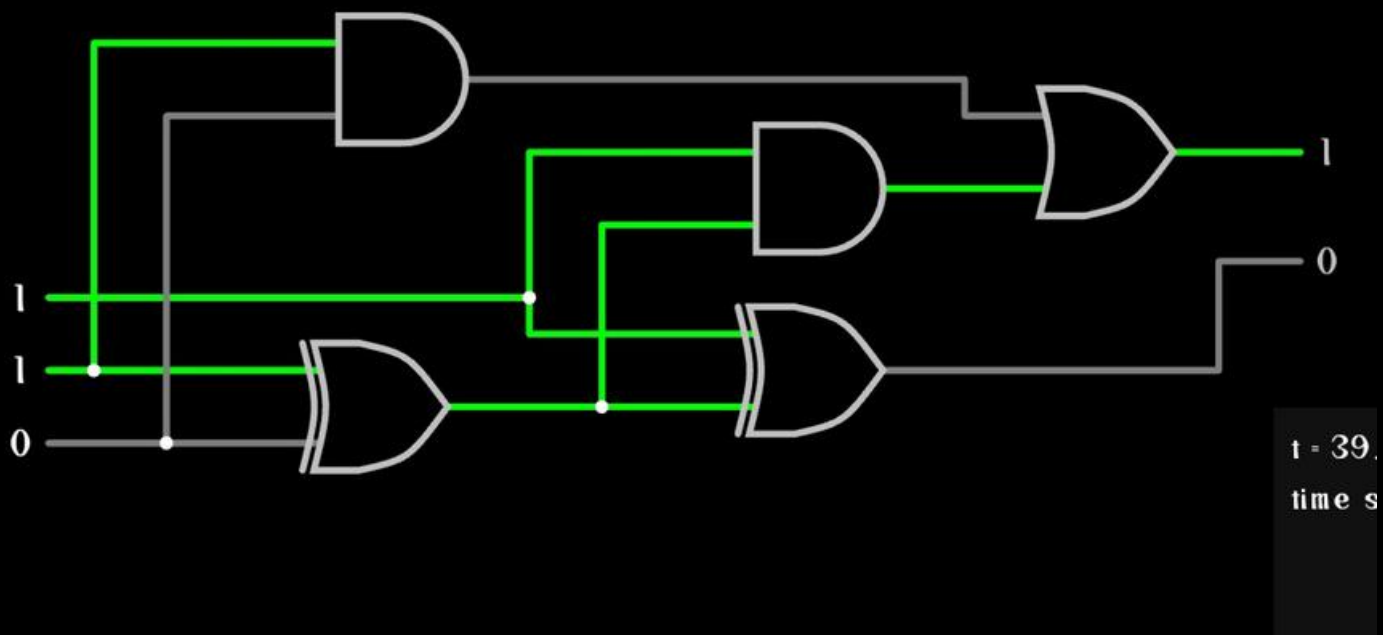


- ◆ Adds three input bits and produces a sum and a carry-out.
- ◆ The sum output is generated by an XOR gate (for the two input bits and carry-in), while the carry-out is determined by an OR gate combining the results of two AND gates, each evaluating the carry conditions from the inputs.
- ◆ Used in digital arithmetic operations, including in the construction of ALUs .

Multiplexer (2:1)

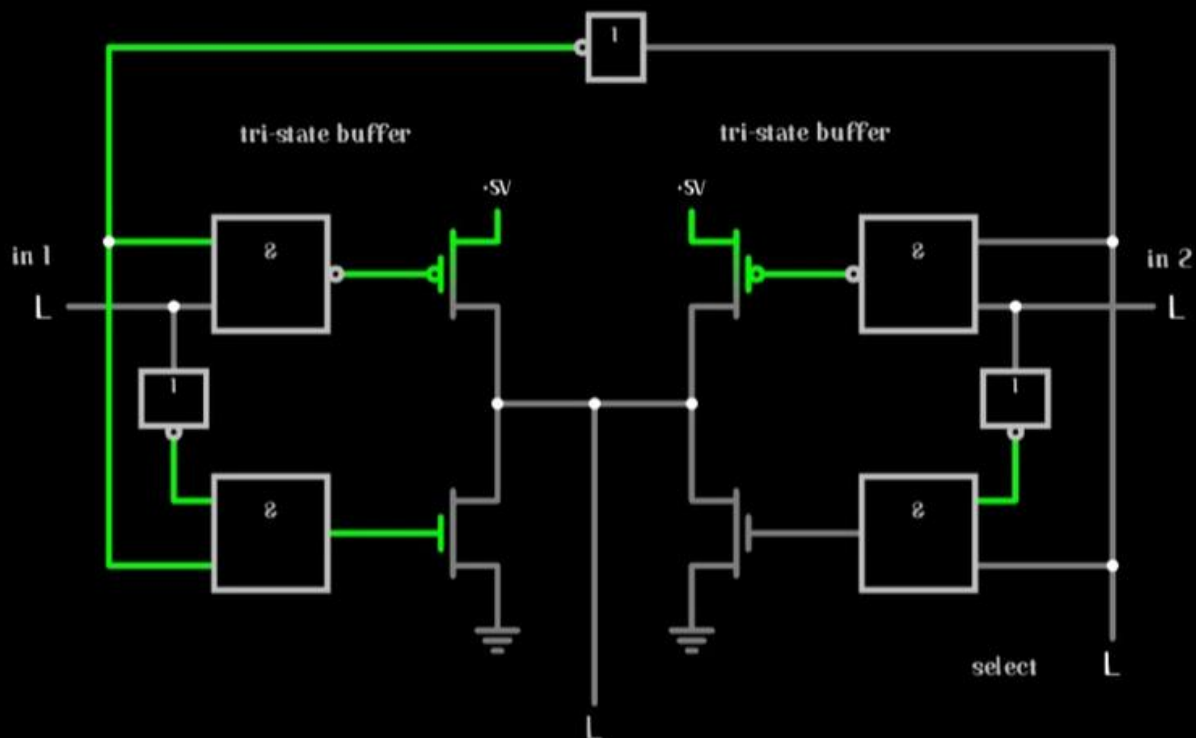


- ◆ Selects one of two input signals based on a control (select) line and outputs the chosen signal.
- ◆ The MUX has two data inputs (I0 and I1), one select input (S), and one output (Y). The output is determined by the value of the select input: when S is 0, the output is I0; when S is 1, the output is I1.
- ◆ Commonly used in digital systems for data routing, signal multiplexing, and in applications requiring the selection between two data sources.

Synchronous counter

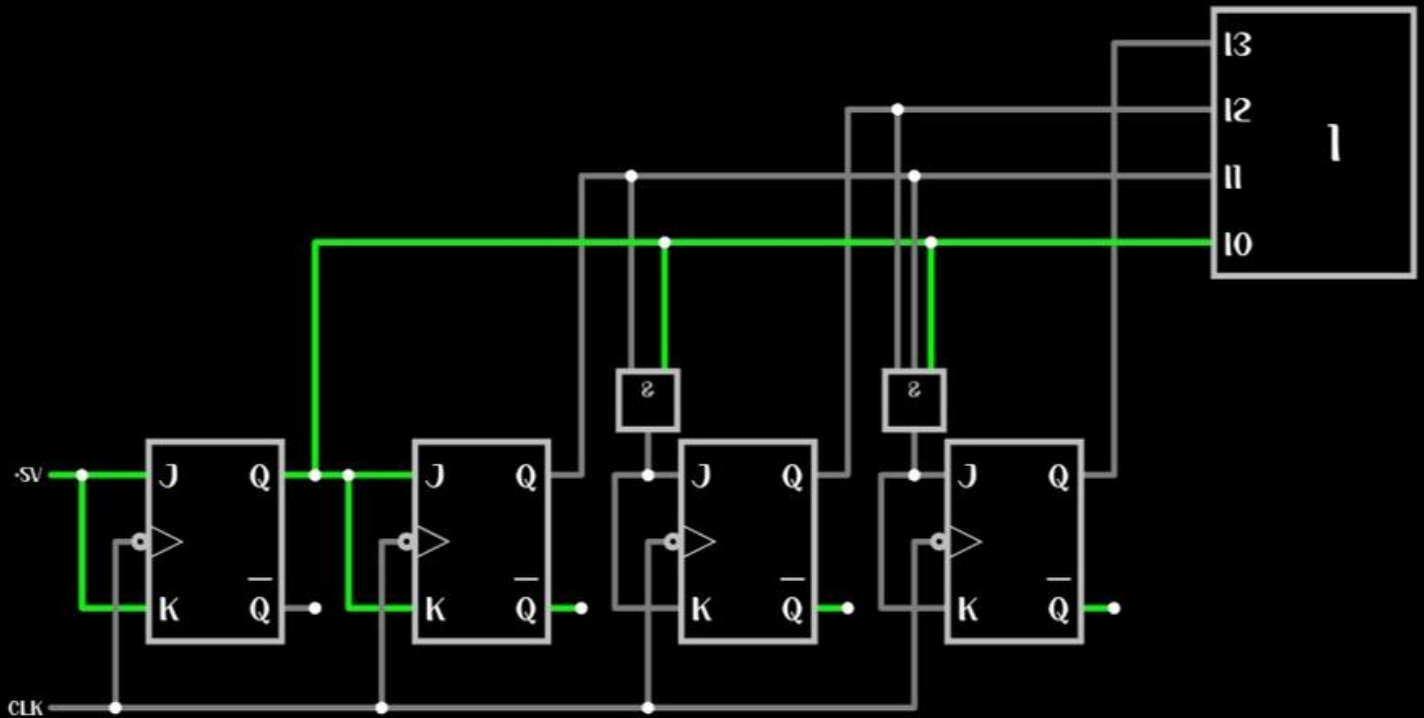


- ◆ Selects one of two input signals based on a control (select) line and outputs the chosen signal.
- ◆ The MUX has two data inputs (I₀ and I₁), one select input (S), and one output (Y). The output is determined by the value of the select input: when S is 0, the output is I₀; when S is 1, the output is I₁.
- ◆ Commonly used in digital systems for data routing, signal multiplexing.

Asynchronous counter

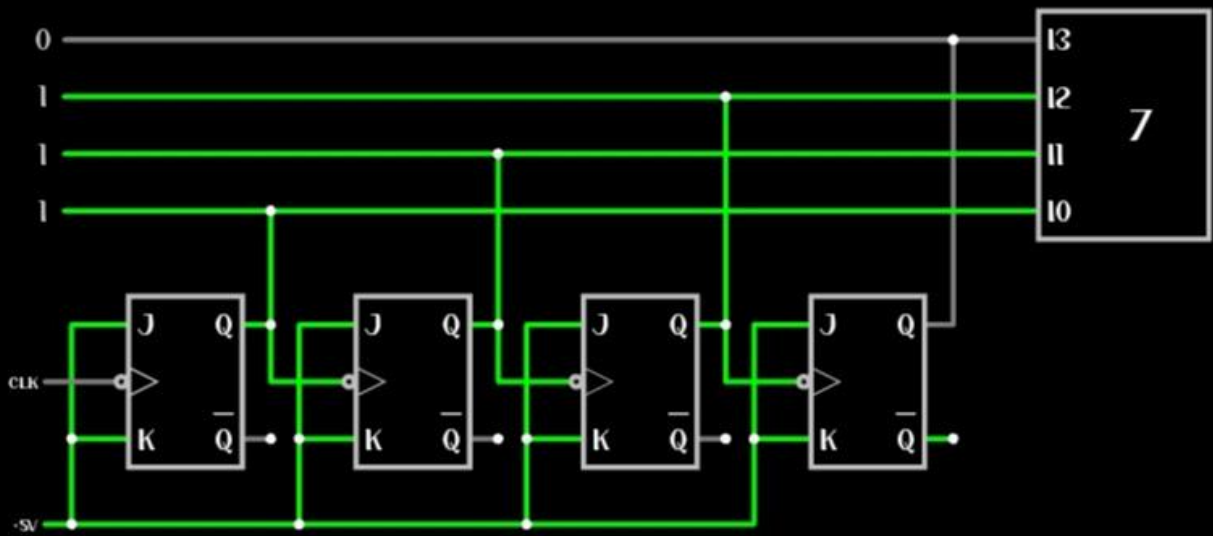


- ◆ Counts in a sequence based on clock pulses, where all flip-flops receive the clock signal simultaneously, ensuring synchronized operation.
- ◆ Each flip-flop in the counter changes state in sync with the clock signal, and the output changes according to the binary counting sequence (e.g., 0-1-2-3, etc.).
- ◆ Used in applications requiring synchronized counting, such as timers, frequency division, and digital clocks.

Serial in - parallel out shift register

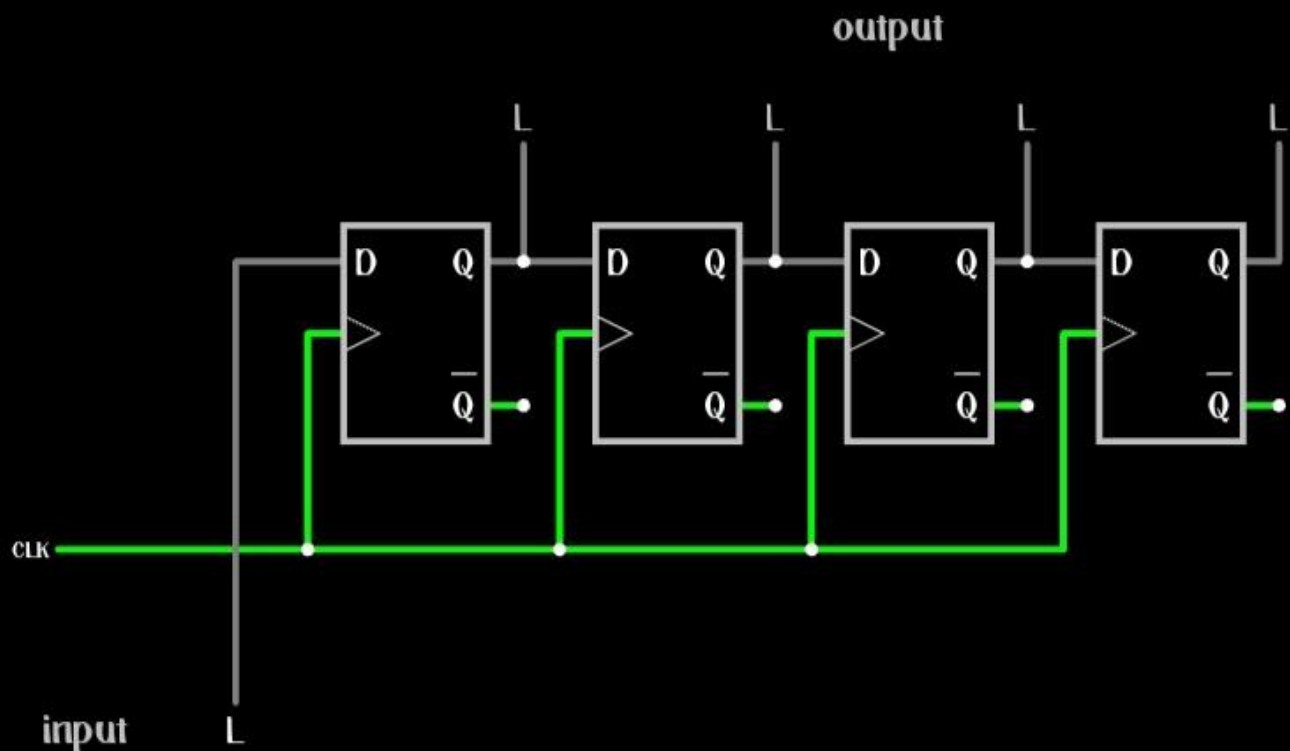


- ◆ Converts serial input data into parallel output, shifting data bit by bit through a series of flip-flops, with each flip-flop storing one bit of data.
- ◆ Data is fed serially into the first flip-flop, and as the clock pulses, each flip-flop shifts its data to the next one. After several clock cycles, the data is available in parallel at the outputs.
- ◆ Commonly used in data transfer applications where serial data needs to be converted to parallel form.

Parallel in - serial out shift register

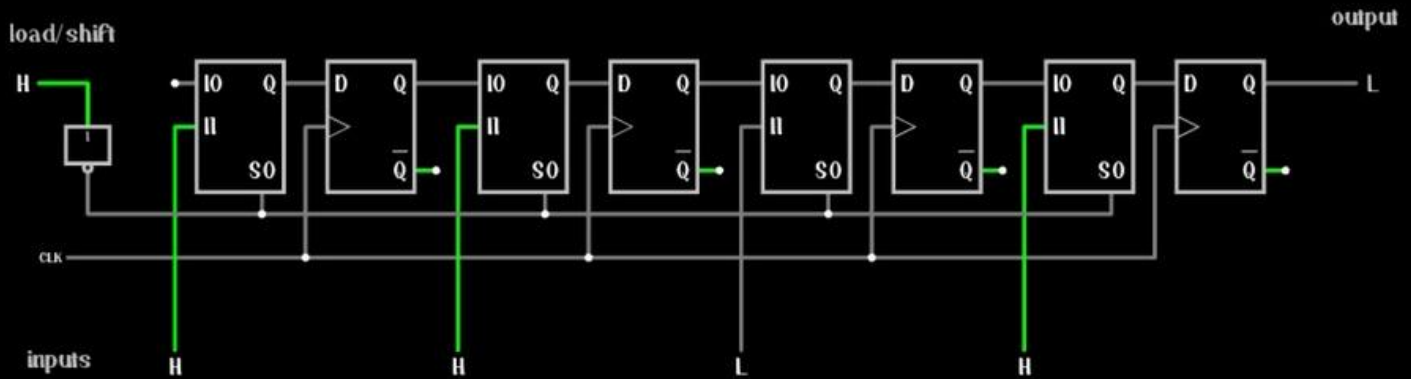


- ◆ Converts parallel input data into serial output, allowing multiple bits of data to be loaded simultaneously and then shifted out one bit at a time.
- ◆ Data is loaded in parallel into the shift register's flip-flops. With each clock pulse, the data is shifted through the register, and eventually, it is output serially from the last flip-flop.
- ◆ Used in digital systems for applications such as data transmission, serial data storage systems.

BCD counter

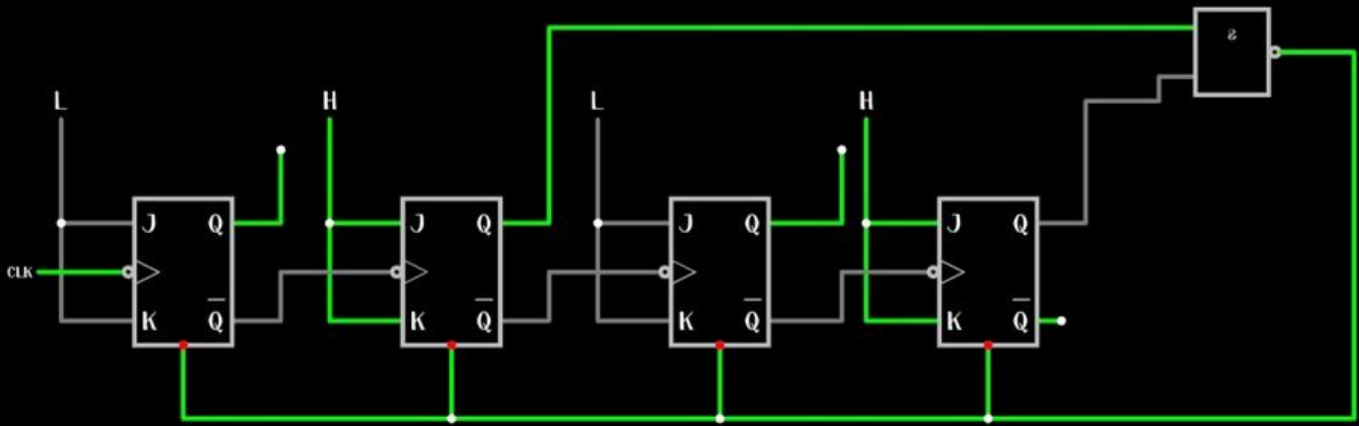


- ◆ A counter that counts in BCD, representing decimal digits (0-9) in binary form, where each digit is encoded using four bits.
- ◆ The counter increments in binary but resets after reaching 9 (1001 in binary), ensuring it only counts valid decimal digits, typically used for displaying decimal numbers.
- ◆ Commonly used in digital clocks, seven-segment displays, and other systems.

Gray code counter

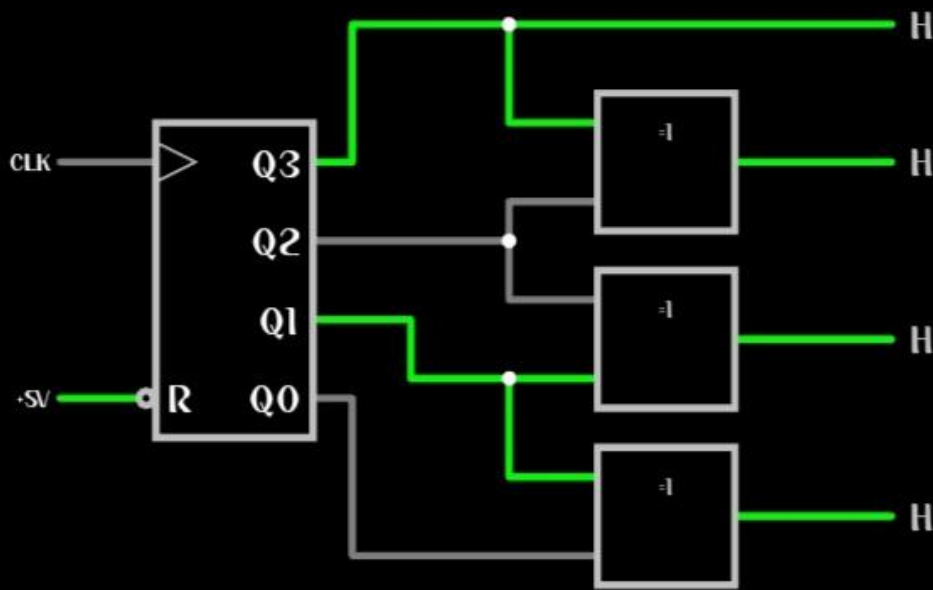


- ◆ A counter that counts in Gray code, where each successive value differs from the previous one by only one bit.
- ◆ The counter generates a sequence of Gray code values, where each output bit changes in such a way that only one bit changes at a time.
- ◆ Used in rotary encoders, digital position tracking, and in systems where minimizing errors during state transitions is critical.

Up-down counter

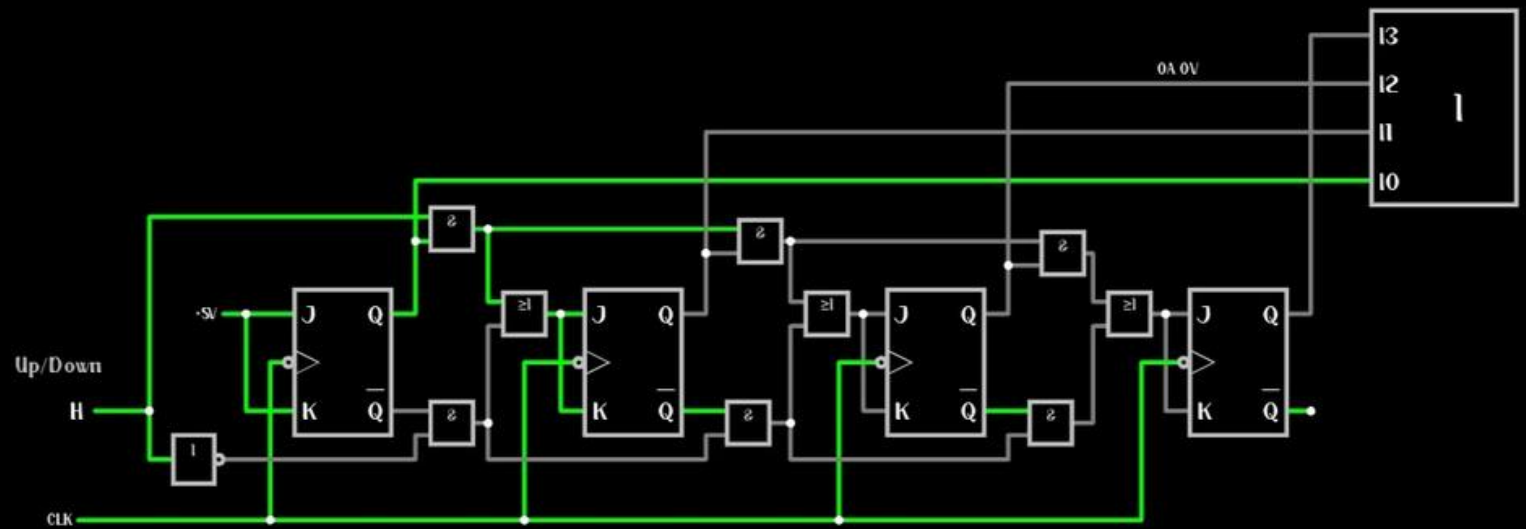


- ◆ A counter that increments or decrements based on a control input (up/down).
- ◆ The counter counts up or down with each clock pulse, depending on the control signal.
- ◆ Used in systems requiring bidirectional counting, such as digital clocks and position encoders.

Decimal counter

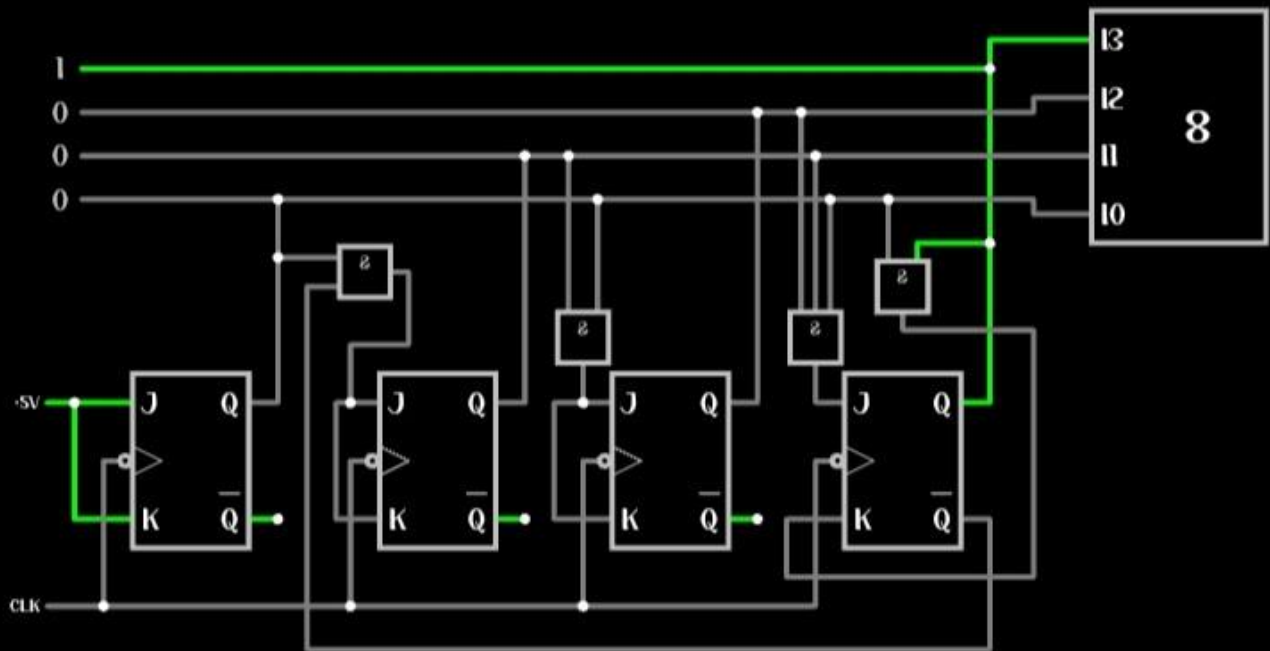


- ◆ A counter that counts from 0 to 9, representing decimal digits in binary.
- ◆ The counter increments with each clock pulse and resets to 0 after reaching 9.
 - ◆ Used in applications requiring decimal digit counting, such as digital clocks, calculators, and frequency counters.

Ring counter

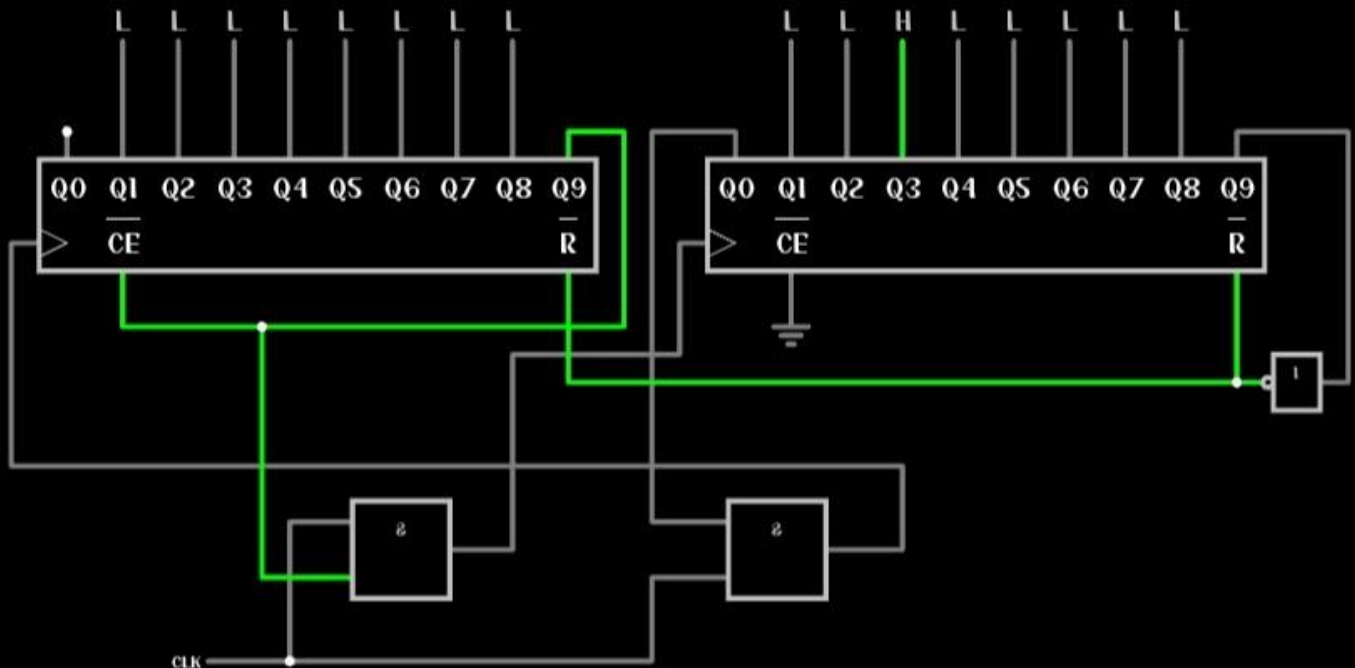


- ◆ A counter where only one bit is "high" at any time, and it circulates through a sequence of states, returning to the initial state after completing the cycle.
- ◆ The counter shifts the "high" bit around the register with each clock pulse, creating a continuous loop of states.
- ◆ Used in sequence generation, digital control systems, and in applications where cyclic counting or rotation is required.

Johnson counter

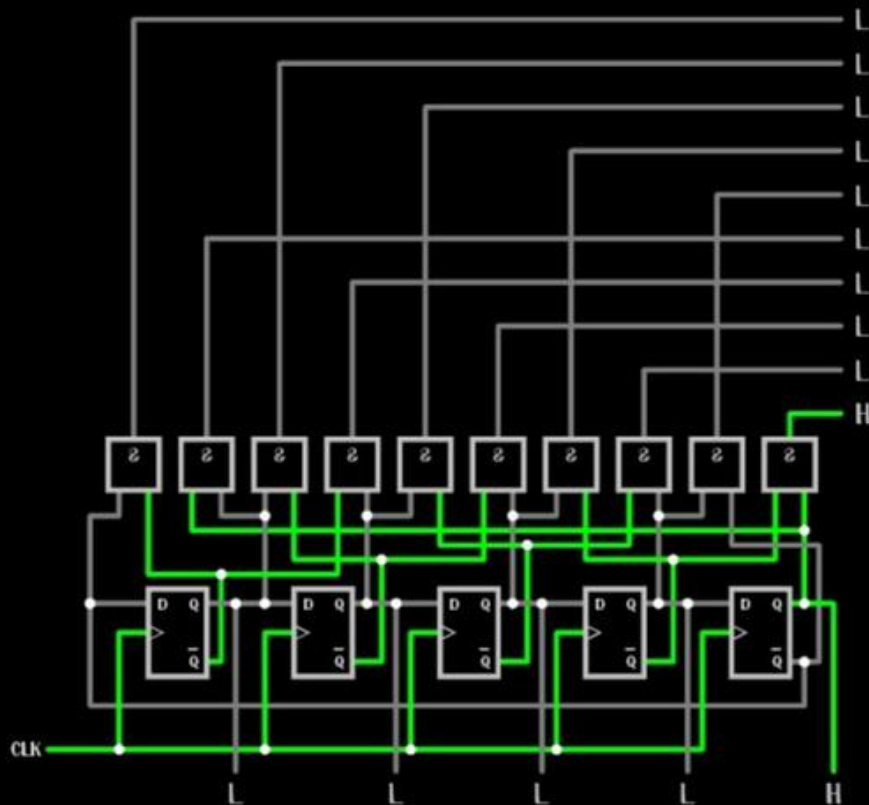


- ◆ A counter that generates a unique sequence by feeding back the inverted output of the last flip-flop into the first.
- ◆ Shifts bits through flip-flops to produce a sequence that cycles through $2n$ states.
- ◆ Used in sequence generation, PWM, and LED control.

555 Timer delay circuit

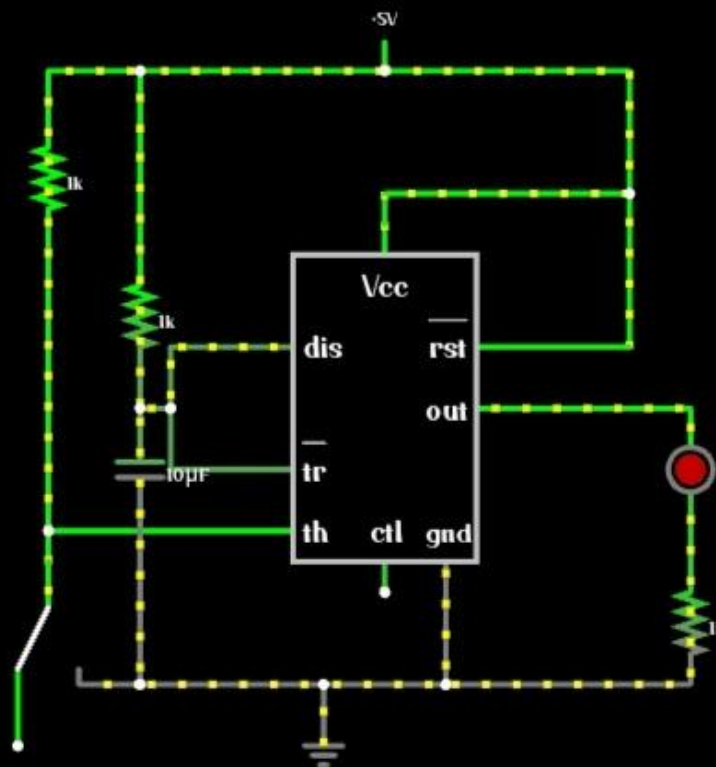


- ◆ Generates a precise time delay based on external resistor and capacitor values.
 - ◆ The 555 timer operates in monostable mode, producing a single pulse of desired duration when triggered.
- ◆ Used in timing applications like delay circuits, pulse generation, and triggering systems.

555 Timer pulse width modulation

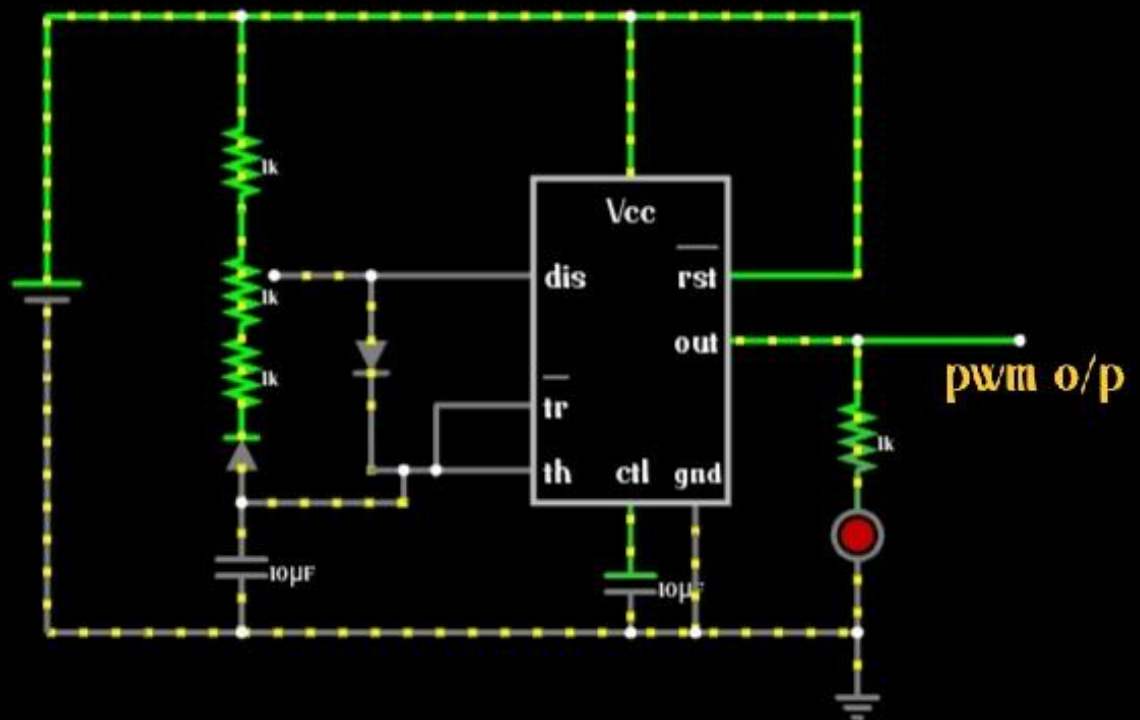


- ◆ Generates a pulse-width modulated (PWM) signal to control the duty cycle of an output waveform.
- ◆ Operates in astable mode, where the duty cycle is adjusted by varying the resistors or a control voltage.
- ◆ Used in motor speed control, LED dimming, and signal modulation.

Sequential timer circuit

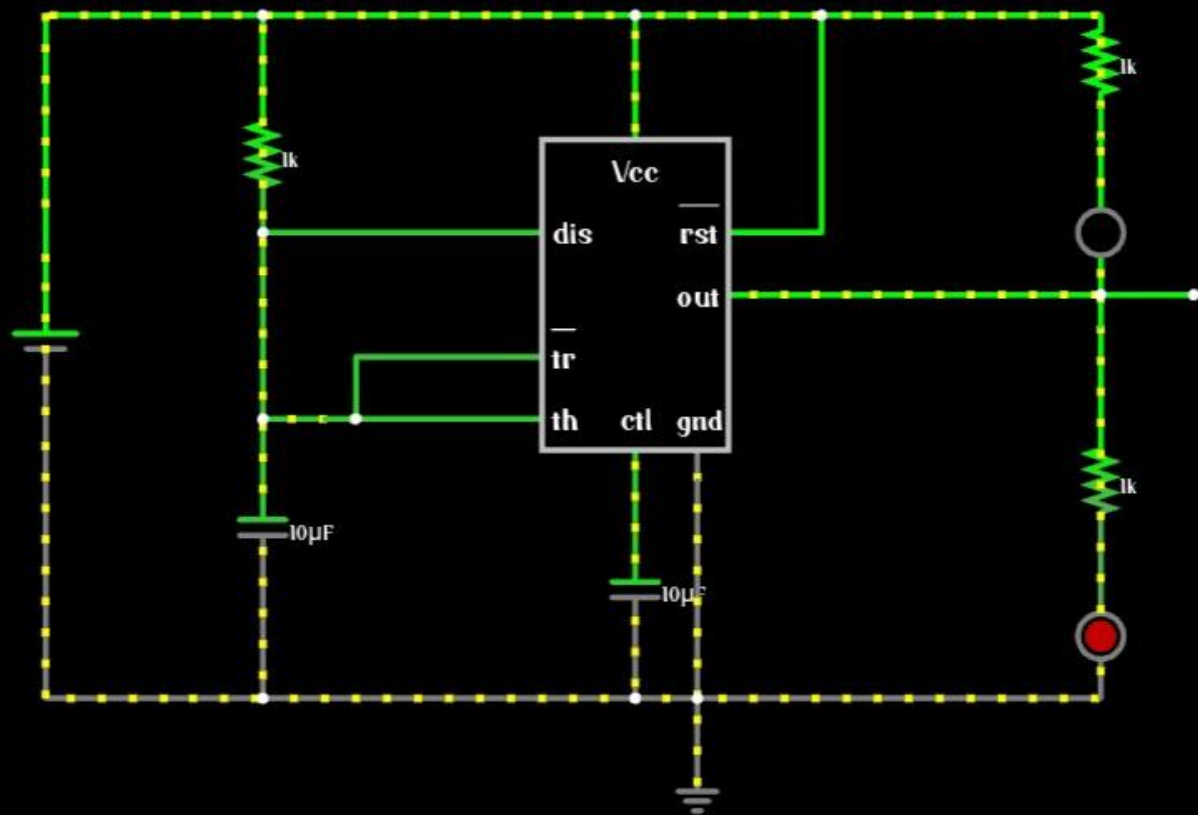


- ◆ Activates multiple outputs sequentially, each for a set time interval, based on a clock or trigger signal.
- ◆ Uses a series of 555 timers or counters to control the timing and order of activation for connected outputs.
- ◆ Used in automation systems, lighting control, and process sequencing.

Dual timer circuit

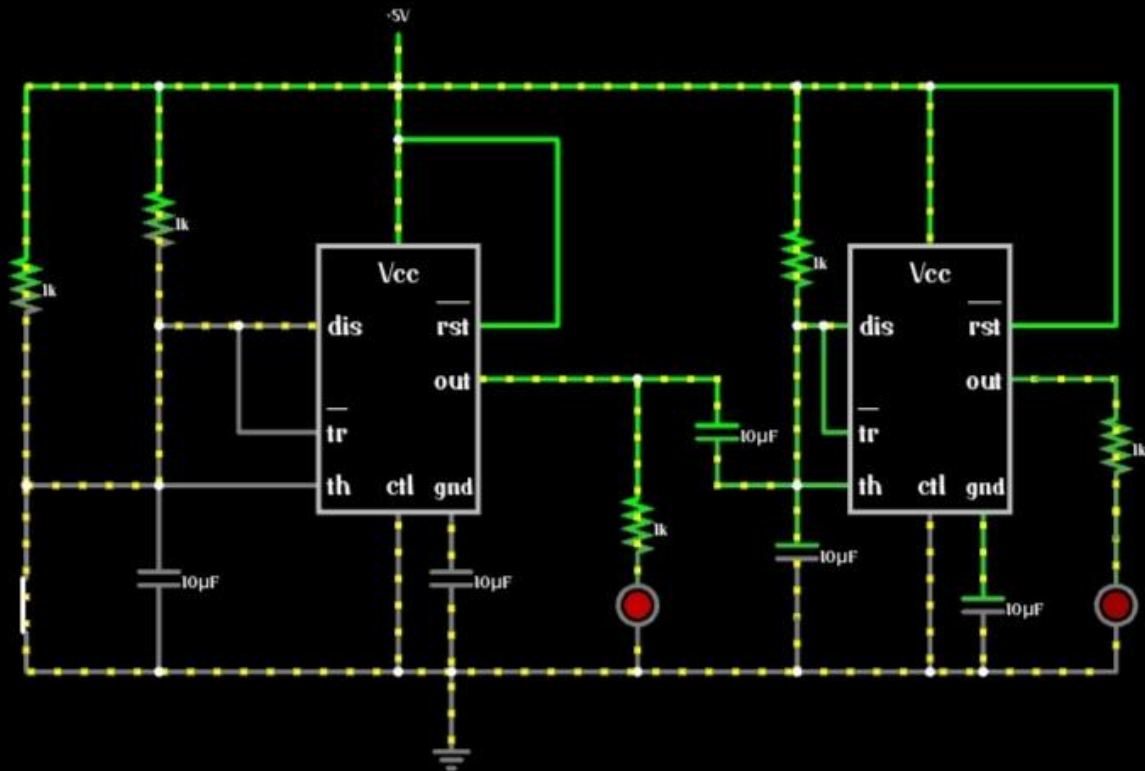


- ◆ Combines two independent timers in a single circuit to generate two different time delays or intervals.
- ◆ Typically uses a dual 555 timer (e.g., NE556) to operate in monostable or astable modes for separate timing functions.
- ◆ Used in multi-stage timing, pulse generation, and sequential operations in automation systems.

One shot timer

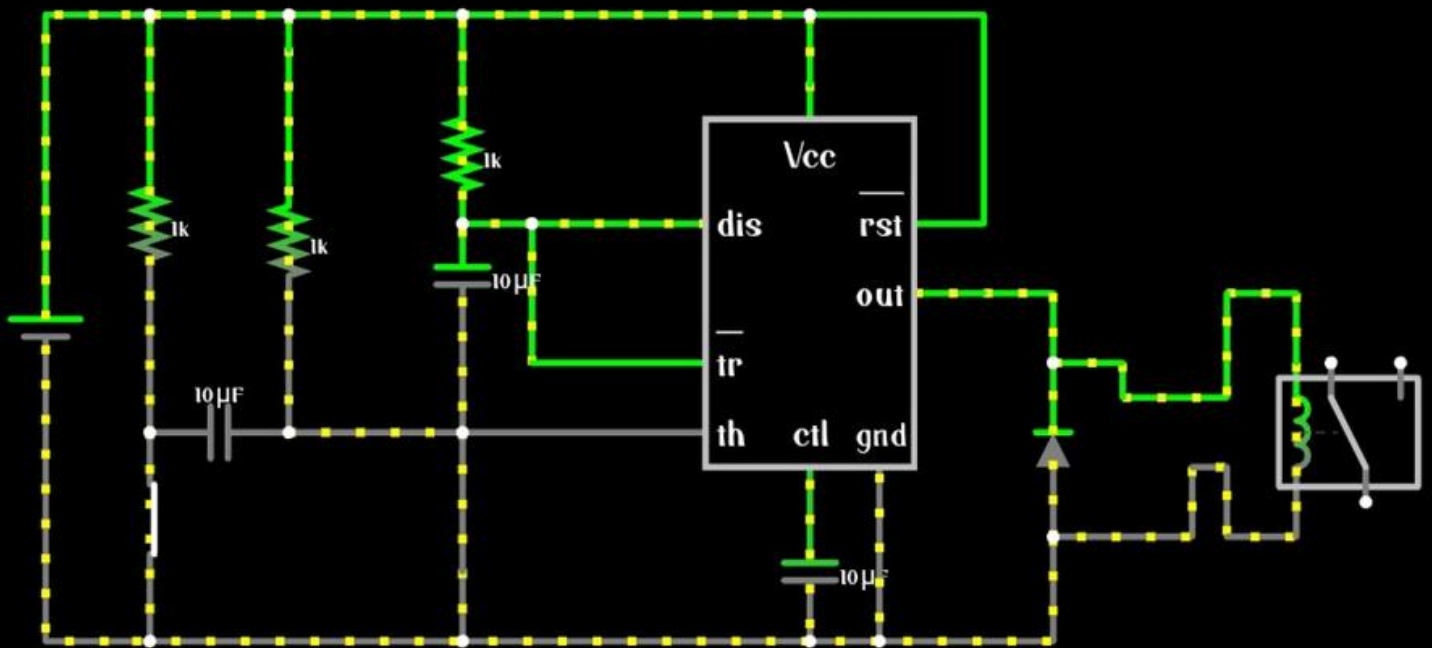


- ◆ Produces a single output pulse of a fixed duration when triggered.
- ◆ Operates in monostable mode, where the pulse width is determined by external resistor and capacitor values.
- ◆ Used in pulse generation, debouncing switches, and triggering events in digital circuits.

555 Timer LED blinking circuit

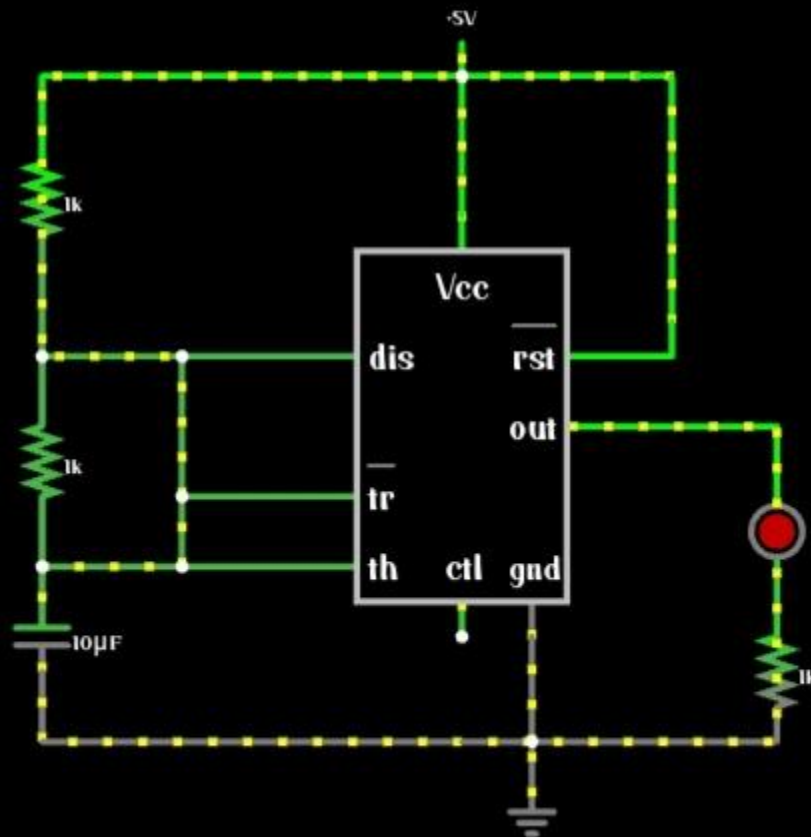


- ◆ Blinks an LED at a regular interval by generating a square wave.
- ◆ The 555 timer operates in astable mode, with the blinking rate controlled by external resistors and a capacitor.
- ◆ Used in basic LED indicators, signal testing, and timing demonstrations.

Pulse generator

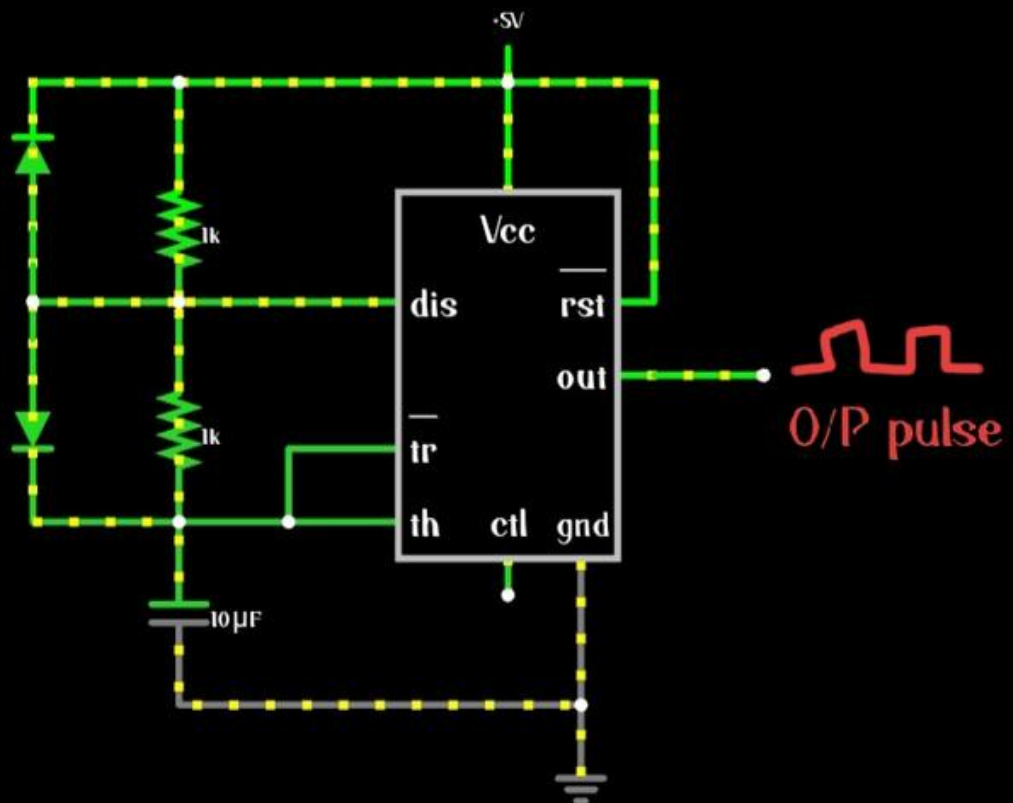

- ◆ Generates periodic pulses of a specific width and frequency.
- ◆ Often built using a 555 timer in astable mode, with pulse characteristics controlled by external components.
- ◆ Used in clock signal generation, testing digital circuits, and triggering applications.

Time delay relay circuit

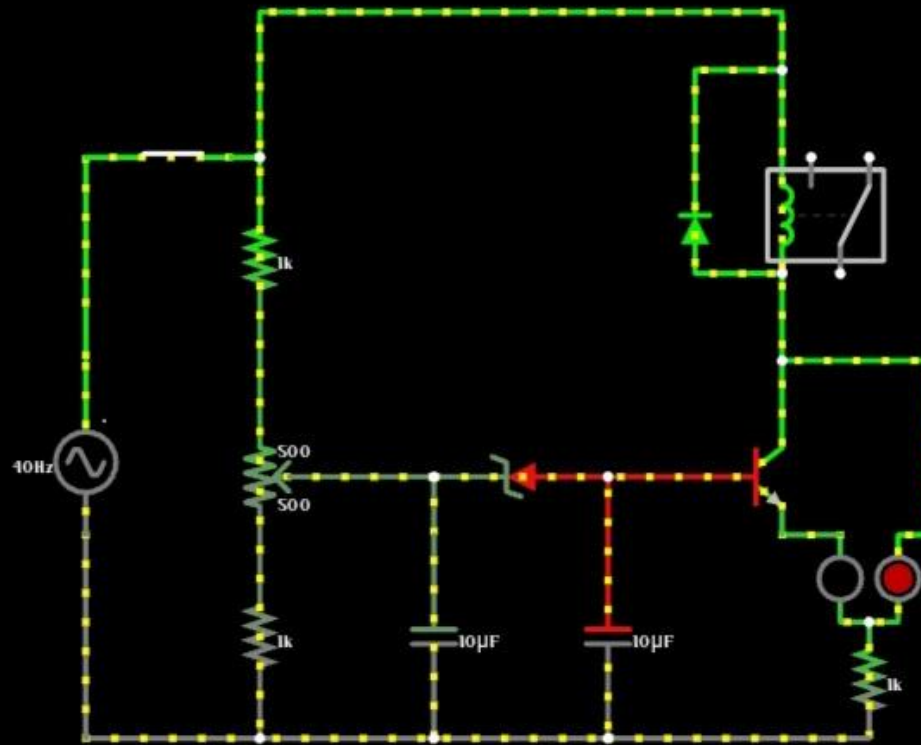


- ◆ Activates a relay after a preset time delay.

- ◆ Uses a 555 timer or similar device to generate a delay based on resistor and capacitor values, triggering the relay once the delay elapses.


- ◆ Used in automation systems, motor control, and delayed power-on circuits.

Temperature controlled fan

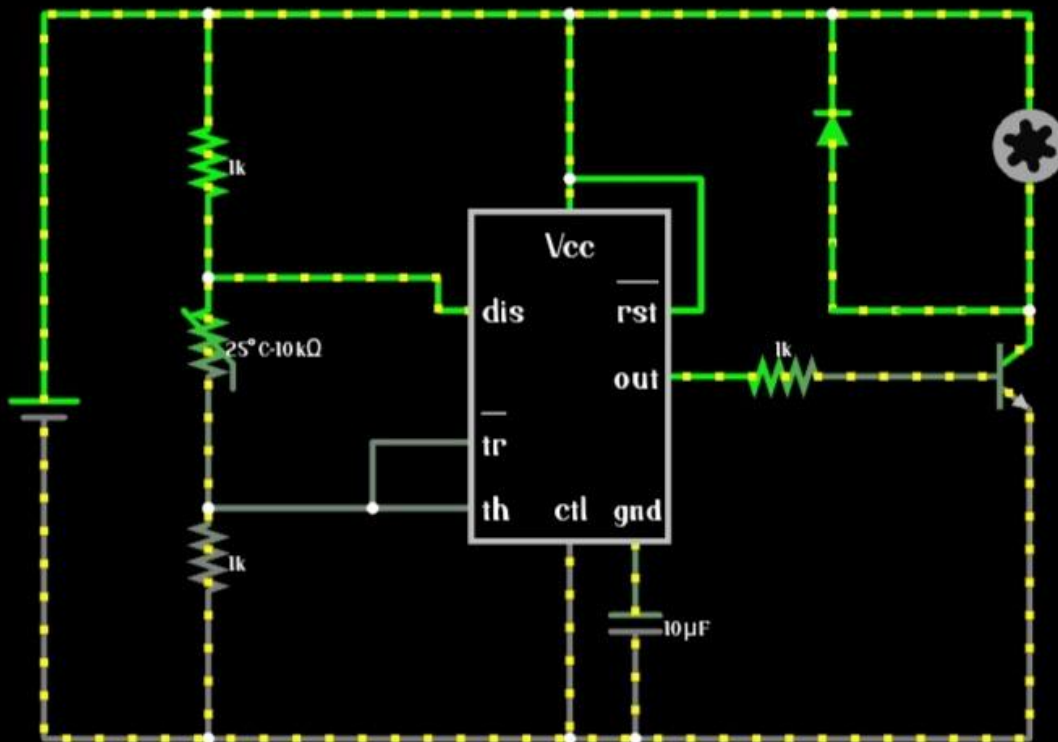


- ◆ Automatically adjusts the fan speed based on temperature changes.
- ◆ Uses a temperature sensor (e.g., thermistor or LM35) to detect heat levels and control the fan through a transistor or PWM signal.
- ◆ Used in cooling systems for electronics, HVAC systems, and appliances.

Motion detector alarm

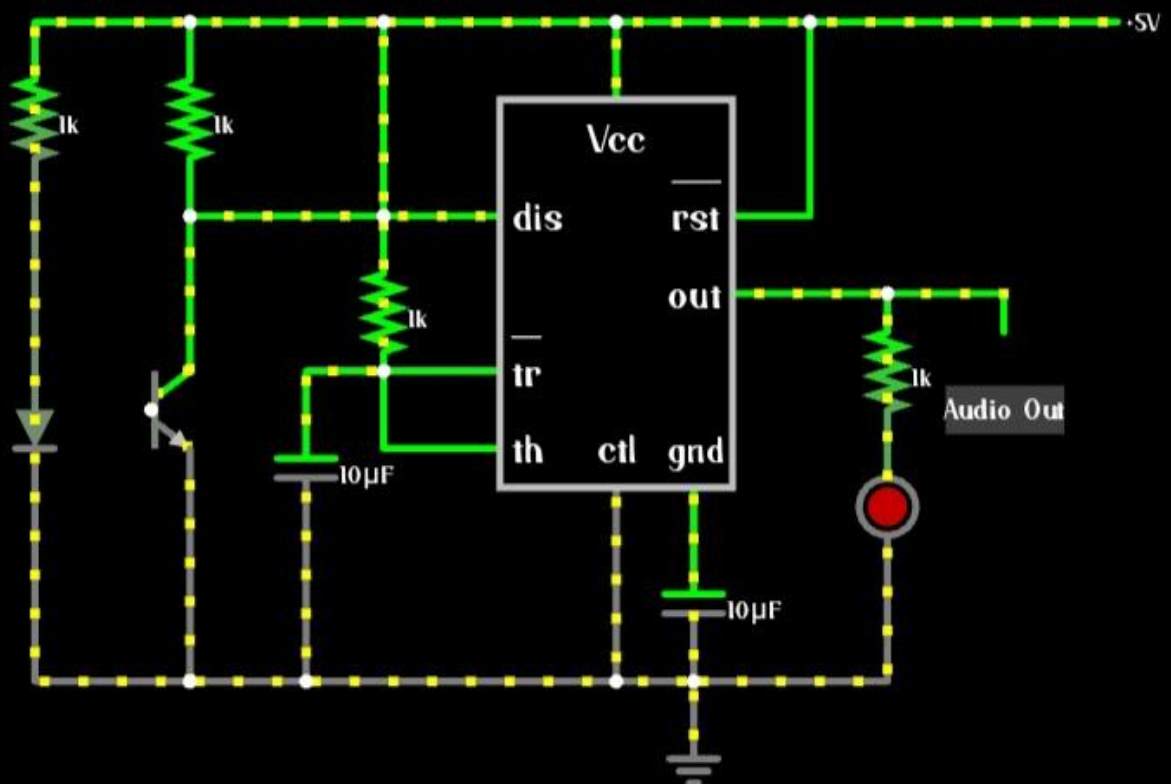


- ◆ Detects motion and triggers an alarm or alert system.
 - ◆ Uses a motion sensor to detect infrared radiation from moving objects, activating a buzzer or LED when motion is detected.
 - ◆ Used in security systems, automated lighting, and intrusion detection.

Class A amplifier

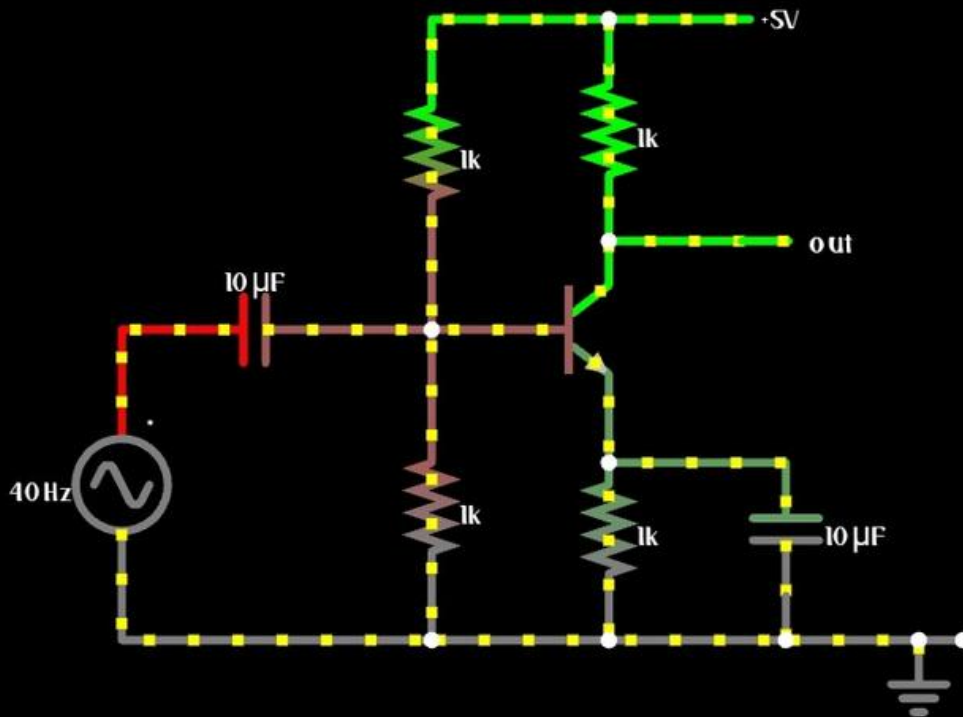


- ◆ Provides continuous amplification by operating in the linear region of the transistor for the entire input signal cycle.
- ◆ The transistor conducts throughout the signal cycle, resulting in high fidelity but low efficiency.
- ◆ Used in high-quality audio amplifiers, signal processing, and precision applications where linearity is crucial.

Class B amplifier

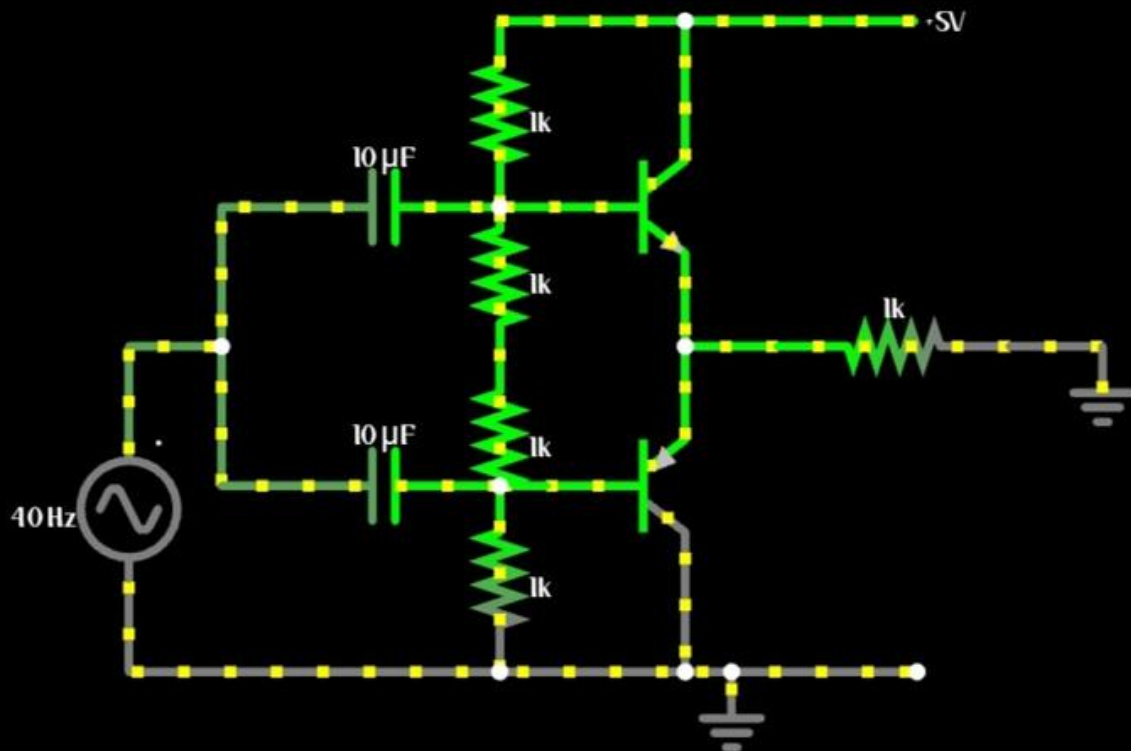


- ◆ Amplifies the input signal by using two active devices, each amplifying one half of the signal waveform.
- ◆ Each transistor or device conducts for 180° of the signal cycle, reducing power loss compared to Class A but introducing crossover distortion.
- ◆ Used in power amplifiers for audio systems, radio transmitters, and other applications.

Class AB amplifier

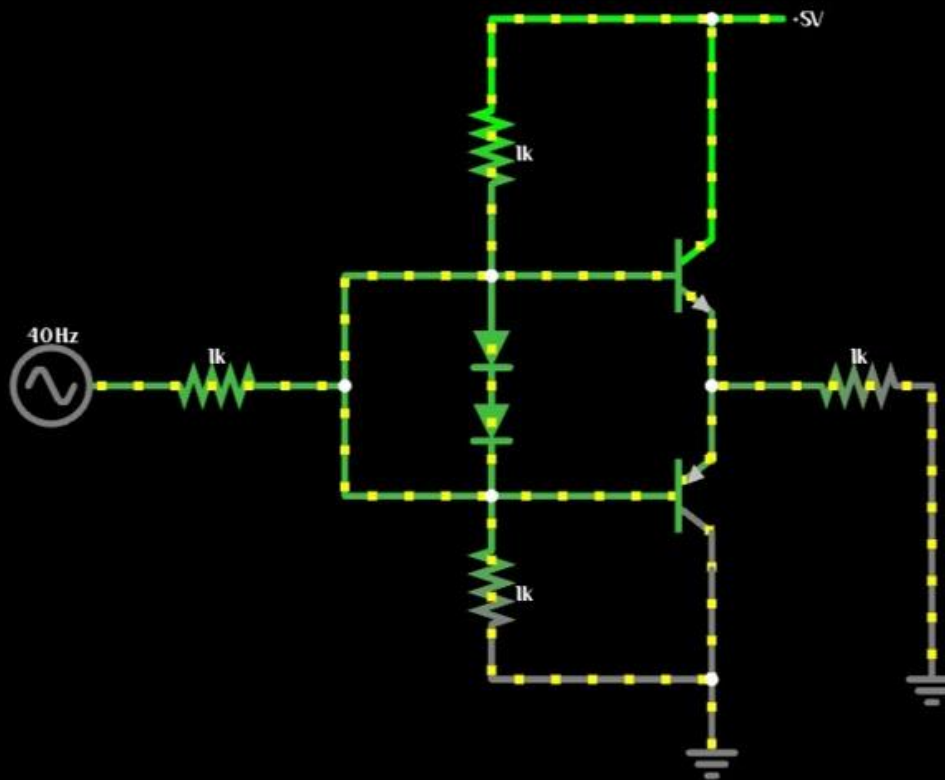


- ◆ Combines the advantages of Class A and Class B amplifiers, providing high linearity with improved efficiency.
- ◆ Each transistor conducts for more than half of the input signal cycle, reducing crossover distortion while maintaining better efficiency than Class A.
- ◆ Commonly used in audio amplifiers, home theater systems, and high-fidelity sound equipment.

Differential pair amplifier

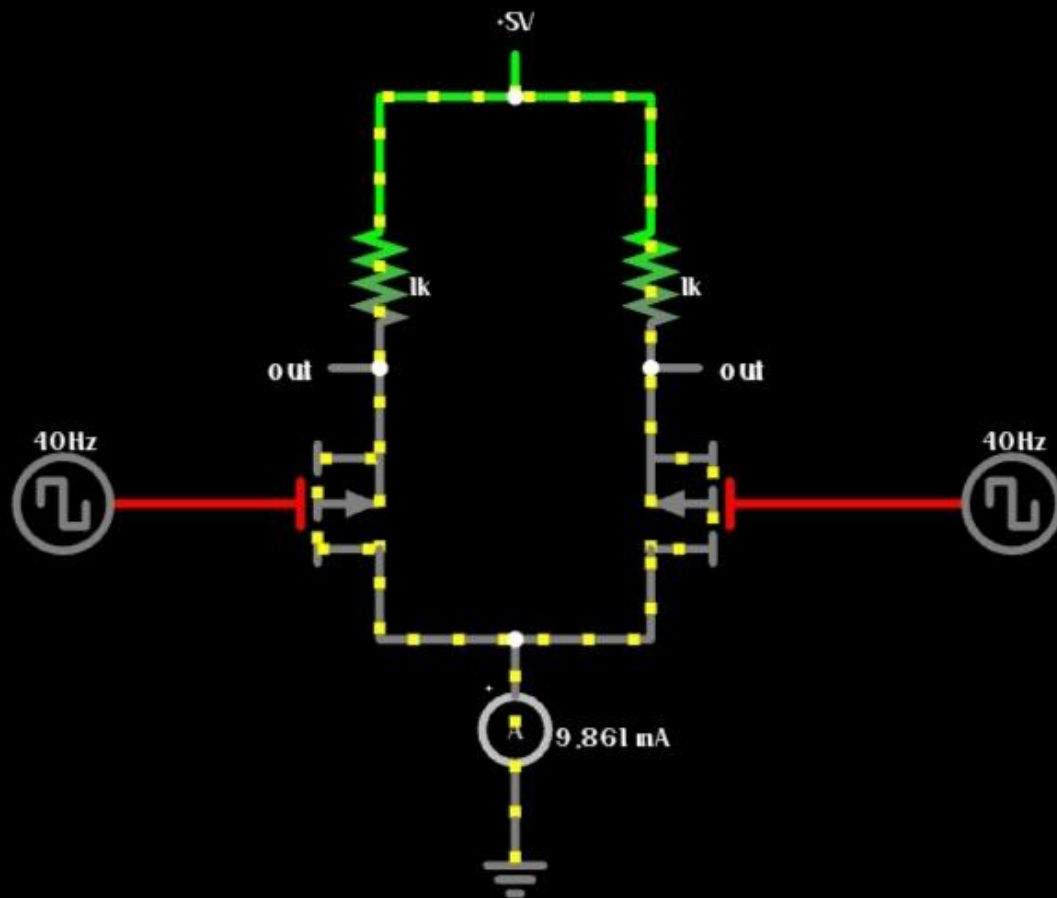


- ◆ Amplifies the voltage difference between two input signals.
- ◆ Uses two transistors to amplify the difference while rejecting common-mode noise.
- ◆ Used in operational amplifiers, audio systems, and instrumentation for noise rejection.

Common Emitter amplifier

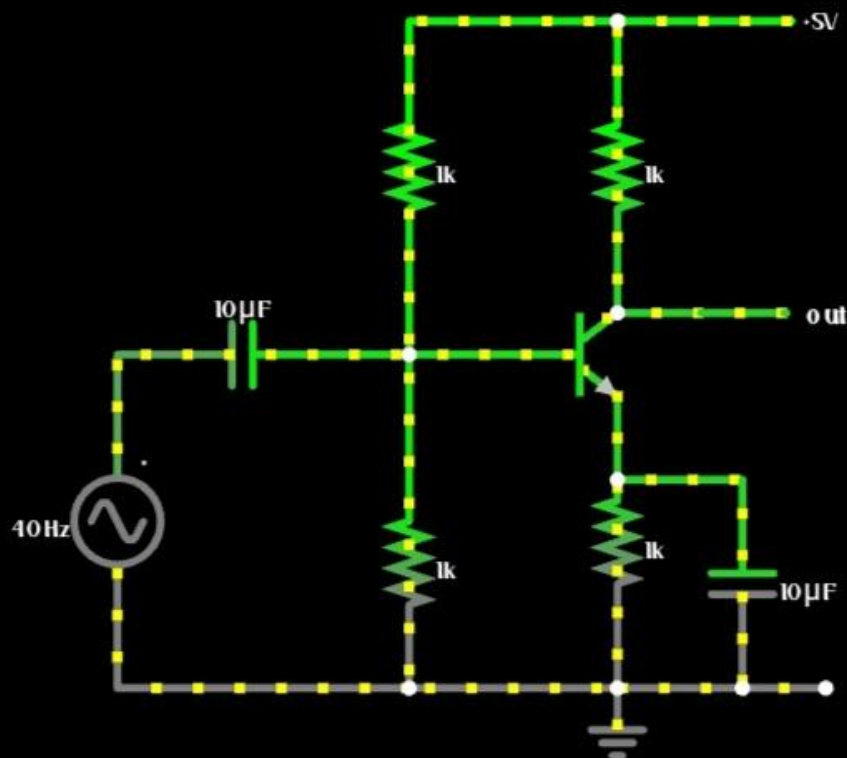


- ◆ Provides voltage amplification with moderate gain and phase inversion.
- ◆ The input signal is applied to the base, and the amplified output is taken from the collector, with the emitter typically grounded.
- ◆ Used in signal amplification for audio and RF circuits, as well as in analog signal processing.

Common collector amplifier

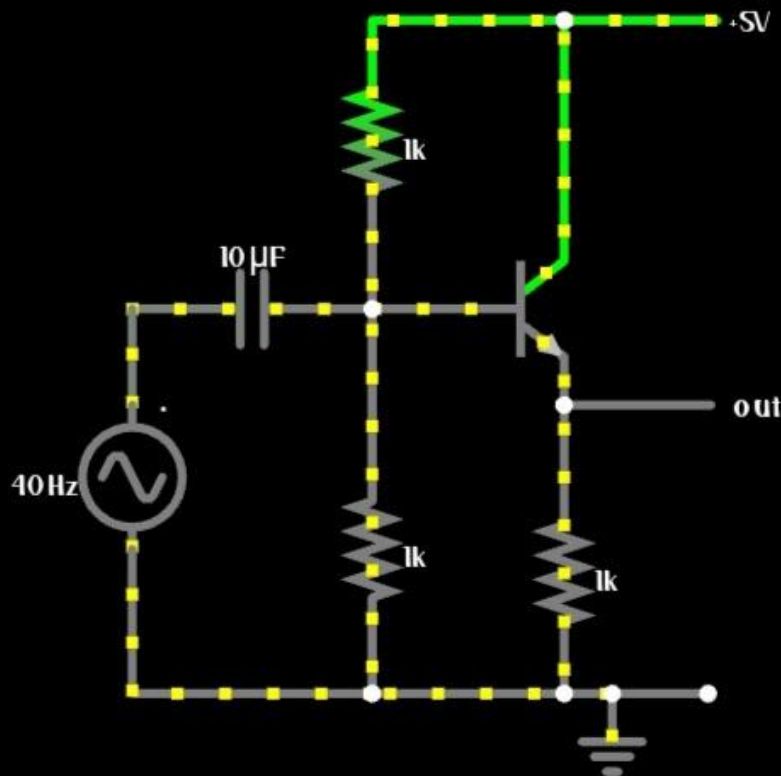

- ◆ Provides voltage gain with high input impedance and low output impedance, acting as a buffer.
- ◆ The input signal is applied to the base, with the output taken from the emitter, resulting in no phase inversion.
- ◆ Used in impedance matching, signal buffering, and as a voltage follower in various electronic circuits.

Common base amplifier

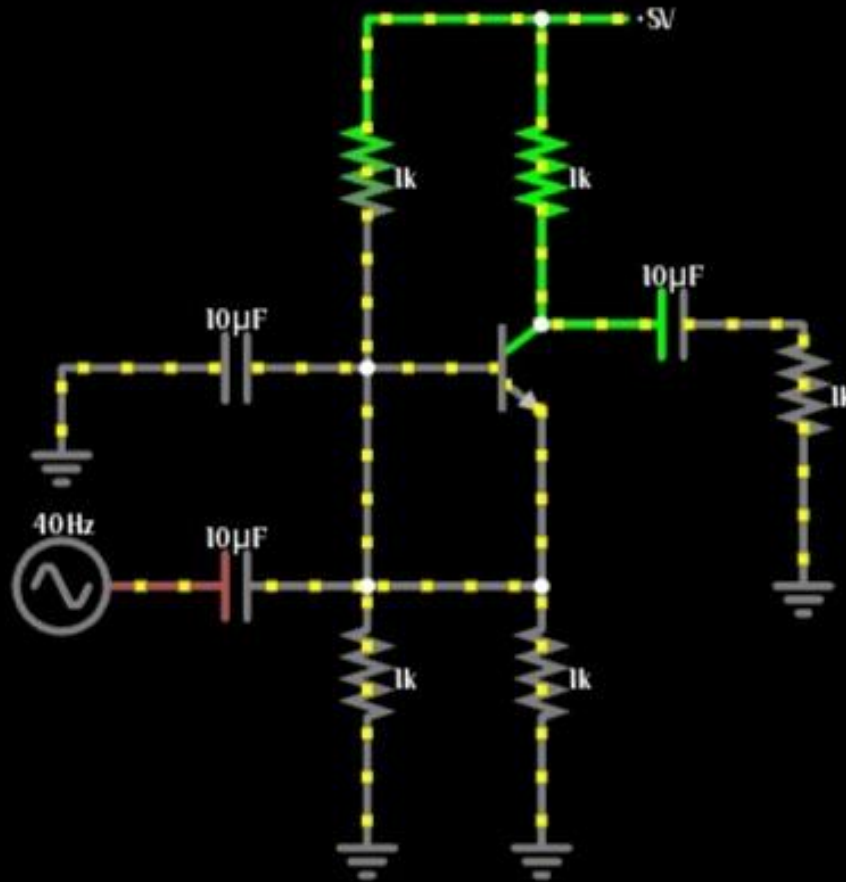

- ◆ Provides voltage amplification with low input impedance and high output impedance.
- ◆ The input signal is applied to the emitter, with the output taken from the collector, resulting in no phase inversion.
- ◆ Used in high-frequency applications, such as RF amplifiers and impedance matching in communication systems.

Darlington pair amplifier




- ◆ Provides high current gain by combining two transistors in a way that amplifies current more efficiently.
- ◆ The output of the first transistor is connected to the base of the second, resulting in a combined current gain while maintaining the voltage gain characteristics.
- ◆ Used in power amplifiers, audio amplifiers, and driver circuits where high current gain is required.

Push - pull follower




- ◆ Provides efficient amplification by using two transistors to handle both positive and negative halves of the signal.
- ◆ One transistor amplifies the positive half of the signal, while the other amplifies the negative half, improving efficiency and reducing distortion.
- ◆ Used in power amplifiers, audio systems, and signal amplification where high efficiency and low distortion are essential.

Op amps instrumentation amplifier

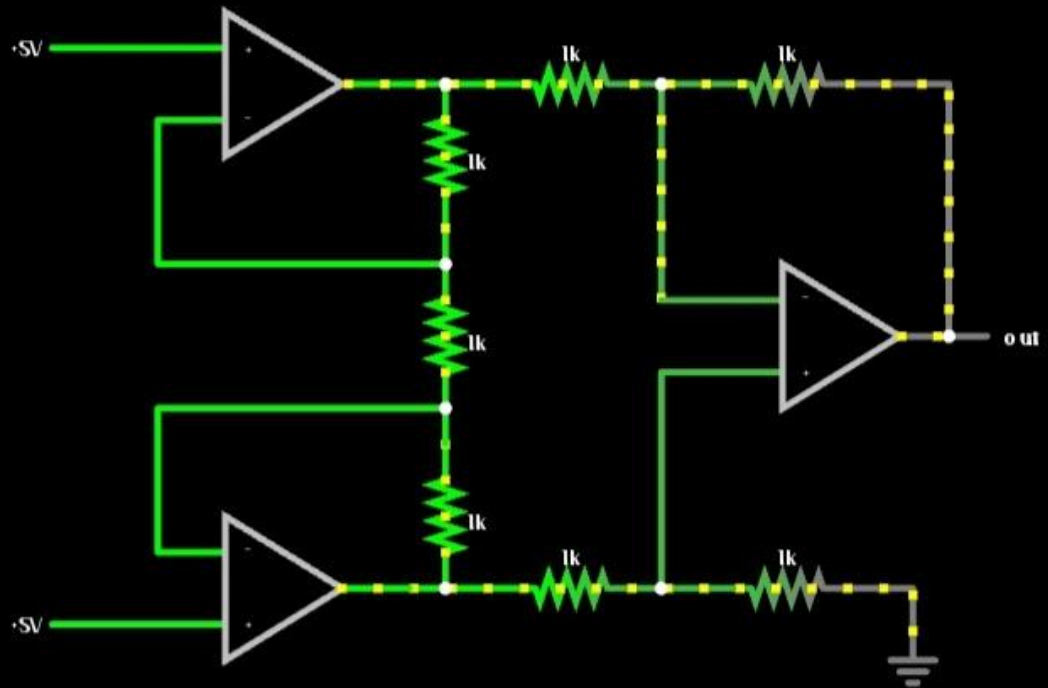

- ◆ Amplifies the difference between two input signals while rejecting common-mode noise.
- ◆ Consists of three op-amps, with two forming a differential amplifier and the third providing gain control, ensuring high input impedance and precise output.
- ◆ Used in applications requiring high accuracy and noise rejection, such as sensor signal amplification.

Resistor cube

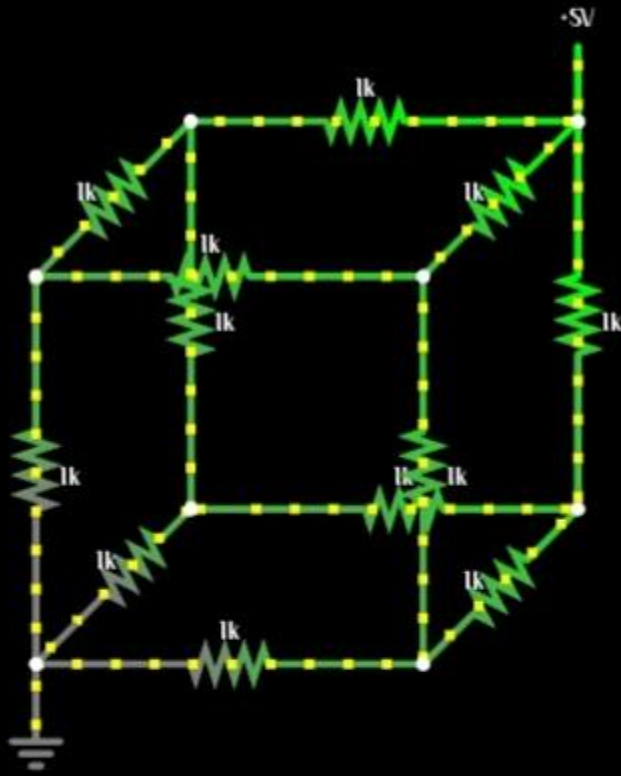


- ◆ A symmetrical network of resistors arranged in a cube structure to analyze equivalent resistance between any two points.
- ◆ Uses symmetry and network analysis techniques to calculate the total resistance based on series and parallel combinations.
- ◆ Commonly used in circuit theory problems and for teaching network analysis concepts.

Resistor grid




- ◆ A network of resistors arranged in a grid pattern to calculate equivalent resistance between two nodes.
- ◆ Uses series-parallel reduction and symmetry, or advanced techniques like Kirchhoff's laws for complex grids.
- ◆ Used in teaching network analysis, circuit theory problems, and resistance measurement studies.

Voltage level detector

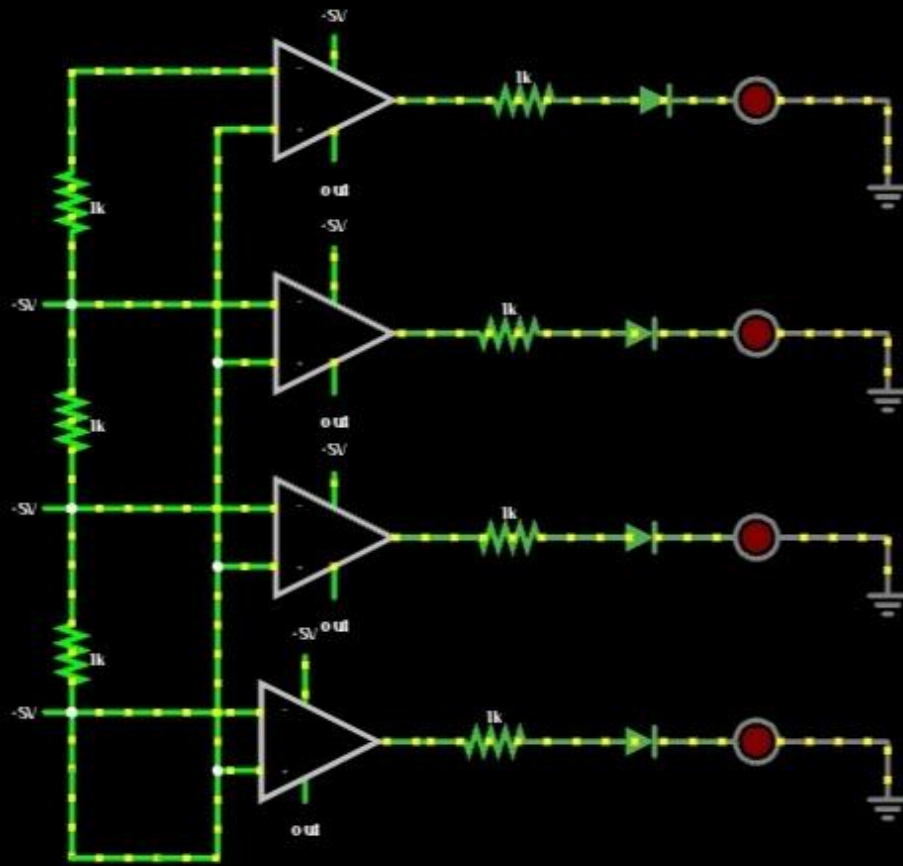


- ◆ Detects and compares input voltage against a reference voltage to indicate specific voltage levels.
- ◆ Uses a comparator or operational amplifier to output a high or low signal based on the input voltage relative to the reference.
- ◆ Used in battery level indicators, power supply monitoring, and threshold detection systems.

Digital sine wave

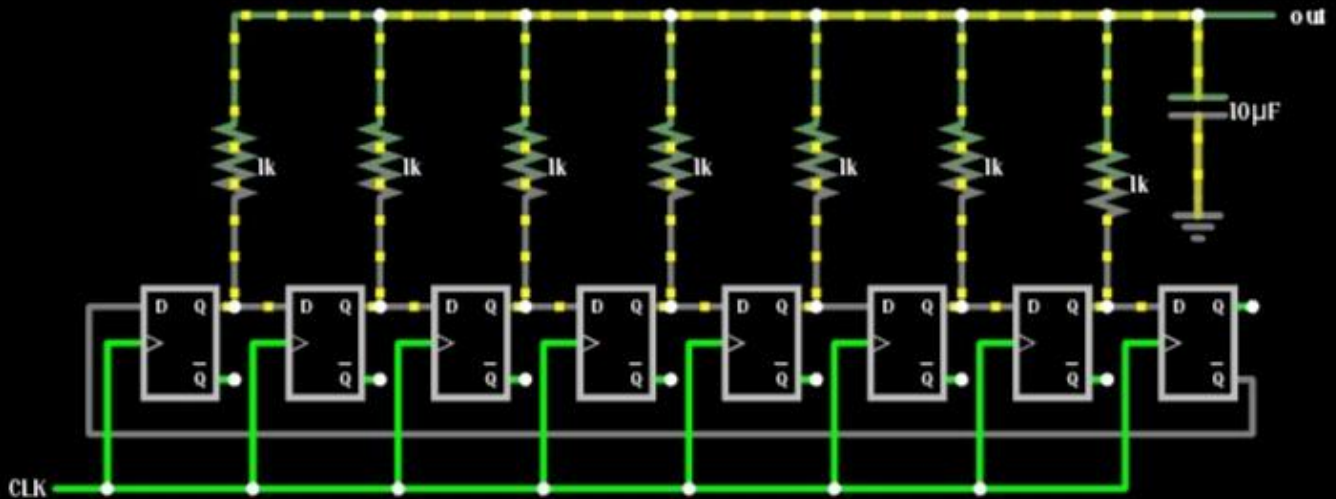


- ◆ Generates a sine wave signal using digital techniques, often for testing or modulation purposes.
- ◆ Utilizes a microcontroller, DAC, or digital logic to create a sine wave through waveform synthesis methods like lookup tables or PWM.
- ◆ Used in signal processing, communication systems, and waveform testing.

Transmission line termination

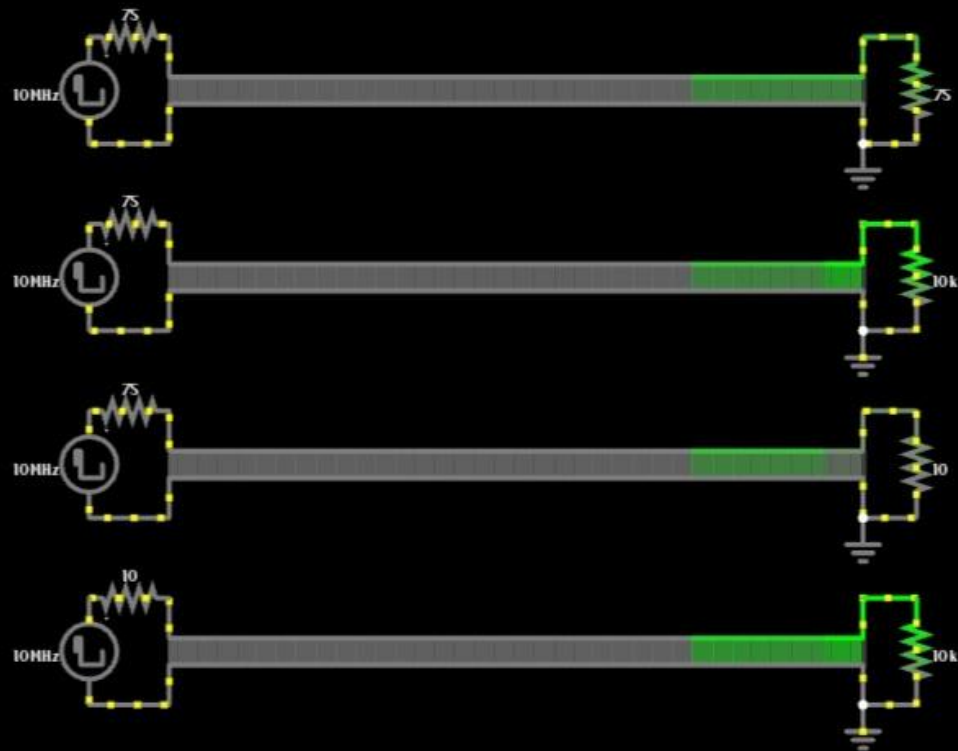


- ◆ Reduces signal reflections by matching the line's impedance.
- ◆ Demonstrates the effect of proper and improper terminations on signal integrity.
 - ◆ Used in RF systems and high-speed communication to ensure signal fidelity.

Audio power amplifier

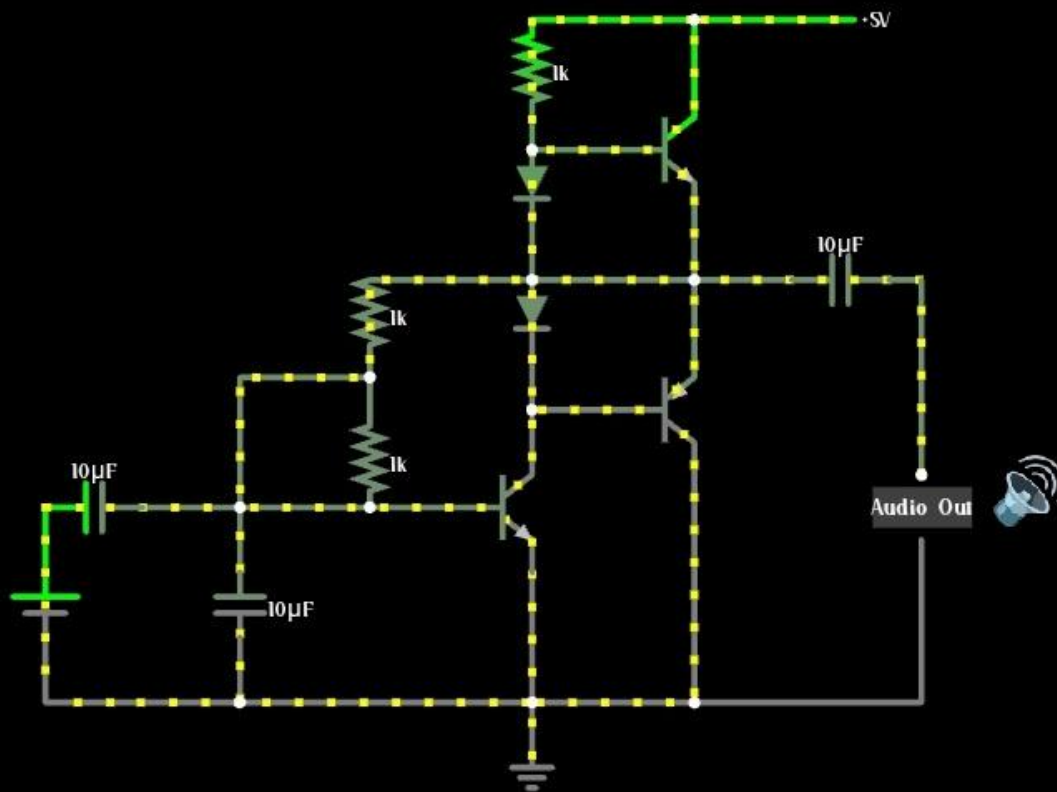


- ◆ Amplifies low-power audio signals to drive speakers or headphones.
- ◆ Boosts the signal's power using transistors or ICs while maintaining audio quality.
- ◆ Used in sound systems, home theaters, and portable audio devices.

Frequency doubler

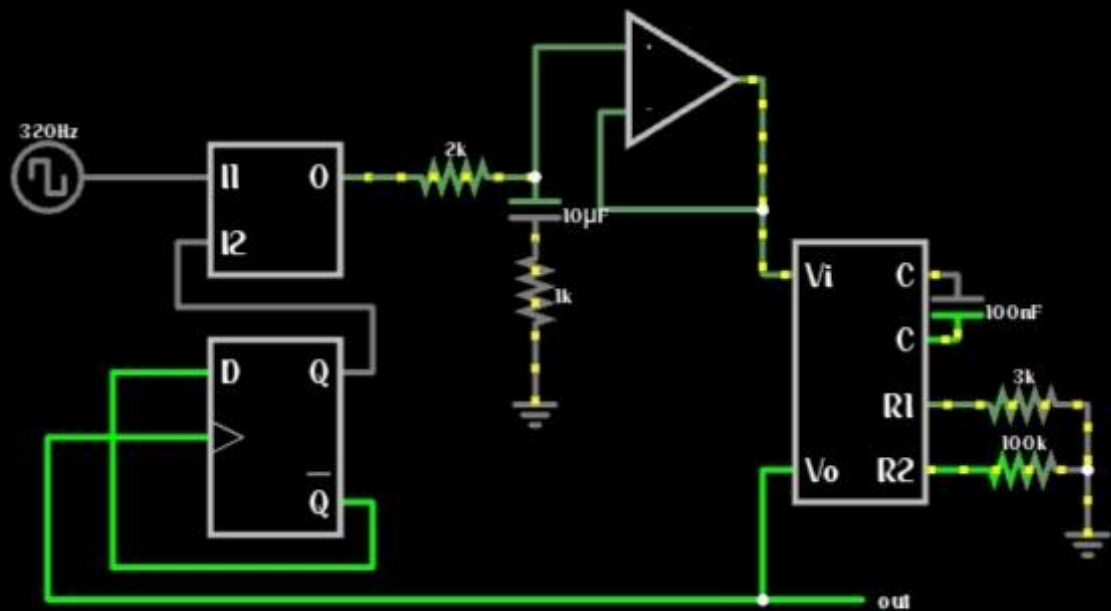


- ◆ Generates an output signal with double the frequency of the input signal.
- ◆ Uses nonlinear components like diodes or op-amps to create harmonics, extracting the second harmonic as the output.
- ◆ Used in RF communication, signal processing, and waveform generation.

Touch switch

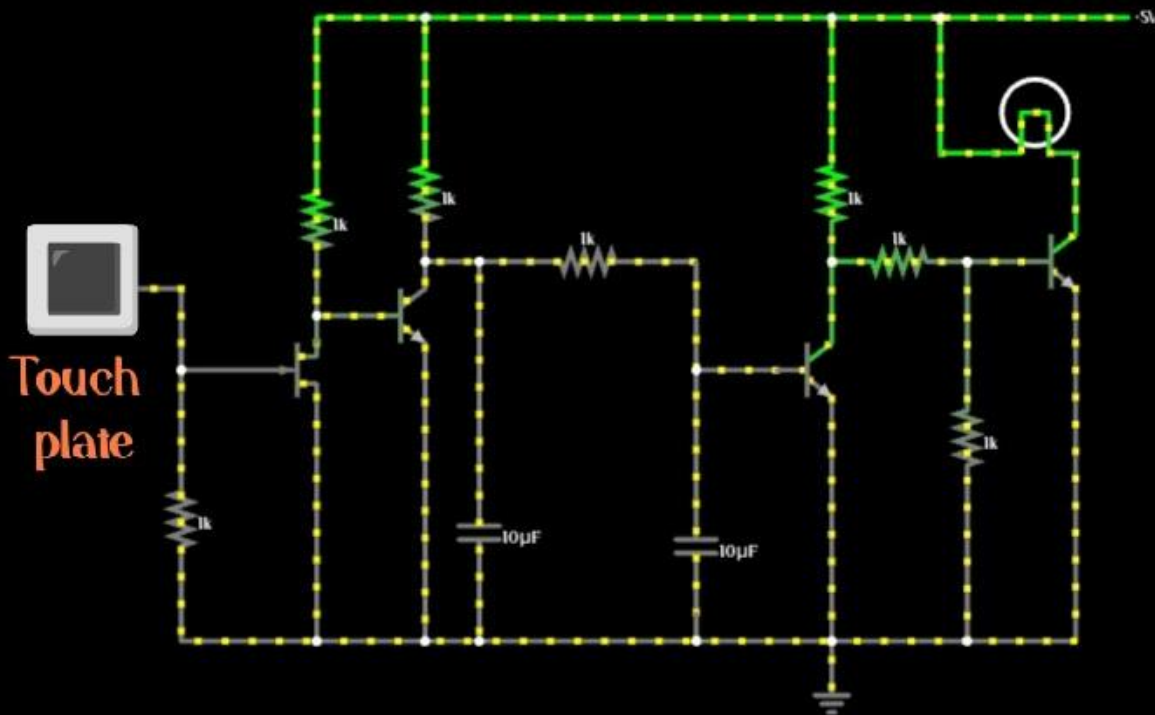


- ◆ Activates a circuit or device by detecting a user's touch, usually through capacitive or resistive sensing.
- ◆ Detects changes in capacitance or resistance when a finger touches the sensor, triggering an action like turning on or off.
- ◆ Common in consumer electronics, home automation, touchscreens, appliances, automotive systems, and security devices.

Marx generator

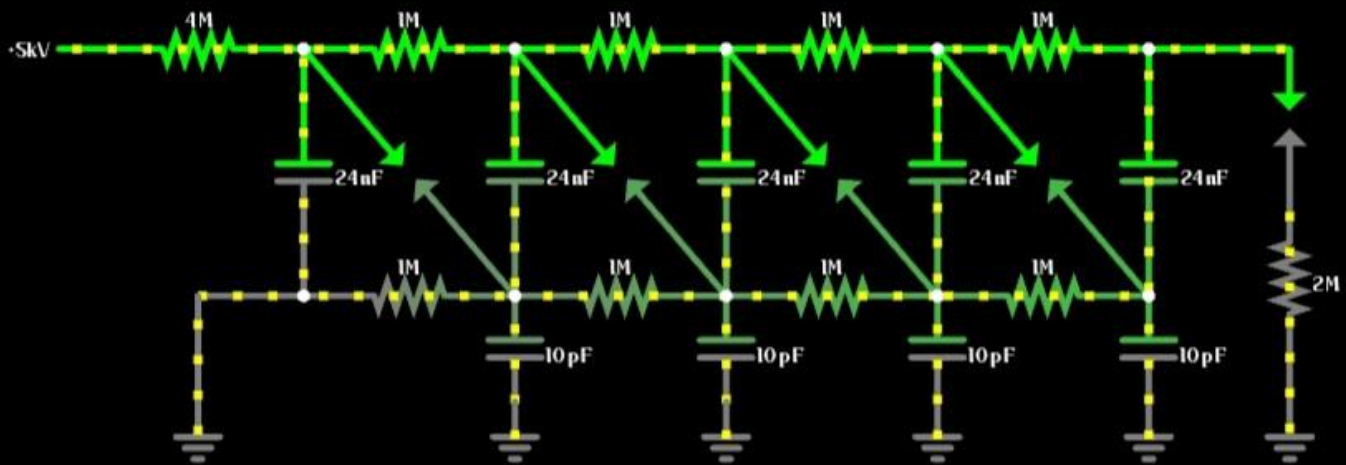

- ◆ Produces high-voltage pulses by charging capacitors in parallel and discharging them in series.
- ◆ Capacitors charge and discharge through spark gaps to create a high-voltage output.
- ◆ Used in high-voltage testing, pulsed power systems, and particle accelerators.

Traffic light

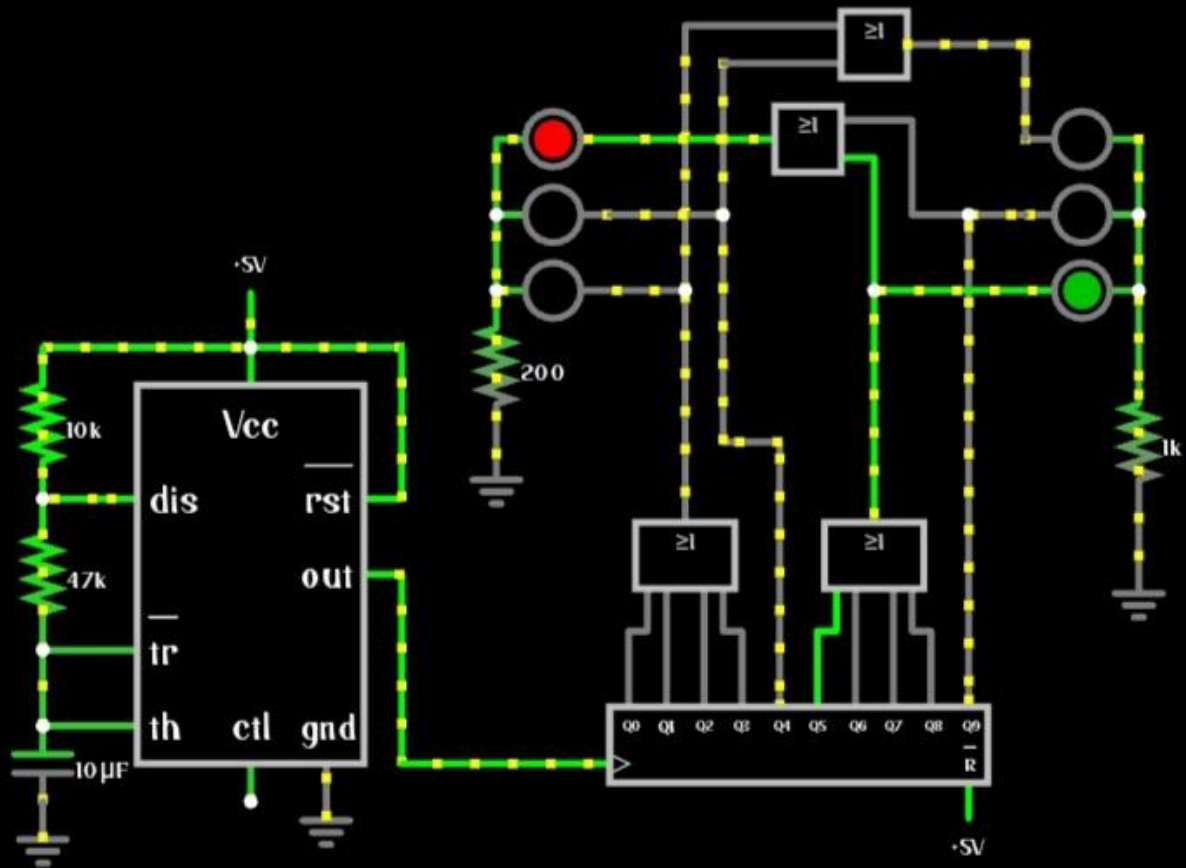

- ◆ Controls the flow of traffic by using colored lights (red, yellow, green) to indicate stop, caution, or go.
 - ◆ A timer system switches the lights in a cycle to manage vehicle and pedestrian movement.
- ◆ Found at road intersections, pedestrian crossings, and busy traffic areas to ensure safety and efficient traffic management.